

M.A.H

7 new projects

eLektor

www.elektor.com

Cloud Altimeter

the sky is not the limit



+ VisiOLED


+ DIY Fuel Cells

+ MPPT Regulator

+ EV Charger

dsPIC Control Board

for major applications

 

Worry-free Drilling

a hands-on test of pipe & wire locators



SPEED.
FLEXIBILITY.
PERFORMANCE.

Vinculum VNC2

A programmable system-on-chip dual USB 2.0 host/ slave controller.

- Handles USB host interfaces and data transfer functions using the in-built 16-bit enhanced MCU with 256 kbyte Flash and 16kbyte RAM.
- Royalty-free flexible 'C' language Integrated Development Environment including compiler, drivers, libraries and RTOS kernel to provide the designer with the ability to customise their own firmware.
- Libraries for several USB classes FAT file system support.
- Interfaces to UART, FIFO, SPI Slave, SPI Master and PWM.
- Multiple package size options including VNC1L pseudo compatible option, provide cost effective solutions for the different applications.
- Time to market can be reduced using the wide range of available development modules.



USB MADE EASY


www.ftdichip.com



WE MAKE IT SIMPLE

MikroElektronika is a well-known manufacturer of a wide range of development tools, compilers for various microcontroller families and books for electronics. Our goal is to provide our customers with reliable, high-quality, yet cost-effective products as well as the first-rate service.

 
EXPERIENCE THE EASE OF CREATING YOUR OWN ELECTRONIC DEVICE WITH OUR DEVELOPMENT TOOLS



Mikroelektronika manufactures competitive development systems suitable for programming and experimenting with different microcontroller families such as PIC®, dsPIC®30F, dsPIC®33/PIC®24, PIC32®, AVR®, PSoC®, 8051 and ARM®. They feature numerous on-board modules but also have the possibility of improving their performance by interfacing additional modules ordered separately.



 MAKE A GREAT CODE FOR YOUR MICROCONTROLLER WITH OUR COMPILERS



Mikroelektronika also manufactures compilers and integrated development environments for popular microcontroller families. Mikroelektronika offers C, BASIC and Pascal compilers for PIC®, dsPIC®30/33-PIC®24, AVR® and 8051 microcontrollers.

- FREE PRODUCT LIFETIME TECHNICAL SUPPORT
- FREE UPDATES OF NEW COMPILER VERSIONS
- WIDE-RANGE OF SUPPORTED MICROCONTROLLERS
- NUMEROUS EASY TO USE PRACTICAL EXAMPLES

LEARN MORE ABOUT MICROCONTROLLERS AND HOW TO USE THEM WITH OUR BOOKS



What are microcontrollers, anyway? Electronics built into one single chip capable of controlling a small submarine, a crane or an elevator... It's up to you to decide what you want them to do. Just dump a program containing appropriate instructions into the chip...

EXPLORE CAPABILITIES OF MICROCONTROLLERS WITH OUR ACCESSORY BOARDS

Accessory boards are designed to allow students and engineers as well to easily experiment and explore the capabilities of various microcontrollers when connected to peripheral modules such as ADC, DAC, CAN communication module, Ethernet, IrDA, MP3, RS485 module etc.

Energetic with energy

Although we are all electronics-minded people here at Elektor and this edition has a focus on sustainable energy sources and new ways of reducing energy consumption, it's curious and worrying to note that it took decades until electronics finally gets utilized to reduce the negative effects of, and created by, electronics itself. To be fair, that's the electronics at the heart of electrical equipment doing the actual amps guzzling from the wall outlet. It also underscores the powerful effect of good electronic design in high-energy consumption systems. Let's consider an industry-grade electric heater with a remote thermostat 'embedded style'. As much as the microcontroller manufacturers will like to tell you that their 32-bit XYZ product is now down to nano-amp standby current and awake in nanoseconds in response to a non-maskable interrupt or a key press, you should not care too much and get down to programming. Actually one second less of heater-on time due to smarter programming of the micro will result in a real energy saving and less carpet eating by the CFO as a result of the monthly energy bill (delivered to him/her by post). This year's Embedded Systems show in Nuremberg was all about 'green approaches' suitably backed by 'rapid prototyping' — see page 44. On the face of it, that's a logical combination — if you can't do the programming and prototyping in 'like' under 10 minutes including removing the kit from the plastic blister packaging you are wasting valuable energy. Interfacing microcontrollers to the real world has never been easier and the traditional gap between the pale pizza-fed programmer and the construction engineer wielding big spanners and 'doing the AC stuff' seems to vanish rapidly. The dsPIC board on page 20 and the associated solar heat collector application on page 26 are green as can be but fail miserably in terms of rapid prototyping, so don't tell anyone and optimise the system programming like a good engineer should. We're providing all the materials and design information to get you going, like a good publisher should, and it shall be our silent mutual understanding, satisfaction and enjoyment once the system operates exactly as you want it and you've experienced a steep learning curve. Agreed? We put a lot of energy in it — not all electrical I'm glad to say.

Jan Buiting, Editor



6 Colophon

Corporate information on Elektor magazine.

8 News & New Products

A monthly roundup of all the latest in electronics land.

14 Clean Power from Hydrogen

Hydrogen appears to be a very promising candidate for mobile applications so let's have a look at what you can actually do with fuel cells.

20 dsPIC Control Board

A heavyweight control board for industrial applications like motor control.

26 Solar Thermal Energy Regulator

Put this board is at the hub of your solar collectors, valves, pumps and hot water storage tanks.

32 Worry-free Drilling

Thirteen pipe and wire locators tested and compared for their ability to detect electrical wiring, wood and water pipes in walls.

40 Make Room for the Roomba!

At Elektor we like to take things apart. This month a Roomba robot vacuum cleaner was our unsuspecting victim.

42 Design Tip: Star LED instead of incandescent lamp



Caveats and considerations on one for one replacement, which may not be feasible in all cases.

43 Measured again ...

Further investigation into power factor correction (PFC) of LED lamps — with worrying results.

44 Embedded World 2010

  A report on the world's largest show on microcontrollers and embedded technologies.



CONTENTS

Volume 36
May 2010
no. 401

20 dsPIC Control Board

The control board based on the dsPIC30F6010A microcontroller 'Plus' has been designed for incorporation into typical industrial electronics applications like controlling motors or adjustment of static up- or down-converters.

26 Solar Thermal Energy Regulator

This board is useful for regulating installations comprising several sets of solar collectors with different orientations or configurations with several hot-water storage tanks, requiring several valves and pumps to be controlled.

32 Worry-free Drilling

A pipe and wire locator (called stud locator in the USA) can come in very handy for locating all sorts of things inside walls before you start drilling, including electrical wiring, pipes, and even joists or studs. We tested thirteen different models in the Elektor lab to see what they can (and can't) do and how deep they can find studs, joists, pipes and wiring inside walls.

48 Cloud Altitude Meter

'AirControl' is a portable instrument indicating cloud altitude by measuring air temperature and humidity and then silently doing a mass of scientific calculations. It should make an interesting meteorological tool for people who keep an eye on the sky.

46 The making of the dsPIC board (2)

Straight from the Elektor lab, the how-it-got-designed story of the dsPIC control board featured in this issue.

48 Cloud Altitude Meter

Here's Aircontrol, a portable instrument that will tell you the height of the cloud base straight above you.

54 In-vehicle CO₂ Meter

This fast responding CO₂ meter for use in cars reliably detects air conditions that can lead to loss of concentration. Time to open a window!

58 VisiOLED

An ATM18 based wireless door opener using RFID for visitor identification, with his/her face appearing on an OLED display.

64 Colossus – the Rebuild

Resurrected and now on display at Bletchley Park, the 1943 computer with its valve-based XOR functions that helped crack Enigma encrypted messages in WW2.

68 Low-cost Electric Vehicle Charge Station

Here comes the roadside coin-operated kWh vending machine; EV owners will like this!

74 Retronics: Grid Dipper (ca. 1950)

Regular feature on electronics 'odd & ancient'.

77 Hexadoku

Our monthly puzzle with an electronics touch.

84 Coming Attractions

Next month in Elektor magazine.

Elektor International Media provides a multimedia and interactive platform for everyone interested in electronics. From professionals passionate about their work to enthusiasts with professional ambitions. From beginner to diehard, from student to lecturer. Information, education, inspiration and entertainment. Analogue and digital; practical and theoretical; software and hardware.

elektor
 ANALOGUE • DIGITAL
 MICROCONTROLLERS & EMBEDDED
 AUDIO • TEST & MEASUREMENT

Volume 36, Number 401, May 2010 ISSN 1757-0875

Elektor aims at inspiring people to master electronics at any personal level by presenting construction projects and spotting developments in electronics and information technology.

Publishers: Elektor International Media, Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England. Tel. (+44) 208 261 4509, fax: (+44) 208 261 4447 www.elektor.com

The magazine is available from newsagents, bookshops and electronics retail outlets, or on subscription. Elektor is published 11 times a year with a double issue for July & August.

Elektor is also published in French, Spanish, American English, German and Dutch. Together with franchised editions the magazine is on circulation in more than 50 countries.

International Editor:
 Wisse Hettinga (w.hettinga@elektor.nl)

Editor: Jan Buiting (editor@elektor.com)

International editorial staff: Harry Baggen, Thijs Beckers, Eduardo Corral, Ernst Krempelsauer, Jens Nickel, Clemens Valens.

Design staff: Antoine Authier (Head), Ton Giesberts, Luc Lemmens, Daniel Rodrigues, Jan Visser, Christian Vossen

Editorial secretariat:
 Hedwig Hennekens (secretariaat@elektor.nl)

Graphic design / DTP: Giel Dols, Mart Schroijen

Managing Director / Publisher: Paul Snakkers

Marketing: Carlo van Nistelrooy

Subscriptions: Elektor International Media, Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England. Tel. (+44) 208 261 4509, fax: (+44) 208 261 4447 Internet: www.elektor.com/subs

NEW!

DVD Masterclass High-End Valve Amplifiers

Specifically for audio designers, audiophiles, DIY enthusiasts etc.



In this Masterclass Menno van der Veen will examine the predictability and perceptibility of the specifications of valve amplifiers. Covered are models that allow the characteristics of valve amplifiers to be explored up to the limits of the audible domain from 20 Hz to 20 kHz. This then leads to the minimum stability requirements that the amplifier has to satisfy. The coupling between output valves and output transformer are also modeled.

Including:

- 3.5 hours of Video material
- PowerPoint presentation (74 slides)
- Scanned overhead sheets (22 sheets)
- AES Publications mentioned during the Masterclass

Contents:

Part 1 Preamplifiers

Equivalent schematics, limits in the frequency.

Part 2 Power amplifiers

Modeling of class A to B, interaction of the specifications for Output Transformers (OPTs) and frequency range and damping factor.

Part 3 Negative feedback

How negative feedback can be done right, remarkable experiments in the project.

Part 4 Output transformers

Limitations and possibilities of the output transformer.

ISBN 978-0-905705-86-6 • £24.90 • US \$40.20

elektor

Further information and ordering at
www.elektor.com/shop

Email: subscriptions@elektor.com
Rates and terms are given on the Subscription Order Form.

Head Office: Elektor International Media b.v.
P.O. Box 11 NL-6114-ZG Susteren The Netherlands
Telephone: (+31) 46 4389444. Fax: (+31) 46 4370161

Distribution:
Seymour, 2 East Poultry Street, London EC1A, England
Telephone: +44 207 429 4073

UK Advertising:
Huson International Media, Cambridge House,
Gogmore Lane, Chertsey, Surrey KT16 9AP, England.
Telephone: +44 1932 564999, Fax: +44 1932 564998

Email: r.elgar@husonmedia.com
Internet: www.husonmedia.com
Advertising rates and terms available on request.

Copyright Notice

The circuits described in this magazine are for domestic use only. All drawings, photographs, printed circuit board layouts, programmed integrated circuits, disks, CD-ROMs, software carriers and article texts published in our books and magazines (other than third-party advertisements) are copyright Elektor International Media b.v. and may not be reproduced or transmitted in any form or by any means, including photocopying, scanning or recording, in whole or in part without prior written permission from the Publisher. Such written permission must also be obtained before any part of this publication is stored in a retrieval

system of any nature. Patent protection may exist in respect of circuits, devices, components etc. described in this magazine. The Publisher does not accept responsibility for failing to identify such patent(s) or other protection. The submission of designs or articles implies permission to the Publisher to alter the text and design, and to use the contents in other Elektor International Media publications and activities. The Publisher cannot guarantee to return any material submitted to them.

Disclaimer

Prices and descriptions of publication-related items subject to change. Errors and omissions included.

© Elektor International Media b.v. 2009 Printed in the Netherlands

Active cell balancing chip for high-cell-count Li-Ion battery packs

Atmel's new battery management circuit ATA6870 is claimed to be the industry's first solution that features active cell balancing with capacitors or inductors for high-cell-count Li-Ion batteries supporting supply voltages up to several hundreds volts such as used in electrical/hybrid vehicles, e-bikes or uninterruptible power supplies.

The advantage of an active cell balancing is that it avoids the energy loss as occurs with passive balancing methods. The charge is transferred with a shuffle capacitor or inductor from one cell to another with nearly no losses, leading to higher efficiency and a longer battery life. In passive methods, cells of large battery stacks are balanced by discharging overcharged cells through a resistor.

In a typical battery pack, no cell is identical to another. The cells differ in the state-of-charge, self-discharge rate, cell impedance and capacity, and aging. After several charge and discharge cycles, this may result in increased voltage differences between the individual cells. This effect will impact the cells where several cells may no longer be properly charged, with the possibility of weak cells being over or undercharged. This will decrease the overall lifetime of a battery. Active balancing is a perfect method to constantly ensure that all the cells have the same state-of-charge.

The new IC monitors up to six battery cells and can be stacked up to 16 times. For the highest communication robustness between the stacked ICs, the IC features level shifters based on current sources. In addition, the ATA6870 includes an 8-bit checksum monitor that helps further increase data communication robustness.

The ATA6870 provides a dedicated AD converter for each battery cell to be monitored. This enables the device to simultaneously measure the voltage of all cells within one battery string for precise state-of-charge determination of Li-Ion battery cells.

Same as IC, the integrated power supply for the microcontroller can be stacked. Therefore, the current required to supply the microcontroller can be taken from the top cell and be fed back into the battery string's bottom cell. As a result, the microcontroller's current consumption will not cause any cell imbalance helping designers save expensive high-voltage devices. The on-board balancing capability can be used for various balancing techniques like passive balancing with a resistor or active balancing with a capacitor or an inductor.

www.atmel.com/dyn/products/product_card.asp?part_id=4641

(100266-1)



indicate relay/logic power. Inputs can be configured to handle a different range of input voltages. The new kit retails at \$49.99. In the UK, contact Milford Instruments or Spinvent. On the Parallax website, search for '27113'.

www.parallax.com
(100266-11)

Dual synchronous buck regulator for 'green' applications and battery-powered devices

Intersil's ISL8088 dual synchronous buck provides exceptionally high power conversion efficiency and low quiescent current in an ultra-small package. The ISL8088 is an 800 mA/channel dual step-down regulator with integrated power MOSFETs. The 2.7 V to 5.5 V input voltage range and 35 microamps quiescent current make the ISL8088 ideal for battery powered and other 'Green Power' applications. The selectable operation between forced PWM mode and automatic PWM/PFM mode maximizes battery life.

Featuring a switching frequency as high as 2.25 MHz, along with internal digital soft-start and internal compensation, the ISL8088 can reduce total component count, cost and overall size for a wide range of applications. External synchronization capa-



bility up to 4 MHz reduces beat frequencies in multiple IC systems. Independent Enable and PowerGood signals for both channels provide inherent sequencing capability in a multi-chip system. Protection features include peak current limiting, short circuit protection and thermal shutdown for reliable operation under adverse conditions.

The ISL8088 is designed for a wide range of products including digital cameras, personal media players, printers, copiers, storage drives, LCD-TVs, set-top boxes, graphics cards and automotive applications. In

Digital I/O board from Parallax

The Parallax Digital I/O Board Kit enables your microcontroller to interface to high voltage circuits allowing you to read up to 8 optically isolated inputs and control up to 8 isolated outputs. Inputs can be a voltage from 5-30VDC (AC compatible) and outputs can be either mechanical or solid state relays that can switch up to 12 A loads, such as cooling fans, solenoids, heating elements and more.

Simple parallel input/output control for ease of use or you can use the serial interface to minimize I/O pin usage. The logic circuits operate from 3.3 V to 5 V making



them compatible with most microcontrollers. The ICs in the kit are all socketed making replacement easy should it ever be necessary. 8 green and 8 red LEDs indicate the status of input and outputs. 2 yellow LEDs

addition, it can be used in portable medical instrumentation and industrial process control systems, providing the benefits of low-cost, flexible operation, low-power and ultra-small footprint.

The ISL8088 is available now in compact, space-saving 10-lead DFN packages.

www.intersil.com/products/deviceinfo.asp?pn=ISL8088
(100266-IV)

Low resistance current sense resistors

Providing design engineers with robust resistive devices capable of withstanding large surge currents, TT electronics IRC offers two series of low resistance metal alloy current sense chip resistors. Designated the ULR and LRMA Series, the resistors feature a metal strip construction capable of withstanding high temperatures and large currents.

The ULR and LRMA resistors are constructed with a low temperature coefficient resistive alloy that provides a large mass, or cross section, for carrying current when compared to film-based devices. This large mass is claimed to provide a robust structure, enabling the resistors to withstand large surge currents resulting from fault or other transient conditions that may exist in detection and protection circuits.

The ULR and LRMA Series resistors are ideal for use in current sense circuits in power electronics and automotive systems.

The RoHS compliant and halogen free ULR and LRMA Series resistors feature low TCRs (50, 75, and 100 ppm/°C) and inductance values. Resistance ranges from 0.5 mΩ to 100 mΩ, with power ratings from 1 W to 3 W, depending on device. The ULR Series resistors are offered in 1206, 2010 and 2512 chip sizes, while the LRMA Series devices are available in 0815, 1206 and 2512 chip packages.


www.irctt.com/products.aspx?frmCategory=22
(100226-V)



Lotus Evora 414E hybrid with sound contouring

Introduced at the 80th International Geneva Motor Show, the Lotus Evora 414E Hybrid has a plug-in series hybrid drive system and new technologies for enhanced driver involvement. The Lotus Evora 414E Hybrid, so-named because this latest environmentally-focused technology demonstrator from Lotus Engineering produces 414 PS (306 kW) of power, promises breathtaking performance from a highly efficient propulsion system. The concept showcases new developments in plug-in, range-extended electric propulsion, new electronic technologies to enhance driver involvement, the adaptability of the Lotus Versatile Vehicle Architecture (VVA) that underpins the Evora 414E Hybrid and a dramatic new roof system and interior concept from Lotus Design. Through all of these aspects it ultimately demonstrates the exceptional ability of Lotus Engineering to integrate and develop advanced technologies for exciting, efficient, high performance niche vehicles.

The range extended electric drive of the Evora 414E Hybrid consists of two electric motors driving each of the rear wheels independently via single speed geartrain, integrated into a common transmission housing, thus enabling torque vectoring for stability control of the vehicle. Electrical power is stored in a lithium polymer battery pack optimised for energy density, efficiency and high power demand, mounted in the centre of the vehicle for stability and safety. Additional range is provided by the Lotus Range

 

Extender engine, an optimised 1.2 litre, three-cylinder engine, designed specifically for series hybrid vehicles. The drivetrain is designed to combine astonishing performance with efficient, low emissions driving.

Driver involvement is enhanced by the incorporation of HALOsonic Internal and External Electronic Sound Synthesis technologies from Lotus and Harman International, which provide sound contouring within the cabin and improve pedestrian safety outside the vehicle. Integrated with the HALOsonic technology, the Evora 414E Hybrid also showcases a brand new technology from Lotus Engineering, a sports mode that simulates a 7 speed, paddle shift transmission that combines exceptional driver involvement for a hybrid sports car and optimised energy recuperation.

The Evora 414E Hybrid has a total hybrid range of over 300 miles (483 kilometres). The vehicle energy storage system is made up of the latest Lithium Polymer battery chemistry providing 17 kWh energy storage capacity. The battery pack is optimised for energy density, efficiency and high power demand, with over 100 kW discharge capability.

For everyday commuting journeys, up to 35 miles can be travelled using battery power. The battery can be charged overnight using a conventional domestic mains supply through a socket concealed by the rear number plate. This permits the vehicle to operate with zero tailpipe emissions. For longer journeys, exceeding the battery capacity, the highly efficient range extender engine is used as a generator to supply the motor with electrical power and top up the battery.

www.lotuscars.co.uk (100266-III)

Key British computer innovator to speak at Britain's first Vintage Computer Festival in June

One of the leading innovators of British microchip and computing technology will be a special guest at Britain's first Vintage Computer Festival to be held at The National Museum of Computing at Bletchley Park on 19-20 June 2010.

Sophie Wilson, co-designer of the BBC micro – the machine that introduced computing to a generation – and developer of the RISC/ARM processor – the chip at the heart of over 90% of mobile phones – will talk about her time and experiences at Acorn, when British brains led the world in the microcomputer revolution.

"We are thrilled to have Sophie Wilson as a key speaker at this first British Vintage Computing Festival," said Simon Hewitt, VCF Programme Co-ordinator at TNMOC. "Anyone whose first computing experience was on a BBC B, and anyone who uses a mobile phone will be familiar with her work. This is a rare opportunity to hear her speak."

Hewitt continued: "The list of exhibitors, speakers and special guests is growing rapidly and we have some excellent surprises in store. Tickets, costing only £10, will be going on sale in April and we will be releasing more news as speakers and exhibitions are confirmed."

Already other confirmed speakers include Christine Finn, print and broadcast journalist, and author of 'Artifacts: an archaeologist's year in Silicon Valley', ZX Spectrum expert and former games developer Chris Smith, and Karl Pantling-James from the Retro Computer Museum. TNMOC's own system restoration experts including Tony Sale, leader of the Colossus rebuild project, and Tony Frazer, project manager of the Harwell/WITCH computer restoration, will also be in the line-up.

One of the largest exhibitors will be Acorn World which will also be there in force with a display including Acorn micros through the ages, BBC games, a fully working Domesday system, new and retro software and even a Beeb repair centre where visitors can bring faulty BBC Micros in hope and expectation of a quick fix.

Retro-gamers will be in their element at the Retro Computer Museum with an eclectic display of hands-on systems, consoles and a special gaming competition. Other exhibitors include Amiga and Atari user groups, the SpectraNet project, the Sun-down Demoparty team, and the MK Amateur Radio Society.

Media sponsors of the event are ZDNet. Companies interested in sponsoring other elements of the event should contact Kevin Murrell: email kevin.murrell@tnmoc.org.



The National Museum of Computing at Bletchley Park, an independent charity, houses the largest collection of functional historic computers in Europe, including a rebuilt Colossus, the world's first electronic programmable computer.

The Museum complements the Bletchley Park Trust's story of code breaking up to the Colossus and allows visitors to follow the development of computing from the ultra-secret pioneering efforts of the 1940s through the mainframes of the 1960s and 1970s, and the rise of personal computing in the 1980s. New working exhibits are regularly unveiled and the public can already view a rebuilt and fully operational Colossus¹, the restoration of the Harwell / WITCH computer, and an ICL 2966, one of the work-horse mainframes computers of the 1980s, plus many of the earliest desktops of the 1980s and 1990s. The latest display is the much-talked-about Technology of the Internet gallery.

The Museum has recently launched a Foundation Sponsorship Programme for corporate. To date, funders of the Museum include BCS, PGP Corporation, IBM, NPL, HP Labs, InsightSoftware.com, Black Marble, and the School of Computer Science at the University of Hertfordshire.

The Museum is currently open on Thursdays and Saturdays from 1 pm, and on Bank Holidays in spring and summer. Groups may visit at other times by arrangement.

¹ see also "Colossus – the Rebuild" elsewhere in this edition.

General: www.tnmoc.org


Programme: www.tnmoc.org/vcf-gb.aspx
(100266-VII)

Ultra small synchronous DC/DC converter

Linear Technology Corporation introduces the LTC3731H, a PolyPhase[®] high efficiency (up to 95%) synchronous DC/DC controller with guaranteed operation for junction temperatures as high as 140°C offered in a 5mm x 5mm QFN package. This rugged DC/DC controller is expandable from 3- to 12-phase operation for 60 A to 240 A power

supply designs. The precision $\pm 5\%$ output phase current matching simplifies thermal management by evenly spreading the heat among the output stages. Applications include high current ASIC and FPGA supplies, power distribution buses, automotive engine control units and network servers. The LTC3731 can be configured as a buck or boost converter and operates with all N-channel MOSFETs from an input voltage ranging from 4.5 V to 28 V. The power-

ful onboard gate drivers minimize MOSFET switching losses and allow the use of multiple MOSFETs connected in parallel. A fixed operating frequency can be programmed for each phase from 250 kHz to 600 kHz or can be synchronized to an external clock with its phase-locked loop (PLL). The device's minimum on-time of just 110 ns makes the LTC3731 ideal for high step-down ratio applications. The reference voltage maintains $\pm 2\%$ accuracy over the full -40° to 140°C operat-

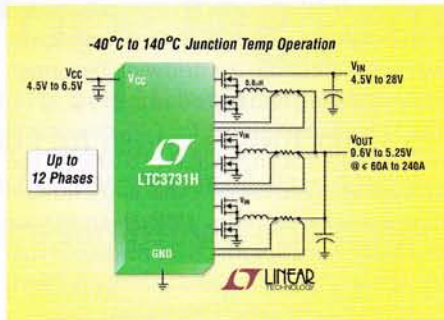

ing junction temperature range. The LTC3731H incorporates a power saving Stage Shedding™ technique to increase the efficiency and improve battery life at light loads by eliminating

the gate charging losses and switching losses of two of its output stages. Additional features include current mode control, programmable soft start, short-circuit and overload protection as well as adjustable soft-start.

The LTC3731 is now available in a 32-lead 5mm x 5mm QFN package as well as a 36-pin SSOP package.

www.linear.com (100266-VI)

CMOS linear VLDO regulator also for >1 amp, <1 volt

ON Semiconductor has extended its product portfolio with the introduction of five new CMOS linear voltage regulator families. The NCP69x families are optimized for use in low current consumption portable battery-powered and 'always on' applications such as cable modems, satellite receivers, digital-set-top boxes and electricity meters.



The NCP690, NCP691, and NCP692 are Very Low Dropout (VLDO) 1 A regulator devices available with an adjustable output voltage from 5.0 V down to 1.25 V or in fixed voltage versions. The devices offer a power supply rejection ratio (PSRR) of 62 dB, low quiescent


current (145 μ A typical) and low noise (50 μ Vrms) operation, as well as short circuit and thermal protection. They have greatly enhanced electro-static discharge (ESD) protection of 4 kV compared to standard CMOS LDOs and are designed to be utilized with low cost ceramic capacitors. The NCP691 includes an enable-low function, while the NCP692 has an enable-High function. The NCP693 1 A regulator operates with a supply current of only 65 μ A at no load, and a standby mode with a supply current less than 0.15 μ A, selected by a chip enable pin. Standard voltage versions are 0.8 V, 1.0 V, 1.2 V, 2.5 V and 3.3 V. This series is

THE HIGHEST PERFORMANCE PC OSCILLOSCOPE



PICOSCOPE 6000 SERIES

 350 MHz BANDWIDTH
5 GS/s SAMPLING
UP TO 1 GS MEMORY



4 Channel oscilloscope with spectrum analyzer

- Built-in arbitrary waveform generator
- CAN bus decoding
- Advanced triggering
- Mask limit testing
- Full math and measurement functions
- High Speed USB connection
- Easy-to-use software
- SDK for major third party applications

Five-year warranty

All included, from only £2995



pico
Technology

www.picotech.com/scope2002

complemented by the NCP694, which is an Ultra Low Dropout (ULDO) 1 A regulator for applications where there is a small differential between the input and output voltage. It offers -3 mV (typical) load regulation, and a 60 µA (typical) quiescent current. A ripple rejection of 70 dB (typical), along with a current limit and thermal protection makes this a very robust and versatile device. It is available in an adjustable version with a minimum output voltage of 1.0 V, and in fixed voltage options of 0.8 V, 1.0 V, 1.2 V, 2.5 V, and 3.3 V.

The NCP690, NCP691 and NCP692 are all offered in 6-lead, 3 mm x 3 mm DFN packages. The NCP693 comes in a 1.8 x 2.0 mm DFN package. The NCP694 is housed in 6-pin HSON and 5-pin SOT-89 packages.

<http://www.onsemi.com> (100266-VIII)

Cache-In-Trash-Out events and the Magellan eXplorist GC



Magellan, new eXplorist GC is said to be the first dedicated GPS device for geocaching that includes out-of-the-box paperless geocaching, pre-loaded with the most popular geocaches in the world, a brilliant colour screen, rich graphics and an easy to use interface all packed into a rugged and waterproof device, that connects seamlessly to www.geocaching.com. The Magellan eXplorist GC will ship in April.

Geocaching is a high-tech version of a 'treasure hunt', where adventure seekers use GPS technology to hide and find physical objects, solve location-based puzzles, and share experiences online. Geocaching is enjoyed by people of all ages and promotes

a strong sense of community and support for the environment.

The Magellan eXplorist GC GPS receiver is made exclusively for geocaching with an intuitive interface and the ability to sort and search thousands of geocaches. The device has multiple fun and familiar graphics, such as smiley faces for logs and merit-based awards to show off your geocaching expertise.

Powered by two AA batteries, the device can provide up to 18 straight hours of outdoor adventure along with a highly-sensitive SiRFstarIII GPS chipset that provides 3-meter accuracy. Geocachers can easily mark finds and quickly add field notes.

Additionally, the product comes pre-loaded with common outdoor GPS features such as waypoint creation, a worldwide basemap, active tracking and trip odometer.

The Magellan eXplorist GC GPS device will be introduced at an M.S.R.P. of \$199.99. The unit will ship with a USB cable and 2 lithium disposable AA batteries. With the purchase of a Magellan eXplorist GC GPS device customers will receive a 30-day free premium membership to geocaching.com.

www.magellangps.com/exploristgc
www.geocaching.com
www.magellangps.com
 (100266-X)

dsPIC33F 'GS series' Digital Signal Controllers for digital power supplies

Microchip announces the expansion of its 16-bit dsPIC® Digital Signal Controller (DSC) portfolio for digital power-conversion applications. Microchip's 16-bit dsPIC33F 'GS' Series DSCs provide on-chip peripherals specifically designed for high-performance, digital power supplies. On-chip digital power peripherals include high-speed pulsewidth modulators (PWMs), ADCs and analogue comparators. The newly expanded dsPIC33F 'GS' family supports applications such as induction cooking, uninterruptable power supplies, solar and pure sine-wave inverters, intelligent battery chargers, power factor correction, HID lighting, fluorescent lighting, LED lighting, and AC-DC and DC-DC power converters.



These new DSCs provide up to four times the memory, compared to Microchip's existing SMPS & Digital Power Conversion families. Additionally, these flexible DSCs can be configured for a variety of topologies, giving power-supply designers the complete freedom to optimise for specific product applications. The eight new DSCs offer up to 18 channels of PWMs with 1 ns resolution, enabling an unprecedented number of completely independent digital control loops.

The eight new dsPIC33F 'GS' series digital-power DSCs enable digital control loops with 12 to 18 high-speed, 1ns resolution PWMs and one or two 10-bit, on-chip ADCs, providing 2 to 4 million samples per second (MSPS) for low latency and high-resolution control. They range from 64 to 100 pins and 32 to 64 KB Flash memory. These DSCs feature interactive peripherals that both minimize the intervention of the processor and are able to handle the real-time needs of high-speed current-mode control.

The dsPIC33F "GS" series DSCs are supported by the MPLAB® Integrated Development Environment, MPLAB C Compiler for dsPIC DSCs, MPLAB SIM 30 Software Simulator, MPLAB ICD 3 In-Circuit Debugger and MPLAB REAL ICE™ In-Circuit Emulation System. For advanced development, Microchip's Explorer 16 Development Board (part # DM240001) can be used with the Buck/Boost Converter PICTail™ Plus Daughter Board (part # AC164133). A new dsPIC33F "GS" series Plug-in Module (part # MA330024) is available today for the Explorer 16, which enables development with this new DSC family; specifically, the 100-pin dsPIC33FJ64GS610.

www.microchip.com (100266-IX)

How to Get a Large Screen, Modern Digital Oscilloscope Without the Hefty Price Tag (and No, it's NOT a USB scope)

There are 10 reasons why you should request your free information pack to find out how you can replace your current oscilloscope and enjoy greater speed, efficiency, ease-of-use and convenience! And the good news is it's surprisingly affordable...

SOMETHING NEW has been introduced in oscilloscopes. And plenty of users from hobbyists to engineers have proven to themselves how it brings them important benefits.

To find out how you can benefit, simply email us at info@screen scopetraces.com for no obligation information on one of the newest developments in oscilloscopes – The Screenscope SSC-A531: a 50MHz real-time stand alone oscilloscope with a difference. It walks you through these advantages:

1. Affordable & Large Clear Display: Until now you simply couldn't have a stand alone oscilloscope with a large screen without breaking your bank. Screenscope solves this problem by letting you use a standard computer monitor for its display. You can pick up a very low cost LCD monitor these days so you can now look at a large screen rather than trying to decipher the signals from a tiny screen. (comparable to watching TV on a plasma vs a 9 inch screen)

2. Easy to get started: The main unit is a compact box with just three BNC sockets on the front panel, but no knobs. You'll find a video socket on the back panel which connects to that nice big monitor. This means all you need to do is plug a monitor, mouse and power directly into the unit and it's up and running in seconds. No computer required. No software to install.


3. Perfect for virtually any monitor: You can use Screenscope with any monitor. It doesn't matter if it's an old CRT, or a brand new LCD widescreen. This means: you can take it anywhere, there's always a monitor somewhere these days. Just plug it in, switch it on and you're ready to go.

4. Fun to use: All controls are graphical on the screen. They are well laid out and intuitively easy to use. You can click controls or grab and drag traces, markers, trig levels and position directly, and you've got a large playing field, all of which makes screenscope a joy to use.

5. Less hassle saves time: No more fiddling around with those plastic controls, knobs and menu buttons. Not to mention those controls that double as different functions when some options are selected.

6. It is NOT a USB oscilloscope: The problem with USB oscilloscopes is you need to install software directly onto the computer - and you can then only use it from your computer. Electronic workbenches can get messy, so you don't want a big computer sitting there just to get a big screen.

 7. Classy 50MHz real-time scope with lots of features: As well as the normal scope functions you get automeasures, and a nice set of manual measurement markers, all with easy to see readouts on screen. It has FFT and you can perform maths between channels and/or trace memories. At slower timebases, Screenscope operates like a chart recorder where you see samples being displayed immediately when they are taken. This mode can log continuous data to a USB memory stick.



8. Easy to save & store screen grabs and waveforms: Reference traces are great for instant comparison of waveforms and Screenscope has four of these and with its USB host port, so you can load or save them externally. With a click you can also do a screen grab to a BMP file to give you a WYSIWYG of your entire screen, which is great for inclusion into reports or just to save a view that is complete with all settings visible.

9. Long term investment: Even though it weighs just 0.95kg, it's rugged, reliable, compact and designed for a long useful life. Also, it's easy to store and always ready for use when required.

10. Save money:

Without all those plastic controls and by separating the screen from the instrument you get a better scope that costs less...saving you money.

Email:

info@screen scopetraces.com now for your free information pack. It will give you the information you need to get a system that's easier to operate... more efficient... faster..and less expensive too.

And visit our website www.screen scopetraces.com



ScreenScope



Clean Power from Hydrogen

Fuel cells in practice

By Thijs Beckers (Elektor Netherlands Editorial)

Sustainable energy is what everyone wants nowadays, but what's the best solution? The options include storing energy in large batteries, hydroelectric power plants with water reservoirs, and hydrogen, but there's still no clear answer to this question. Hydrogen appears to be a very promising candidate for mobile applications. Several car manufacturers already have prototype 'hydrogen cars' driving around, powered by fuel cells. Let's have a look at what you can actually do with fuel cells.

It appears that the worldwide demand for energy will continue to rise. Worldwide energy consumption in 2008 was 474 exajoules ($474 \times 10^{18} \text{ J}$)^[1], which amounts to a constant daily consumption of 15 terawatts ($15 \times 10^{12} \text{ W}$). Worldwide energy consumption is expected to increase by 54% between 1995 and 2015. This results for the most part from rising consumption in Asian countries, with an anticipated increase of 129%. Of course, this is mainly due to the fact that the per capita energy consumption in countries such as India and China is among the lowest in the world and that these countries expect to achieve very strong economic growth, which goes hand in hand with a strong increase in energy demand. Per capita energy consumption in the Western countries is already very high. For instance, the USA accounts for approximately 29% of worldwide energy consumption, despite the fact that its population is only about 5% of the total world population. The industrial and transportation sectors consume enormous amounts of fuel. The majority of this (around 80 to 90%) consists of oil and gas. The rest comes from nuclear energy and sustainable energy generated from natural sources, such as wind, water and sunlight.

Fossil fuels

At the start of the Industrial Revolution in the late eighteenth century, the main sources of energy were oil and coal. We need energy in our daily lives to run our central heating systems, refrigerators, television sets, PCs and cars. All of these systems and devices need energy, which is largely provided by fossil fuels. Our central heating systems run on natural gas, our household appliances run on electricity generated by power plants that operate primarily coal or natural gas, and our cars run on petrol. Our society is almost entirely oriented toward energy from fossil fuels.

However, these energy sources will not last forever. At some point the oil wells will be pumped dry, the gas deposits will be exhausted,

and all the coal will have been mined – and what will we do then? In response to this pressing question, innumerable projects and studies for the development or exploitation of new energy sources have been launched, including cold nuclear fusion, solar energy, biofuels, wind energy, and what have you.

Alternatives


In principle, the amount of energy from the sun that 'bombards' the earth is more than adequate to meet all of our energy needs for the next hundred years. However, we have not yet developed a perfect method for converting this energy into a usable form. Although solar cells are becoming more and more efficient, it still takes a considerable amount of energy to produce them, and most of this energy still comes from fossil fuels.

There's also the question of how to store this sustainable energy. One way to do this in a 'green' manner is to store it in the form of hydrogen. There are presently a good number of tricky issues here, but considerable effort is currently being put into developing suitable storage options and a practical infrastructure for hydrogen as a fuel.

H₂

Hydrogen is a naturally occurring substance that takes the form of hydrogen molecules (H_2) consisting of two hydrogen atoms. It is a gas at room temperature and normal pressure, with a density of 0.084 grams per litre.

 
This makes it approximately 14 times lighter than air. Hydrogen is the lightest and smallest of all elements. As a result, it can easily pass through porous materials and even through metals such as platinum, which is a characteristic that requires special attention in storage systems. Hydrogen forms an explosive mixture with air and gaseous chlorine, but pure hydrogen is very stable.




Electrolysis

Hydrogen can be produced in several ways. The most common method is to use an electric current to decompose water into hydrogen and oxygen. This process is called electrolysis, and it works as follows. Two electrodes are placed in an electrolyte: first an anode, which is connected to the positive terminal of an external voltage source, and second a cathode, which is connected to the negative terminal of the voltage source. These electrodes are made from a metal that is not altered by the electrolytic process, but instead acts as a catalyst for the process. Platinum is often used for this purpose. The surface characteristics of the electrode have a strong effect on the amount of hydrogen that is released.

A DC current is used for electrolysis. There are several options for the voltage source, such as a battery or a solar cell. An electrolyte, such as sodium sulphate (Na_2SO_4), must first be added to the water to provide ions so that a current can flow, since pure water is a very poor conductor of electricity. Oxygen (O_2) forms at the anode (which is connected to the positive voltage), while hydrogen forms at the cathode. Due to the supply of electrons to the cathode (negative voltage), the following reaction occurs at the cathode:

 

 The hydrogen formed at the cathode rises through the liquid and can be captured. The hydroxyl ions (OH^-) formed at the cathode are used in the reaction that occurs at the anode. The following reaction occurs there due to the shortage of electrons (positive voltage):




The oxygen formed at the anode also rises through the liquid and can be captured.

The reaction at the anode requires twice as many OH^- ions as are formed at the cathode. This means that two hydrogen atoms are released for every oxygen atom that is released. In other words, the process produces twice as much hydrogen as oxygen.


Fuel cells

The process of electrolysis is reversed in a fuel cell. The reverse reaction yields an electric current, along with pure water as a by-product. Here again an electrolyte is necessary to allow the reaction to occur. In fuel cells, the electrolyte takes the form of a special membrane. The fuel cells we examined for this article (described below) are all of the type called 'PEM fuel cells', where 'PEM' stands for 'proton exchange membrane'. The advantage of this type of fuel cell is that it can operate at room temperature. There are now many other types of fuel cells that operate under other conditions, including some that operate at much higher temperatures^[2].

The membrane of a PEM fuel cell is made from Nafion. This is a polymer with a molecular structure so dense that only hydrogen ions can pass through the material; oxygen ions are held back. On each side of the membrane, there is an electrode consisting of a carbon mat with a coating of vapour-deposited platinum. The anode side receives a continuous stream of hydrogen, while the cathode side receives a continuous stream of oxygen. The platinum catalyst splits the arriving hydrogen molecules into hydrogen ions according to the following formula:

 

 The electrons are absorbed immediately by the electrode. They pass through the connected external load and arrive at the cathode. The positively charged hydrogen ions diffuse through the membrane to the cathode, where they react with the released oxygen ions to produce water according to the following formula:



The electrons necessary for this reaction are supplied by the cathode. In this way, the membrane allows hydrogen and oxygen to combine and form water in a clever manner without any visible combustion or explosion.

The voltage generated by this type of fuel cell is usually between 0.6 and 0.9 V, which is too low for most applications. For this reason, it is common practice to connect several fuel cells in series in order to obtain the required voltage. The required current capacity is achieved by ensuring that each cell has sufficient surface area.

Try it yourself

It's now relatively easy to perform your own experiments with fuel cells, since a number of kits are available commercially. They are primarily intended to be used for educational purposes in order to explain the concept of sustainable energy. We put several kits through their paces and examined what they could do (caution: most of the fuel cells concerned are intended to be used with the accompanying kit, but not for other experiments. Otherwise the warranty is rendered void).

Fischertechnik

We received the *Hydro Cell Kit* from Fischertechnik [3]. This kit consists of an integrated unit containing a PEM fuel cell, water tank and gas reservoir; a solar panel; and some fastening hardware. This kit is actually an accessory for the *Eco Tech* kit from Fischertechnik, in



which ten different constructions operate from solar power. With the combination of the two kits, the fuel cell can be used for electrolysis in order to buffer the solar energy by storing it in the form of hydrogen gas. When the solar panel does not receive enough light, the fuel cell can be used to generate electricity from the hydrogen gas. This combination illustrates precisely what is expected from a sustainable solution to our virtually insatiable demand for energy.

Heliocentris

We received the *Dr FuelCell Science Kit* from Heliocentris [4], a company that specialises in fuel cells. This very extensive kit comes with four books full of theory, explanations and instructions for experiments and measurements, which are clearly oriented toward educa-



tional use. The kit has a separate unit for electrolysis and storing the hydrogen and oxygen, a solar panel to supply power for electrolysis, a PEM fuel cell for DIY assembly, and a measuring unit with several different loads. The kit also includes a methanol fuel cell, which we ignored during our tests. This kit includes everything you need for experimenting with sustainable energy solutions.

Eitech

Eitech [5] sent us their *Construction Set C30*. This kit includes instructions for building three different structures powered by a hefty PEM fuel cell. A special feature of this kit is that it comes with a small canister holding 20 litres of hydrogen gas, which can also be refilled



(but only by the manufacturer, unfortunately). This kit is not suitable for generating your own hydrogen. There is a booklet with a concise explanation of how it all works, and from the specifications alone



you can see that this fuel cell is more powerful than those in the other kits. All in all, this is an excellent choice for DIY experiments.

Kosmos


Kosmos^[6] sent us their *Brennstoffzelle Classic* ('Classic Fuel Cell'). This kit also includes a reversible PEM fuel cell, which means that it can be used to generate hydrogen or to generate electricity. Here the fuel cell is used to power a small car using hydrogen as the fuel.



not as user-friendly or convenient as the others, but it works. The fuel cell has the lowest power output of the lot, which is obviously due to the relatively small surface area of the membrane.

Horizon

 
We also included the *Hydrocar* from Horizon Fuel Cell Technologies in our test. This kit is similar to the Kosmos kit in terms of content, but the documentation is not nearly as extensive.



Everything necessary for performing experiments, such as hoses, cables, a gas canister, a multimeter and a solar panel, are included in the kit. The extensive assembly instructions also include a detailed description of the operating principle of the fuel cell (and the solar cell). Highly educational.

Franzis

The *Lernpaket Experimente mit der Brennstoffzelle* ('Learning Kit for Fuel Cell Experiments') from Franzis^[7] contains the components necessary for making your own fuel cell. With a bit of patience, you can assemble the small cell in 15 minutes. However, you have to make the fuel (hydrogen) yourself. Along with several other experiments, this is described in the accompanying user guide. This approach is

 

A few measurements

Naturally, the first thing we wanted to know about the fuel cells is how they actually performed in practice. For this reason, we made several measurements intended to clearly show the power and energy characteristics of the fuel cells at a glance. We connected the fuel cells to several different loads in order to obtain an idea of how much power they could supply.

Determining the efficiency is more difficult because it is necessary to know exactly how much energy in total is used to generate the hydrogen. However, some of the kits specify that both reservoirs (oxygen and hydrogen) must be completely full in order to obtain maximum power. This results in the generation of more hydrogen than can be held in the hydrogen reservoir, so it bubbles out of the reservoir and is lost. Consequently, the energy that is used can never be fully recovered, which makes the efficiency appear worse than it actually is.

Figures 1a and 1b show the output power of the kits versus time (during which the amount of fuel in the reservoir gradually decreases). Due to the low voltage generated by the cells, the loads have low resistance: $4\ \Omega$ for the first measurement and $1.2\ \Omega$ for the second measurement. With such low load resistances, cable resistance and contact resistance also become important factors. For instance, the measurements with a $1.2\text{-}\Omega$ load were actually made with a $1\text{-}\Omega$ load resistor; the remaining $0.2\ \Omega$ came from the cable and contact resistances.

With most of the cells, the output power remained fairly constant until it dropped abruptly when the fuel was used up. The cells from

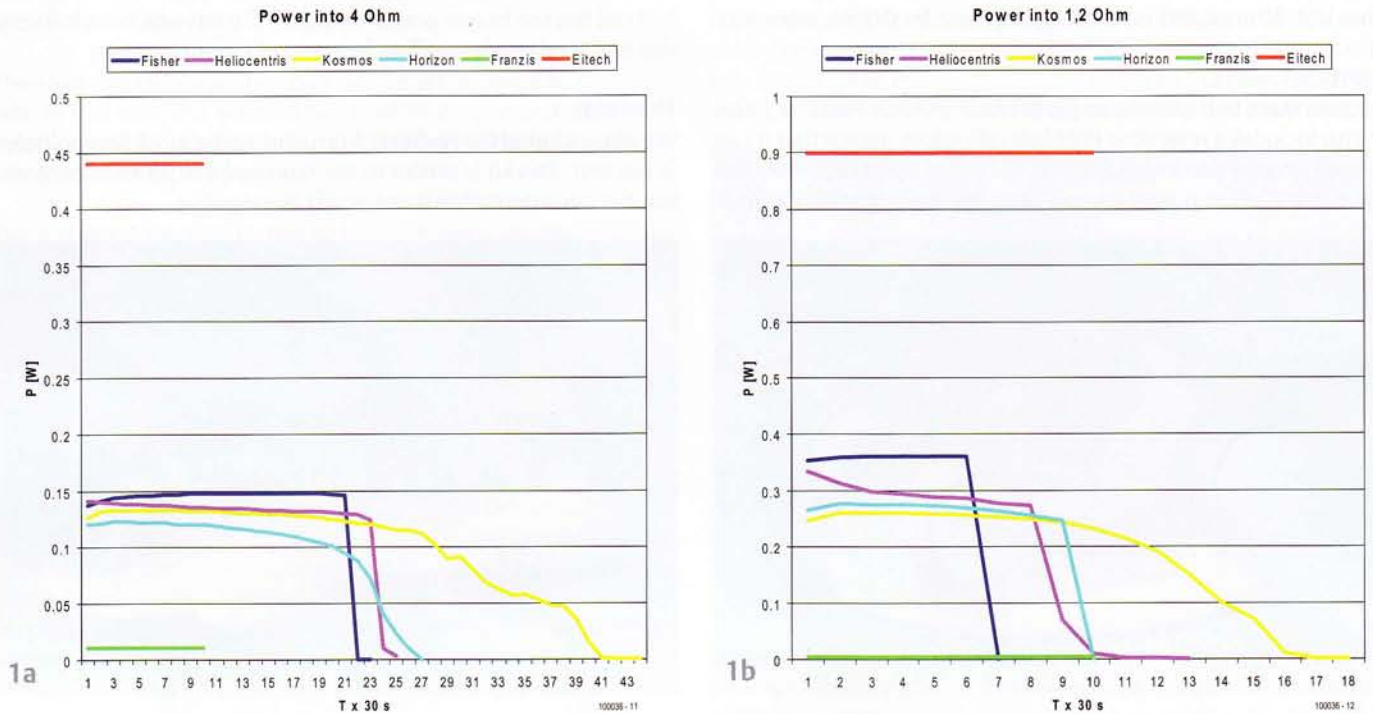


Figure 1a/1b. The output power of the fuel cells drops abruptly when the fuel supply is used up.

Eitech and Franzis were fuelled with hydrogen from the gas canister of the Eitech kit and therefore delivered a constant power level. Only the fuel cell in the Kosmos kit showed a slowly decreasing power level. This is probably related to the construction of the water reservoir and gas storage unit. The relative high power of the Eitech fuel cell is also remarkable — nearly three times as large as most of the other cells. With its two membranes, this fuel cell also has a considerably larger surface area. By contrast, the power output of the self-assembly fuel cell from Francis was rather low. Of course, this is partly due to the small surface area of the membrane, but it could also be partly due to the cell design intended for DIY assembly, which results in higher contact resistance and reduces the overall performance.

Figures 2a and 2b show the amount of energy used by the fuel cells for electrolysis (indicated as 'U') and the amount of energy generated by the fuel cells (indicated as 'G') with different loads (4 Ω and 1.2 Ω), combined in a single chart for each resistance value. Of course, this does not include the Eitech and Franzis fuel cells because they are not designed to generate hydrogen. Only the output energy is shown for these two fuel cells on the charts. The energy input was stopped when the reservoirs were full. Depending on the individual kit, the total energy input for fuel gen-

eration was 250 to 300 joules. The total energy output with a 4-ohm load ranged from 75 joules with the Horizon fuel cell to 123 joules with the Kosmos fuel cell, corresponding to an efficiency range of 27 to 40% (roughly speaking). This may not appear especially high, but it is actually not bad if you compare it with the efficiency of an internal combustion engine in a car (around 25%). The results are slightly worse with a 1.2-ohm load: 63 joules from the Heliocentris fuel cell and 90 joules from the Kosmos fuel cell, with corresponding efficiencies of 24 and 30%. These are still very acceptable figures.

Applications

The small fuel cells we tested generate enough power to meet the needs of 'small' applications with power consumption up to 0.5 W. The Eitech fuel cell can be used to power a respectable pocket torch (1 watt) if you use a suitable voltage converter. The gas canister is small enough to be portable and contains a reasonable amount of hydrogen. Unfortunately, a practical and commercially feasible solution to the problem of hydrogen storage is not yet available. However, Toshiba has already developed a methanol fuel cell [8] that is commercially available, so a solution for hydrogen should not be too far away. Research on hydrogen storage in special alloys that allow it to be stored at room temperature with approximately the same density as in liquid form is presently underway at full speed.

 
 


Figure 2a/2b. The total energy generated by the fuel cells is less than the amount of energy used to produce the hydrogen, but with a yield of around 30% for the overall process the efficiency of these simple cells is five percentage points better than the efficiency of a typical internal combustion engine.

Ready for the future?

Our test results show that you can achieve respectable efficiency with a relatively simple fuel cell. With the PEM fuel cells in our test, the process of converting energy (such as solar energy) into stored energy in the form of hydrogen and then generating power from the stored hydrogen yielded an overall efficiency of around 30%. This already a good deal better than the efficiency of typical internal combustion engines, even ignoring the energy necessary to produce the fossil fuel used by the internal combustion engine (the solar energy accumulated by plants millions of years ago, pumping the oil, refining the crude oil, transport and so on).

The lifetime of early fuel cells was not especially satisfactory. Nowadays this is not such a problem, although it varies considerably depending on the type of fuel cell. The lifetime of PEM fuel cells is now long enough for use in cars (including hybrid cars).

A more significant problem is hydrogen distribution (or hydrogen availability). Filling stations for conventional fuels are widely distributed, but stations where you can fill up with hydrogen and locations where hydrogen tanks can be delivered are few and far between. To give the 'society with water as a fuel' described by Jules Verne in his novel *The Secret Island* (1874) a chance to become reality, our infrastructure must be adapted to using hydrogen as a fuel. That's a tall order, but it doesn't seem impossible. The first hydrogen station for

home use is already on the market [9].

The further course of these developments is something that only the future can tell. Nevertheless, the fact is that our fossil fuel resources are nearly exhausted and we must look for new options.

(100036-1)

We wish to express our thanks to Eitech, Fischertechnik, Franzis, Heliocentris and Kosmos for providing the experiment kits.


Internet Links

- [1] http://en.wikipedia.org/wiki/World_energy_resources_and_consumption
- [2] http://en.wikipedia.org/wiki/Fuel_cell
- [3] www.fischertechnik.com
- [4] www.heliocentris.com
- [5] www.eitech.de
- [6] www.kosmos.de
- [7] www.franzis.de
- [8] www.toshiba.co.jp/about/press/2009_10/pr2201.htm
- [9] www.horizonfuelcell.com/store/hydrofill.htm

dsPIC Control Board

for industrial applications

 By Yannick Louvrier & Yves Birbaum (Switzerland)



The control board shown in this article has been designed for incorporation into typical industrial electronics applications like controlling motors or adjustment of static up- or down-converters.

Technical specifications:

- universal dsPIC30 microcontroller board
- isolated CAN bus
- serial port via USB
- 14 analogue inputs
- 8 PWM outputs
- I²C bus

The objectives were to obtain a board with a large number of pulswidth modulation (PWM) generators, which enables us to control several motors and static converters at the same time. The cost of the control board needed to be as low as possible too. In addition, it must be possible to construct the board using a soldering iron, without requiring use of a reflow oven. On this basis, it was logical for us to turn to the range of

dedicated motor control microcontrollers offered by Microchip. Out of the range of devices on offer, our attention was drawn by the dsPIC30F series. This series of 16-bit hybrid microcontroller-DSP devices is capable of performing up to 30 MIPS and has a 40-bit register, thus allowing overflow detection along with the possibility of performing 16×16 multiplications and 32×16 and 16×16 divisions, making it very interesting in adjustment applications. To take advantage of maximum flexibility in this series of devices, we picked the dsPIC30F6010A microcontroller [2]. This microcontroller has 68 input/output ports and allows up to eight PWM signals to be generated. This characteristic meets our specifications perfectly, especially since it has a 144 KB flash

memory, allowing relatively complex applications to be controlled.

In addition to all these qualities, the dsPIC30F6010A also has a 16-bit A/D converter, eight output compare outputs, eight input capture inputs, two UARTs, two SPI ports, two I²C ports, two CAN controllers, and five counters.

There is plenty of free documentation about this device, with numerous examples and applications.

Another advantage is the MPLAB programming environment, which can be downloaded free from the Microchip website [3] — but is unfortunately only available for Windows. However, even though this programming environment can be a bit laborious when applications are relatively com-

plex, it does have the merit of offering lots of features, like the possibility of simulating code and controlling the time needed to execute each instruction. Although these tools aren't really essential for expert users, they do make learning to program PIC microcontrollers more fun.

The block diagram of the control board is shown in **Figure 1**. A 50-pin connector gives access to the microcontroller's 43 configurable pins, including the PWM modules, output compare, and input capture. This connector also carries the connections for the incremental detectors, allowing direct access to one of the dsPIC's counters. This port can also be used for expansion purposes.

This board designed for controlling systems of greater or lesser complexity needs to allow us to measure the dimensions to be adjusted. So 14 analogue values between 0 and 5 V can be read via a 20-pin connector. In addition to the analogue and digital ports, this board has a lot of communication peripherals. It has a CAN field bus, a UART connection via USB, and an I²C connection. The board uses SMD components so as to keep it as small as possible — 80 × 100 mm on a double-sided PCB. However, the board is not difficult to build, with the help of a good soldering iron.

The board in detail

After a generic explanation of the functions implemented on this control board, we must explain in more detail the hardware used and the board's various features. It goes without saying that readers should refer back to the dsPIC30F6010A documentation available from the Microchip website. The circuit diagram of the board is shown in **Figure 2**.

The big connector K5 makes it possible to utilise lots of the microcontroller's functions. It offers access to:

- port A, which, in addition to the digital input/output functions, also lets us define the analogue voltage levels for the A/D converter. It offers two external interrupt inputs (INT).
- pins RC13 and RC14 of port C, which

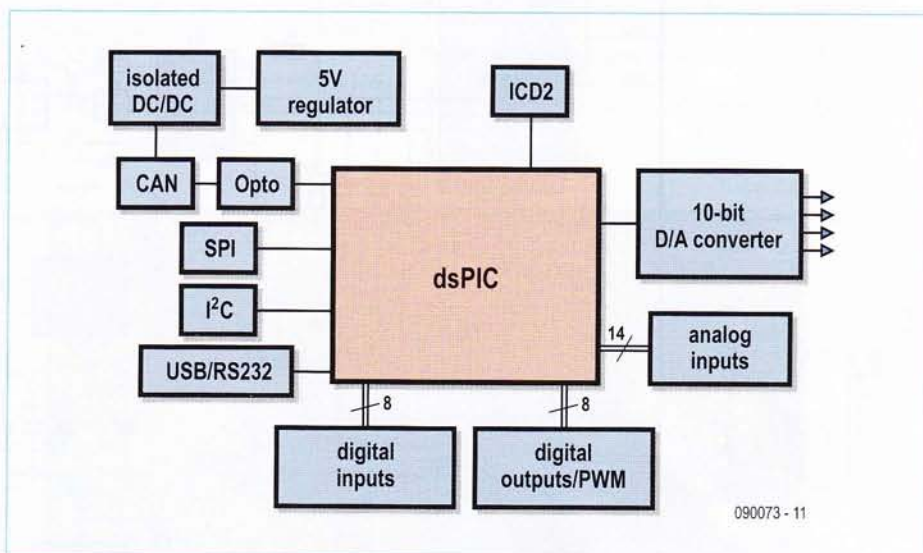


Figure 1. Block diagram of the dsPIC control board.

make it possible to configure the second channel of the ICD (In-Circuit Debugger), as well as to implement an external timebase for a real-time clock.

- port D, which has 8 input capture modules and 8 output compare modules. This register also allows programming of seven interrupts and access to the ICD's third channel.
- port E, which lets us generate 8 PWM signals. This port also offers two external interrupt inputs.
- ports RF4–RF8, which bring together the SPI1, UART2, and ICD channel 4 functions, as well as two possibilities for external interrupts.
- ports RG0, RG1, RG6–RG8 which make it possible to use the CAN2 controller, the SPI2 link, and three sources of external interrupts.
- the MCLR pin, which allows the microcontroller to be reset.

Connector K4 is assigned to measuring analogue signals, and so is connected to microcontroller pins RB2–RB15, allowing 14 analogue signals to be measured.

The 4-channel, 10-bit digital/analogue converter used is an AD5336 (IC4). The digital value to be converted is transferred via ports RE0–RE9. For the conversion to take place, the function has to be enabled by the

microcontroller by way of pin RF4. The four analogue outputs are addressed by way of microcontroller pins RC1 and RC3.

The microcontroller's built-in CAN1 controller is used for communicating with the microcontroller via the CAN field bus. In order to avoid the control board's being destroyed by possible voltage surges on the line, it was decided to equip the interface with an isolated 5 V PSU (IC2) and two optoisolators in addition to the transceiver IC9. Two pull-up resistors are all it takes to implement the I²C bus. The resistor value will change, depending on the bus speed you want to achieve. The resistor value fitted to the board is 4.7 k Ω , allowing a theoretical transmission speed of 100 kbit/s.

In order to improve the control board's connectivity and so make it easier to use, an FT232RL chip (IC5) from FTDI has been used to allow it to be connected via a computer USB port. Together with the driver [4], this IC has the effect of adding a virtual serial port when connected to the computer. This function thus allows the user to communicate via the USB port as if it was an RS-232 link.

The board is powered from a DC supply of 5–55 V, thereby affording an opportunity to recycle an old mobile telephone charger. In our case, we used a Nokia charger that provides a 5 V supply at a current of 890 mA.

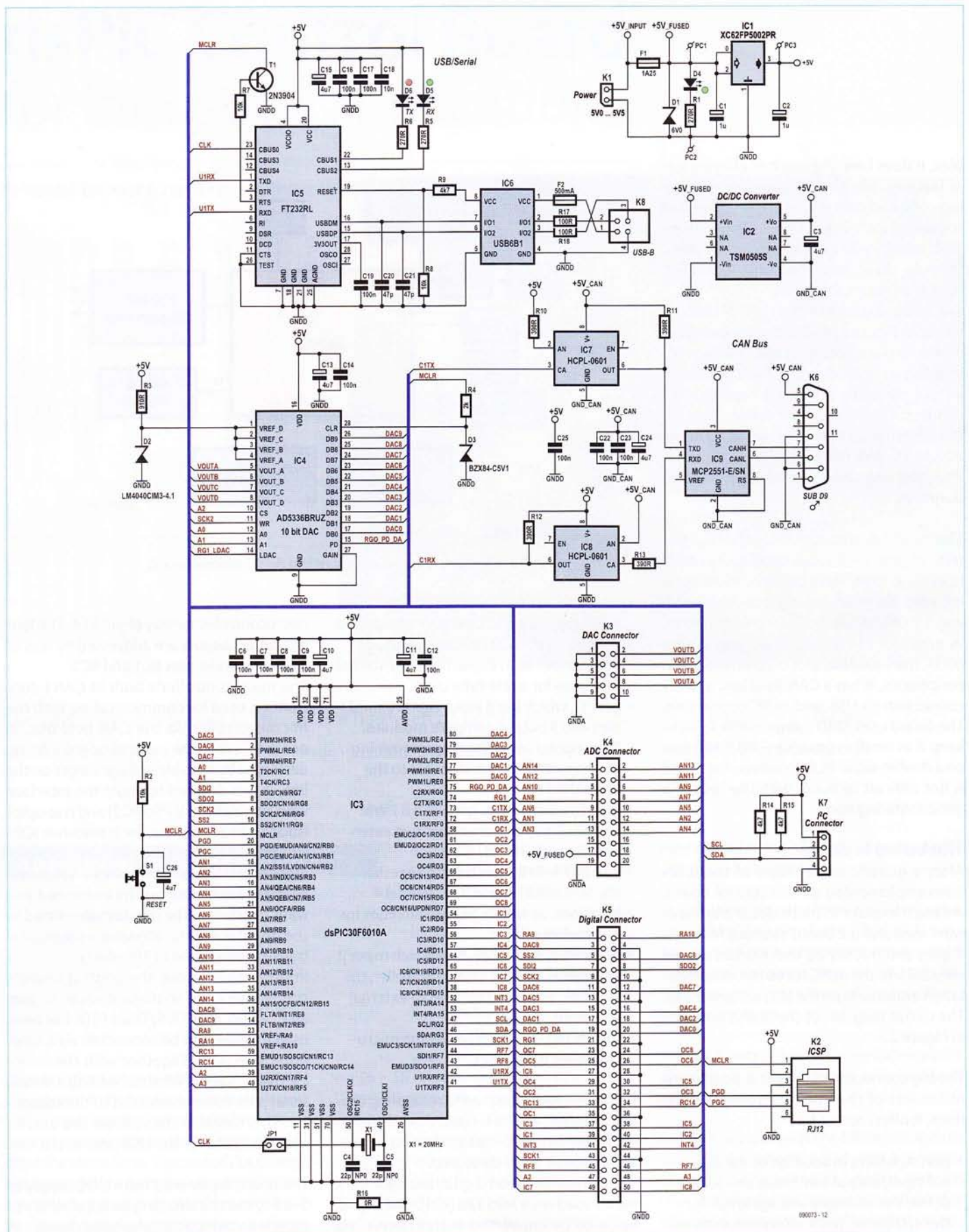


Figure 2. Circuit diagram of the dsPIC microcontroller-based board.

COMPONENT LIST

Resistors

(1%, 250 mW, SMD 0805 unless indicated otherwise)

R1, R5, R6 = 270Ω
 R2, R7, R8 = 10kΩ
 R3 = 910Ω
 R4 = 2.0kΩ
 R9, R14, R15 = 4.7kΩ
 R10–R13 = 390Ω
 R16 = 0Ω, 1%, 125mW, SMD 0805
 R17, R18 = 100Ω

Capacitors

C1, C2 = 1μF 16V, tantalum, case 'A'
 C3, C10, C11, C13, C15, C24, C26 = 4.7μF 16V, tantalum, case 'A'
 C4, C5 = 22pF, NP0, SMD 0805
 C6, C7, C8, C9, C12, C14, C16–19, C22, C23, C25 = 100nF, X7R, SMD 0805
 C20, C21 = 47pF, NP0, SMD 0805

Semiconductors


IC1 = XC62FP5002PR, SOT-89-3 (Torex)
 IC2 = TSM 0505S DC/DC converter 5V / 1W (Traco)
 IC3 = dsPIC30F6010A-30I/PF (Microchip)
 IC4 = AD5336BRUJZ (Analog Devices)
 IC5 = FT232RL (FTDI)
 IC6 = USB6B1 (STMicroelectronics)
 IC7, IC8 = HCPL-0601 (Avago)
 IC9 = MCP2551-E/SN CAN (Microchip)
 D1 = Diode SMCJ6V0A (Fairchild Semiconductor)
 D2 = LM4040CIM3-4.1/NOPB (National Semiconductor)
 D3 = zener diode BZX84-C5V1 5.1V / 250mW, SOT23 (NXP)

D4, D5 = LED, green, SMD 1206 (e.g. Farnell # 1226371)
 D6 = LED, red, SMD 1206 (e.g. Farnell # 1318261)
 T1 = 2N3904BU (Fairchild Semiconductor)

Miscellaneous

K1 = 2-way boxheader, angled pins, lead pitch 3.5mm, Weidmuller type SL 3.5/2/90G with mating 2-way connector, Weidmuller type BL 3.5/2
 K2 = RJ12 socket (e.g. Farnell # 3938359)
 K3 = 10-pin (2x5) pinheader
 K4 = 20-pin (2x10) boxheader, 3M type N2520-6002-RB

K5 = 50-pin (2x25) boxheader, 3M type N2550-6002-RB
 K6 = 9-way sub-D plug (male) (e.g. Farnell # 1097063)
 K7 = 4-pin pinheader, lead pitch 2.54mm
 K8 = USB-B connector (e.g. Farnell # 1308876)
 F1 = fuse, 1.25A 125V, fast, SMD, e.g. Farnell # 1596473)
 F2 = fuse, 500mA, fast, SMD, (e.g. Farnell # 9922156)
 S1 = pushbutton, SPNO (e.g. Farnell # 1555982)
 X1 = 20.000MHz quartz crystal, HC-49US
 PCB # 090073-1, see [1]

 

Programming and start-up

The board is programmed using the MPLAB development software [3]. For the 16-bit range of microcontrollers, programming is done in ASM30 assembler directly available in MPLAB. For programming in C, the C30 compiler too can be downloaded from the Microchip website.

First-time start-up requires a compatible programmer that will let you load the bootloader into the microcontroller. In our case, programming is performed using the ICD2 programmer [5] and the MPLAB programming environment. However, you can also use another compatible programmer. If everything goes according to plan, the programmer is only required once, then the bootloader will be used for 'flashing' the microcontroller via the USB port. The Tiny PIC bootloader used has to be downloaded from the Claudiu Chiculita website [6]. A few modifications to the source file are needed to adapt it to the

dsPIC30F6010A microcontroller. The modified file has been renamed `tinybld_ds6010.s` and is available in the download from [1]. It's important to note that the microcontroller's configuration parameters in this file have to be adapted to suit your requirements. The bootloader is located at the end of the microcontroller's memory space, so take care not to overwrite it with an application that's too big.

The first time you use the bootloader, the driver needed for using IC5's virtual COM port must be installed on the computer. Once the drivers are installed, you still need to configure IC5 correctly, using the MPROG3.0 program provided by FTDI. Run the program and open the EEPROM-FTDI.ept file (available in the download from [1]). The parameters needed for IC5 to work correctly will be displayed (Figure 3). Program the chip with these parameters. Once the bootloader has been programmed into the microcontroller and the FTDI IC has

been configured, the MPLAB software and programmer are no longer needed. From this point on, the microcontroller is programmed using the `tinybldwin` software (Figure 4 and [6]).

To put the microcontroller into bootloader mode, the reset mode has to be activated. To do this, an NPN bipolar transistor controlled by IC5's RTS signal forces the microcontroller's MCLR to zero. For this to work, the RTS command needs to be enabled in the `tinybldwin` program options. The transfer speed must be set to 19200 baud/s and the virtual 'comX' port must be selected. Pressing the 'Check PIC' button allows you to check the communication between the microcontroller and the computer.

To program the microcontroller, load the HEX file required and click on "Write Flash". When the microcontroller is rebooted after the reset, the bootloader is loaded. It waits 500 ms to see if there is a request

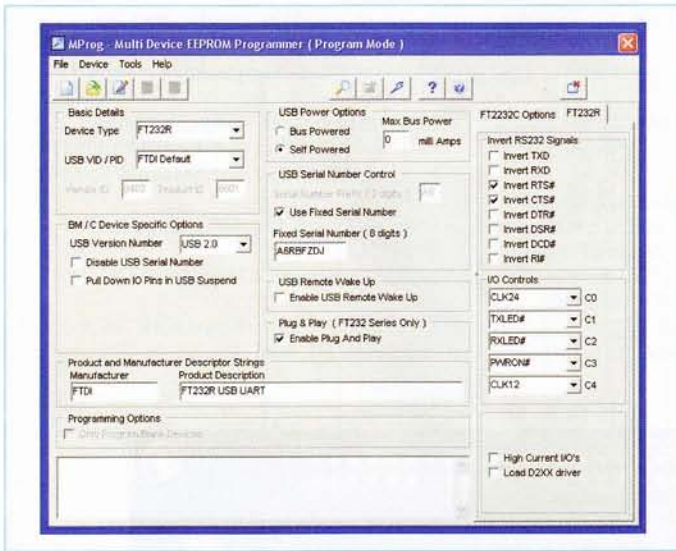


Figure 3. How to configure MPROG for programming IC5.

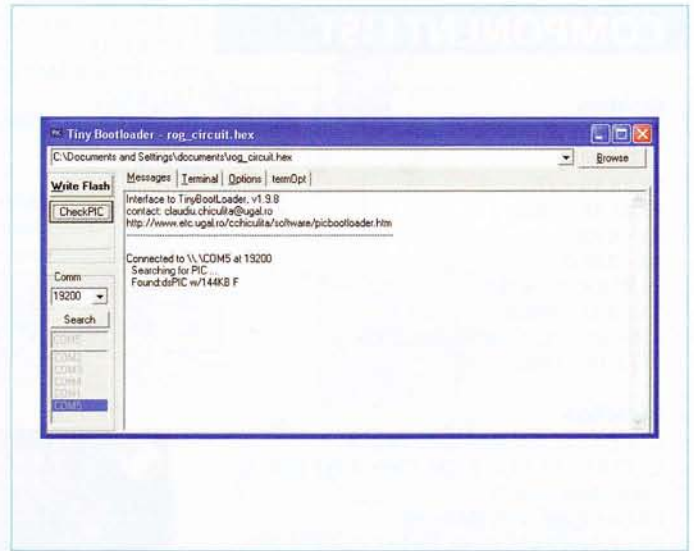


Figure 4. This program lets you load an application into a PIC microcontroller that's been pre-programmed with the Tiny PIC Bootloader program.

from the asynchronous RS-232 serial link. If yes, it goes into programming mode. If not, it runs the application stored in the microcontroller.


Once the board has been commissioned, you can make use of the possibilities it offers, and particularly the use of the DSP library provided by Microchip. This board dedicated to adjusting and controlling applications

needs to be able to carry out a few simple mathematical operations rapidly. To use these functions, the libdsp-coff.a library must be added to the project's other libraries (Library Files). This file can be found (probably, depending on your installation) in C:\Program Files\Microchip\MPLAB C30\lib\libdsp-coff.a

(090073-1)

Internet links

 - [1] www.elektor.com/090073
- [2] ww1.microchip.com/downloads/en/DeviceDoc/70150D.pdf
- [3] www.microchip.com/mplab
- [4] www.ftdichip.com/FTDrivers.htm
- [5] www.microchip.com/icd2
- [6] www.etc.ugal.ro/cchiculita/software/picbootloader.htm



Fixed-point fractional numbers

For its library, and for the fast calculation application based on 16-bit registers, Microchip uses fixed-point fractionals coded using "1.15" notation, which makes it possible to represent numbers between -1 and $1 - 2^{-15}$ (0.999969482). Thus -1 is represented by 0xFFFF and $1 - 2^{-15}$ by 0x7FFF; hence the value 0x0001 corresponds to $2^{-15} = 1/32768$. The advantage of this coding is that it avoids overflow problems during multiplications, since the result of multiplying any numbers between -1 and $1 - 2^{-15}$ also lies between -1 and $1 - 2^{-15}$ (except for -1×-1). Two decimal fractions can be multiplied rapidly by applying the mpy function from the DSP library.

THE ORIGINAL SINCE 1994
PCB-POOL[®]
 Beta LAYOUT
 Specialising in Prototype PCBs

NEW! Free Laser Stencil with all Prototype PCB orders

NEW! 1 WD prototype service

NEW! Chemical Tin Finish (no extra cost)

Free Phone
 UK 0800 389 8560

@ Simply send your layout files and order ONLINE
 PCB-POOL.COM • sales@pcb-pool.com

Beta LAYOUT

Don't just test it...
 ...Analyse it!
 Special Offer prices for limited period or while stocks last!

PEAK
 electronic design ltd

The Famous Atlas LCR, Model LCR40

Best Seller!

Passive component analyser. Identify inductors, capacitors and resistors. Auto frequency selection. Removable probes. Optional SMD Tweezers, Crocs and Clutch Grabbers. Supplied with battery and universal hook probes.

Auto-Ranges:
 1uH - 10H
 1pF - 10,000uF
 1 Ohm - 2M

Nominal Accuracy:
 Resistance 1%
 Inductance 1.5%
 Capacitance 1.5%

Test frequencies:
 1kHz, 15kHz and 200kHz

Dimensions:
 103x70x20mm



Atlas SCR - Model SCR100

Connect Triacs or Thyristors any way round. Auto part-pinout identification. Check gate 100uA to 100mA. Measures gate voltage drop. Regulated load test conditions.



Atlas ESR - Model ESR60

Capacitance and ESR! Capacitance 1uF to 22,000uF. ESR 0.01ohms to 20 ohms. Gold plated croc clips.



Atlas ESR PLUS - ESR70

Audible alerts! ESR 0.01 ohms to 40 ohms. Capacitance measurement. Our best ESR ever!



Atlas DCA - Model DCA55

The famous Peak Atlas! Now with premium probes. Connect any way round to identify semiconductor type, pinout and lots of parameters.



Atlas IT - Model UTP05

Identify network cabling type. Identify many fault types. Tests sockets and cables. Complete with all this:



Atlas Star Pack (LCR/DCA)


Money Saving Packs Save £25! Includes the Atlas LCR, Atlas DCA and a premium padded carry case, with extra spare battery.



Peak Electronic Design Ltd, West Road House, West Road, Buxton, Derbyshire, SK17 6HF. UK: Please add £2.75 p&p per order. Prices include UK VAT. tel. 01298 70012 www.peakelec.co.uk sales@peakelec.co.uk See website for overseas prices.

Digital I/O Board Kit

Make a high voltage interface for your microcontroller with the Parallax Digital I/O Board Kit (#27113). Read up to 8 optically isolated 5-30V inputs and control up to 8 isolated outputs. Outputs can be mechanical or solid state relays that can switch up to 12A loads, such as cooling fans solenoids, heating elements, and more. Soldering assembly required. Relays sold separately: Omron 12A SPDT Relay (#400-00052); Sharp 8A Solid State Relay (#400-00053).

 

PARALLAX INC

www.parallax.com

"ParallaxInc" on Twitter, Facebook, and YouTube



Milford Instruments
 www.milinst.com

Spinvent
 www.spinvent.co.uk

Solar Thermal Energy Regulator

maximum power point tracking explored



By Yves Birbaum (Switzerland)

The aim of this project is to carry out regulation for thermal solar power installations. The unit shown here is useful for regulating installations comprising several sets of solar collectors with different orientations or configurations with several hot-water storage tanks, requiring several valves and pumps to be controlled.

The solar energy regulator board has been designed so it can be used as a universal control board

Commercial solar power regulators can handle one or two solar heat exchange arrays commonly known as collectors (**Figure 1**), but are not suitable for special configurations that comprise, for example, three collector arrays and two hot-water stor-

age tanks (immersion tanks) for the heating, including circulation between the two tanks. The regulation system given here is intended for solar power installations that are complex because of the number of solar collector arrays they have, or installa-


tions that have been added on to an existing system designed to provide heating and/or domestic hot water for the home. It allows energy conscious home owners to maximize use of the stored solar energy and avoids an immersion heater or heating burner turning

Technical specifications

- universal control board
- 10 outputs
230 VAC @ 1.2 A / 120 VAC @ 2.5 A
- 10 binary input/outputs (5 V),
- standard LCD display interface
- 5 pushbuttons
- digital potentiometer

on while there is still enough energy in the installation.

 Regulators for solar power installations are based on the temperature difference between the roof mounted heat exchange units and the storage tank in order to determine if the circulating pump should be turned on or not. The thermal energy transferred



from the collectors to the storage tank depends on the solar energy received, convection and radiation losses throughout the installation, and the energy transfer on the heat exchanger within the storage tank.

The proposed regulation system employs a technique known as MPPT (Maximum Power Point Tracking). This enables the solar installation being controlled to always operate at the point where maximum power is being transferred to the storage tank, which is achieved by adjusting the flow rate so that the temperature at the storage tank corresponds to the best possible heat transfer through the heat exchanger. To be able to control the system in this way, we need to know the temperature of the storage tank and the solar collectors, the temperature difference of the heat transfer fluid between storage tank inlet and outlet, and the flow rate.

The energy transferred to the storage tank is the product of the fluid flow rate in kg/s, the specific heat capacity, and the heat transfer fluid temperature difference between the hot inlet and the cold outlet. The regulator will control the operating point by looking for the maximum instantaneous

power supplied to the storage tank. In the current installation, the flow rate is adjusted by diverting part of the flow directly back from the pump outlet to its inlet, using a 3-way valve.

Hardware

The heart of this regulator is a board based around a dsPIC microcontroller from Microchip, described elsewhere in this issue. A simple microcontroller would have done just as well, as this application doesn't use any calculations requiring a DSP, but as the dsPIC is very reasonably priced and the dsPIC board developed is the basic platform for several projects, we decided to use it for

controlling our solar power regulator. The solar regulation board has been designed so it can be used as a universal control board, with ten binary inputs/outputs (0 or 5 V), a display with four lines of 20 characters, five switches for choosing functions or menus, and ten AC power outputs. The circuit diagram of the board is shown in Figure 2.

The AC power outputs (230 VAC or 120 VAC) are fitted with Panasonic AQH3213 solid-state relays which incorporate an opto-isolator and a triac. These devices allow you to switch AC powered loads with a current of 1.2 A from a dsPIC board output via a 7406

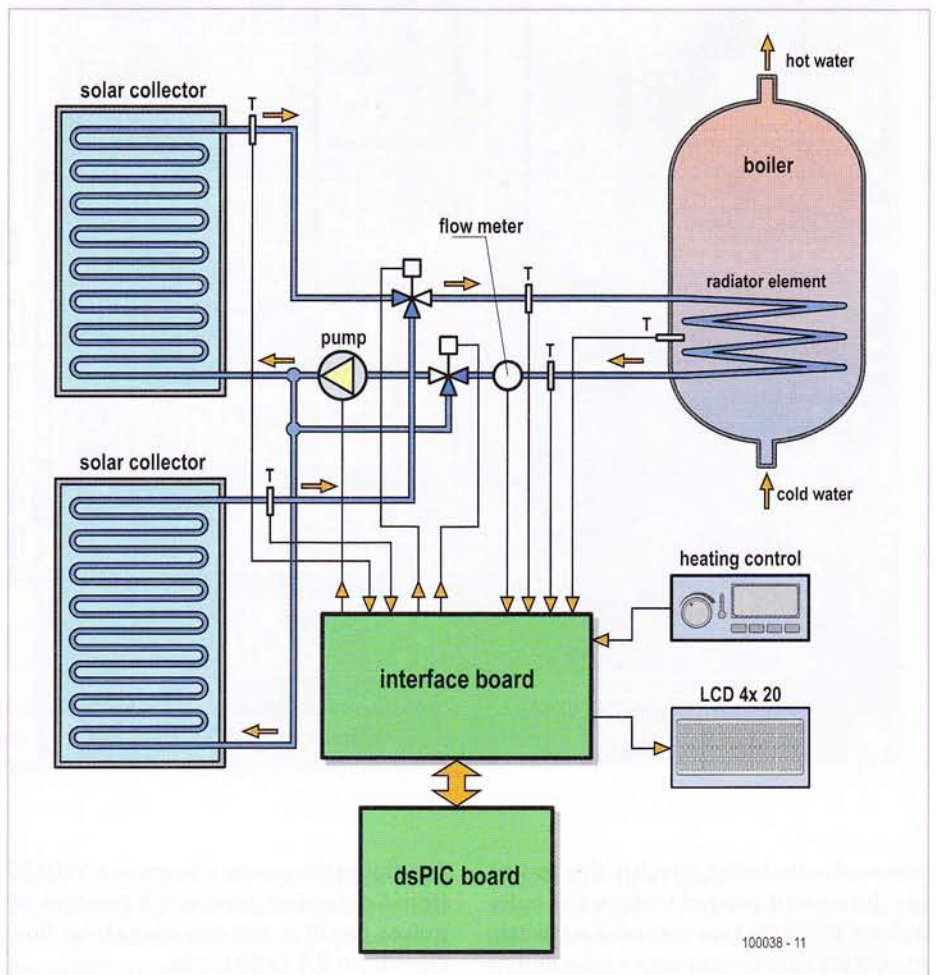


Figure 1. A thermal solar energy system using two solar collector arrays. The solar regulator has been designed for managing even more complex systems.

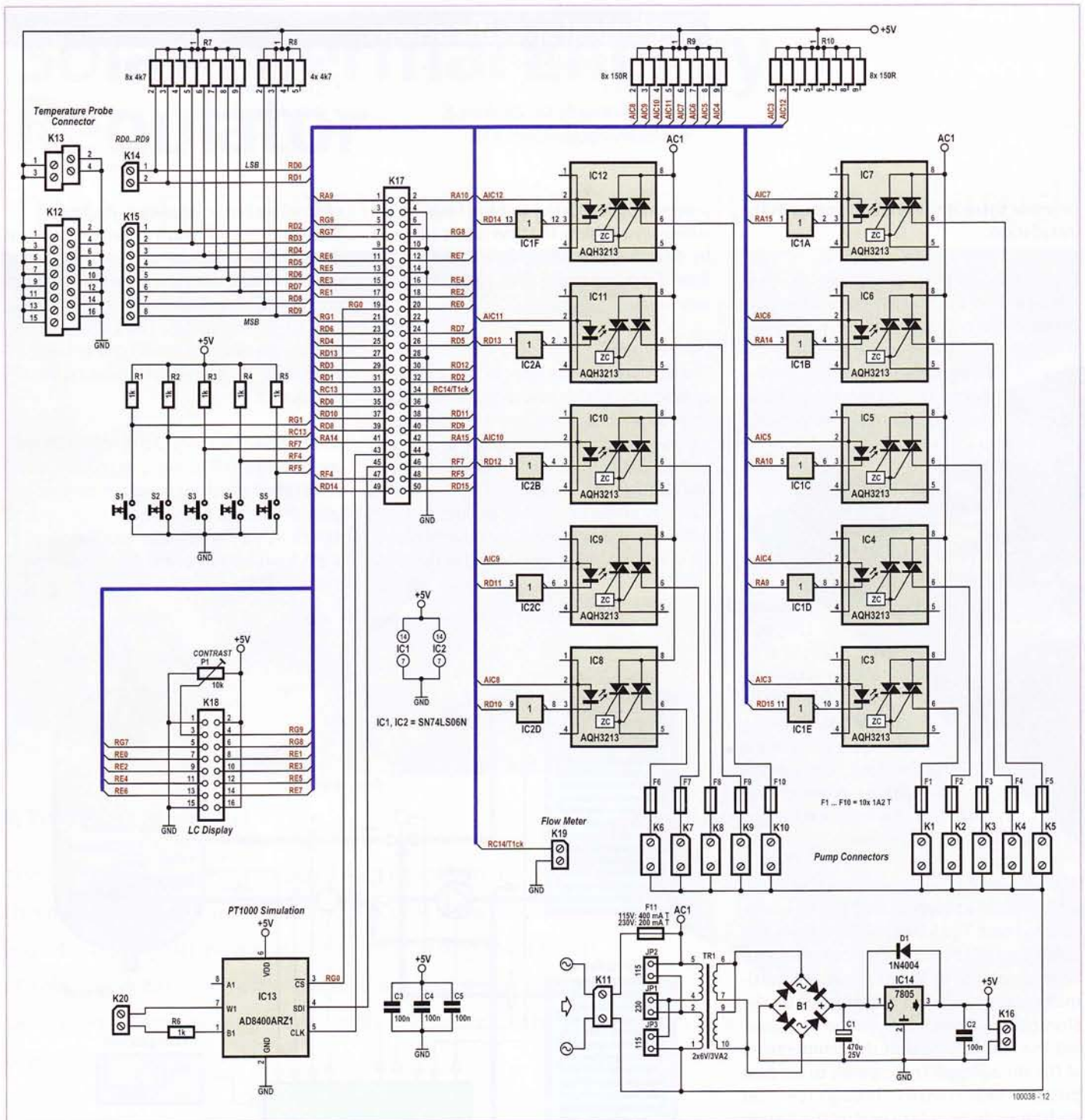


Figure 2. This project aims to be a board that can be used in many applications that require digital I/Os and controls for devices working off the AC grid. Regulating a solar energy system is only one possible application for this board.

open-collector buffer, which is able to supply the current needed to drive the optoisolator. Using the type chosen, load switching occurs at zero-crossings of the AC line voltage. All the AC power outputs are protected by 1.2 A fuses (use 2.5 A for 120 VAC grid and loads).

The flow-rate sensor chosen is a 150175 from Conrad Electronics^[2]; it provides 80 pulses per litre and can operate at flow rates from 0.5 to 50 l/min. The pulse input from the flow meter is fed to the microcontroller's RC14/T1CK digital input, allowing you to couple this

input directly to an internal counter. The temperature sensors used are type DS1821 from Maxim/Dallas. These are 1-Wire interface sensors which provide an 8-bit digital value for temperatures between -55 and +125 °C. Solid-state temperature sensors may seem an unsuitable choice for a

COMPONENT LIST

Resistors

- R1-R5 = 1k Ω 1% 250mW SMD0805
 R6 = 1k Ω 5% 250mW
 R8 = 4.7k Ω 4-element SIL resistor array
 R7 = 4.7k Ω 8-element SIL resistor array
 R9, R10 = 150 Ω 8-element SIL resistor array

Capacitors


- C1 = 470 μ F 25V, radial electrolytic, 10mm diam.
 C2-C5 = 100nF, 5mm lead pitch

Semiconductors

- IC1, IC2 = SN74LS06N (Texas Instruments or equivalent)
 IC3-IC12 = AQH3213 solid state relay (Panasonic)
 IC13 = AD8400ARZ1 (Analog Devices)
 IC14 = 7805
 B1 = 1KAB10EPBF bridge rectifier (Vishay), 1.2A, 100Vpiv
 D1 = 1N4004

Miscellaneous

- F11 = fuse, 200mA 250V (400mA, 120V), slow blow, 5x20mm
 F1-F10 = fuse, 1.2A 250V, (2.5 A, 120 V) slow blow, 5x20mm
 K1-K11 = PCB terminal block, lead pitch 7.5mm
 K12 = 4-way 2-level receptacle type MKKDSN 1,5/8-5,08 (Phoenix Contact)
 K13 = 2-way 2-level receptacle type MKKDSN 1,5/2-5,08 (Phoenix Contact)
 K14, K16, K19, K20 = 2-way PCB terminal block, lead pitch 5.08mm (e.g. Farnell # 3041440)
 K15 = 8-way PCB terminal, lead pitch 5.08mm (0.2 in.) (e.g. Farnell # 3041517)
 K17 = 50-way connector type N2550-6002-RB (3M)
 LCD1 = alphanumeric, 4 lines of 20 characters (Elektor # 050176-73)
 P1 = 10k Ω preset, horizontal
 S1-S5 = pushbutton, SPNO
 TR1 = 2x6V 3.2VA power transformer (Farnell # 1131487)
 11 holders for 5x20mm size fuses (e.g. Farnell # 146123)
 10 IC sockets type DIL-8
 2 IC sockets type DIL-14
 PCB # 100038-1, see [1]

 

solar power installation, as the sensor temperature may exceed 200 °C in the event of heat transfer fluid circulation stopping while the sun is shining. However, this type of sensor is suitable for installations where the circulating pump runs continuously when the sun is out. To avoid excessive domestic hot

water temperature, we need to provide a discharge radiator or to use the excess solar energy to heat a swimming pool, which is the solution usually used.

The advantage of this temperature sensor is the digital interface, which can be con-

nected directly to any microcontroller port. The 1-Wire protocol defines minimum and maximum times for holding the microcontroller output at 0 for the sensor to interpret it as a 1 or a 0. The microcontroller is in charge of the communication, it sends a temperature read request, and the sensor

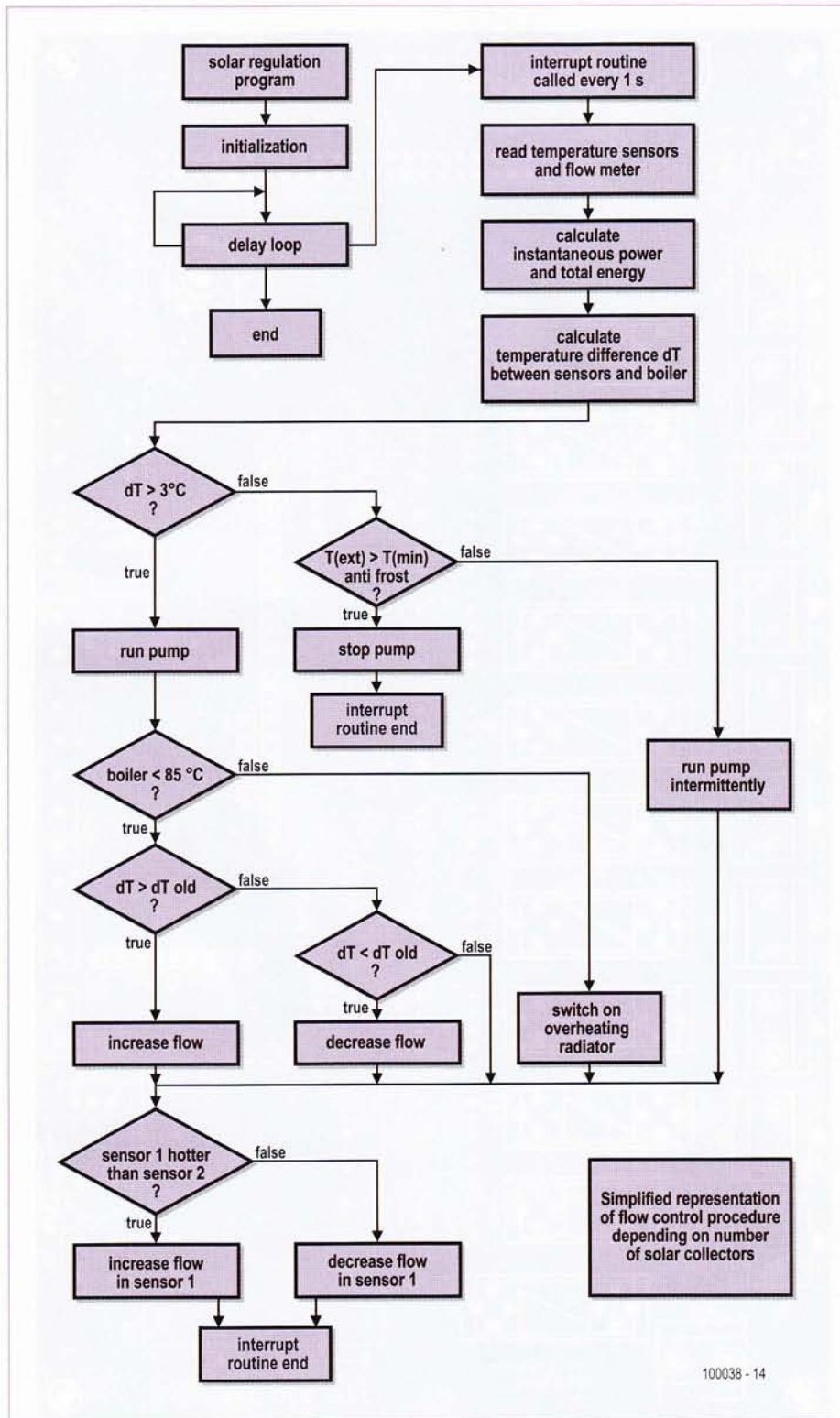


Figure 3. The flow diagram for the software that drives the solar energy regulator board.

An AD8400 digital potentiometer from Analog Devices (IC13) lets you simulate a PT1000 temperature probe. This output is used where the boiler regulator allows control of a simple solar installation but the complexity of the installation requires a separate regulator for the solar system. The AD8400 connected to the heating system regulator lets you simulate the temperature of the solar collectors and in this way avoid the boiler's starting up when the sun is out.

The dsPIC board used for controlling this solar regulator includes a 20-pin connector wired to the microcontroller's analogue inputs. These inputs can be used if you want to use standard analogue sensors, via a circuit for shaping the output signals from the chosen temperature probes.

The regulator measures the temperature of three solar collector arrays, the temperature of the top and bottom of the storage tank (immersion tank), the incoming hot heat transfer fluid from the collectors and the returning cold heat transfer fluid at the storage tank outlet, and the outdoor temperature. The outdoor temperature measurement enables you to avoid the heat transfer fluid's freezing in conditions of extreme cold below usual winter temperatures and there is no sun. When the temperature drops below the rated temperature for the water/antifreeze mixture, the circulating pump cycles (10 s on, 30 s off) in order to avoid the heat transfer fluid's solidifying in the piping, which would impair proper operation of the installation once the sun returns.

The 4-line, 20-character display lets you read the various temperatures of the sensors, storage tank, and heat transfer fluid, and the outdoor temperature. The flow-rate and the instantaneous energy being supplied by the solar collectors are displayed, and the total power supplied to the storage tank by the solar collectors is recorded.

The five switches let you select the operating mode for the regulator. The modes implemented are:

- automatic mode;
- discharge radiator / swimming pool mode, which operates the valve to bring

sends the serial values at the microcontroller's own pace. It takes the line briefly to 0 for each request for the next bit. 1-Wire communication lets you wire up the temperature probes easily using 3-core cable: 0 V, +5 V, and data. The sensor pull-ups are

the 4.7 kΩ resistors recommended by the manufacturer. However, for communication distances over 15 m, it may prove necessary to reduce the value of this resistor to around 2 kΩ so as to ensure a signal waveform that can be interpreted correctly.

the corresponding section of the installation into operation;

- circulator mode, which runs the circulating pump for 30 s to check it is working properly.

In automatic mode, the circuit goes into swimming pool mode when the immersion tank temperature exceeds 85 °C, and the heat transfer fluid circuit is diverted via a 3-way valve to a heat-exchanger connected to the swimming pool water circuit. The swimming-pool mode enables you to heat the swimming pool even when the immersion tank temperature is below 85 °C.

Power for the system (the dsPIC board, the opto-isolators for the AC power outputs, the display, and the temperature probes) is provided by a conventional supply comprising

other is in shadow. A third probe checks the temperature of the solar collector on the west roof.

The program sequence (**Figure 3**) starts by initializing the microcontroller and variables. The main program is implemented in the interrupt generated by timer2. The initialization function has been designed in such a way as to be able to configure the microcontroller easily depending on the desired application. It lets you configure the I/Os, counters, interrupts, and analogue/digital conversions. The interrupt comprising the system adjustment section is called once a second: sun exposure parameters vary quite slowly, so more rapid control is unnecessary. Temperature measurements and the main checks are carried out once per second, flow-rate adjustment and valve setting is performed once every thirty seconds. This delay allows the system to reach

Increasing the flow-rate will reduce the solar collector temperature; maintaining a temperature of 5–10 °C between the collectors and the storage tank should keep system losses close to the minimum possible. This quest for the optimum is especially worthwhile during hazy sunshine. If the flow-rate is too high, the temperature in the solar collector drops below the value that causes the pump to run, and the heated fluid is cooled in the pipes. It is necessary to find the flow-rate that lets you maintain an adequate temperature with causing frequent stopping of the pump. In strong sunshine, the flow-rate will tend towards maximum.

The program includes detection of the maximum temperature of the immersion tank. If this temperature is reached, the valve that diverts the heat transfer fluid to the swimming pool heat-exchanger or overheating

The flow-rate is adjusted to achieve maximum energy transfer to the storage tank

a small 6 volts power transformer, followed by a diode bridge, a smoothing capacitor and a linear regulator.

Software

The program developed is intended for a solar energy installation with three solar collector arrays: two located on the flat roof of a south-facing carport, the third on the west side of the main house roof.

At sunrise, the solar collectors on the carport are illuminated, but from early afternoon, they are gradually obscured by the shadow of the house. In Summer, they get the sun again partly in late afternoon, as the sun reappears in the north-west behind the house. From mid-morning till sundown, the west-facing collectors on the roof are also illuminated. The collectors on the flat roof are connected in series, but two temperature probes have been positioned according to the exposure of the collectors to the sun, in order to avoid one part of the collector overheating while the

a new state of equilibrium after a change in the flow-rate or valve settings, before being able to carry out a fresh correction if necessary.

The interrupt program goes and reads the temperature values from each sensor, it reads the flow-rate, then it calculates the instantaneous power being supplied to the installation and integrates the total energy supplied to the installation.

The temperature differences between the solar collector arrays and the storage tank are calculated. If the temperature of an array is 3 °C higher than the storage tank, the circulating pump is started.

The 3-way valve routing the heat transfer fluid between the solar collectors on the flat roof and the west roof is controlled according to the temperature differences between the various collectors. The system always seeks to balance the temperatures of the solar collectors.

The flow-rate is adjusted to achieve maximum energy transfer to the storage tank.

radiator is operated. In this event, the heat transfer fluid no longer passes through the immersion tank.

This valve is also operated when there is no sun, thereby avoiding thermo-siphon circulation between the immersion tank and the solar collectors during the night.

The minimum temperature of the heat transfer fluid is compared with the outdoor temperature. If this drops below this value, the circulating pump is run intermittently, preventing freezing of the heat transfer fluid the circuit passes via the swimming pool heat exchanger or overheating radiator, and so does not have any cooling effect on the immersion tank.

(100038-1)

Internet Links

[1] www.elektor.com/100038

[2] www.conrad.fr/debitmetre_3_4_laiton_p_18925_18937_127855_127856

Worry-free Drilling

A practical test of pipe and wire locators



By Harry Baggen (Elektor Netherlands Editorial)

All too often when you're drilling holes in a wall, you hit an electrical conduit or (perhaps even worse) a water line, with the usual unpleasant consequences. A pipe and wire locator (called stud locator in the USA) can come in very handy for locating all sorts of things inside walls before you start drilling, including electrical wiring, pipes, and even joists or studs. We tested thirteen different models in the Elektor lab to see what they can (and can't) do and how deep they can find studs, joists, pipes and wiring inside walls.

Everyone who does handyman jobs on a regular basis, either at home or in someone else's home, sooner or later encounters the problem that holes need to be drilled in a location where there's a good chance of encountering a water pipe or an electrical conduit. If you guess wrong, you suddenly get a blast of water in your face or the earth leakage circuit breaker trips. You can avoid these problems by first using a pipe and wire locator to check whether there are any metal pipes or live conductors in the portion of the wall where you want to drill. Locators of this sort are also very

handy for determining where wooden studs are located inside a wall, such as a wall sheathed with gypsum boards.

A variety of manufacturers now have pipe and wire locators in their product lines, including major brands in the power tools world such as Black & Decker and Bosch as well as companies that specialise in this area, such as Zircon. Prices range from around 20 pounds to 100 pounds, depending on the model and the features. There are also professional pipe and wire locators priced at 1000 pounds or more, but they fall outside the scope of this survey.



Naturally, the main question when you're contemplating the purchase of a pipe and wire locator is: does it really work? What can this sort of instrument find, and how deep can it detect something in the wall? We were also curious about this. For this test, we asked several companies to provide us with various models of pipe and wire locators so we could see how well they perform in practice.

Operation

Most of these devices have several electrodes arranged close together for detecting pipes or studs inside walls (see the example in **Figure 1**). These electrodes act as the plates of a capacitor forming part of an oscillator circuit. The coupling between the plates, and thus the capacitance of the capacitor, depends on the type of material near the plates. If the dielectric constant of the material in

 


Figure 1. The sensor surfaces on the back of the PCB are readily visible in this opened-up pipe and wire locator. There is also a coil at the top for detecting metal pipes.

front of the capacitor plates changes, for example because there is a wooden stud inside the wall, the capacitance changes and with it the frequency or the signal level. This is indicated visually by a set of LEDs or an LCD screen. Some scanners use sinusoidal signals, while others emit short pulse, and there are a few instruments that utilise pulse trains. From measurements on several scanners, it appears that the measuring frequency is usually well above 10 kHz.

An additional sensor element in the form of a coil, possibly with a core, is often used for detecting metal pipes. This coil also forms part of an oscillator circuit. The coil responds to changes in the magnetic field, which in turn affect the oscillator frequency or the signal level. Most detectors operate with a measuring frequency of 100 kHz or more.

In addition, many instruments have an AC field indicator to indicate the presence of an AC (mains) voltage. The 50-Hz or 60-Hz 'hum' emitted by power wiring can easily be picked up by a small surface antenna in the unit, which is usually already present in the form of the measuring electrodes. This signal can be amplified and used to drive an LED or a signal level meter.

Practical use

Almost all pipe and wire locators are used the same way in practice. First you hold the unit against the wall in a location where you are sure that there is nothing inside the wall, and then you switch it on. The pipe and wire locator performs a self-calibration procedure, which takes a few seconds. After this you slowly slide the unit over the wall, preferably without lifting it away from the wall, in the area where you want to drill or saw. When it approaches a stud or a pipe, an LED strip or a multi-segment display indicates that the composition of the wall has changed. Using this technique, it's perfectly possible to detect wooden joists and studs or iron and copper pipes up to a depth of several centimetres. PVC pipes are not detected unless they are relatively large, and ordinary PVC electrical conduits are almost never



Figure 2. The Bosch and Skil pipe and wire locators use a coil facing the wall for accurate detection of metal objects. The PCB tracks around the coil form the plates of a capacitive sensor for wood detection.

detected unless they have wiring inside, preferably live. Some of the pipe and wire locators we tested require you to hold a button pressed while you're scanning the wall. Although this prolongs the life of the batteries, it is sometimes not especially convenient, especially when you need to scan an area at the bottom of a wall or in a location that is not easily accessible. A more convenient solution is an instrument that switches on when you press a button and then switches off automatically a while later. This aspect is mentioned in the description of each scanner.

Another feature that can sometimes be annoying is the omnipresent beeper. Some models produce a rather irritating sound that you simply want to switch off after a while. Unfortunately, only two of the twelve instruments we tested allow this (Skil 550 and Bosch PDO Multi).

All pipe and wire locators utilise capacitive coupling between individual metal surfaces to detect wooden joists and studs. This allows the joist or stud location to be determined fairly accurately. Capacitive coupling is less suitable for detecting metal pipes, so it is not as

PIPE & WIRE LOCATORS



easy to determine exactly where they are located in the wall with the capacitive coupling method. For this reason, some scanners also have a coil that responds to changes in the magnetic field. This makes it easier to determine the exact location. With some instruments equipped with a detection coil, the user guide also states that the device is more sensitive to metal pipes if you rotate it by 90° so the coil is parallel to the pipe. The Bosch and Skil units have an especially handy design feature (see **Figure 2**): a hole at the top of the instrument that shows exactly where the measuring coil is located. This way you can accurately determine where it's safe to drill and where it isn't.

Almost all of the instruments we tested (excluding the Bosch PD06) can detect wooden studs and joists, iron and copper pipes, and wires or cables carrying AC voltage. Thin PVC conduits (for electrical wiring) are nearly impossible to detect if they do not contain any wiring. PVC pipes can only be detected if they have thick walls and a diameter of 5 cm or more. Iron, copper and steel pipes and aluminium tubes can be detected reasonably well. Uponor pipes, which are used in floor heating systems and have composite walls (including an aluminium layer), are also detected well. All of the scanners also can also detect the presence of AC voltage, which is shown by an indication on the display or a separate LED.

Some of the scanners even provide 'left' and 'right' indications on the display when you're looking for a stud or pipe, which can sometimes come in handy. The Black & Decker BDS303, Zircon Multiscanner i320 and Zircon Multiscanner i700 provide this feature.

Practical testing

In order to test the capabilities of the pipe and wire locators with various types of material at various depths, we assembled a setup in the Elektor lab with several types of pipes, wires and cables and a wooden stud behind a gypsum board, arranged such that the depth could be varied. This made it easy to determine how deep a particular type of material could still be detected.

All of the test results are listed in the table. These test results of the scanners in this test can readily be compared with each other, but you should be cautious when comparing them with the values stated in the manufacturer's specifications because we made all the measurements with the various pipes and studs located behind a single gypsum board. The results with thicker gypsum boards or solid walls containing embedded pipes or wiring may differ significantly. In any case, it's always worthwhile to first experiment a bit on the wall where you want to locate a pipe, stud or wiring.

Black & Decker BDS300



Price: around £33 / €40

This bright orange pipe and wire locator is suitable for locating wooden joists and studs, metal pipes and live electrical wiring. The on/off button is on the side of the unit and must be held pressed while you're scanning the wall. There is a switch for selecting either wood detection or metal detection. The indicator is a LED strip with five LEDs. A separate LED lights up when a voltage (AC mains voltage) is detected. A buzzer sounds when the detected signal reaches the full-scale limit.

Black & Decker BDS303



Price: around £50 / €60

This larger B&D model has an entirely different form than its smaller brother, with a handle that lets you grasp it firmly. It is also suitable for detecting wooden joists and studs, metal pipes and live electrical wiring. You have to hold the large power button pressed while scanning the wall, but this is fairly easy thanks to the shape of the handle. There is a slide switch for selecting either wood or metal detection. The large LCD screen with orange backlighting has three large bar scales to indicate when the unit has detected something;

it can even sense studs to the left or right of the unit. The centre of a wooden joist or stud is indicated by a bull's-eye icon. A separate LED lights up when an AC voltage is detected. All of this is supported by a buzzer for acoustic signalling.

BASETech 3-in-1 detector

Price: around £16 / €20



The least expensive instrument in the group, this unit can also detect wooden joists and studs, metal pipes and live electrical wiring. It's even smart enough that you don't have to set it to particular type of material – it indicates by itself whether it has found wood or metal. You can also use the Function button to manually set it to wood, metal, or AC voltage. The large display indicates the measured signal level with a beefy 19-segment arrow. This instrument switches off automatically after several minutes of inactivity, or you can switch it off manually. A buzzer emits an irritating noise when the maximum signal level is reached, and at the same time an indicator LED lights up. There is a separate calibration button for recalibration between measurements, so you can adjust the sensitivity as necessary.

Bosch PDO6

Price: around £50 / €60



The PDO6 comes in the usual Bosch green and is the only instrument in the group designed solely to detect metal pipes and live electrical wiring, which is all that many users need in actual practice. You press the on/off button to switch the unit on, and it switches off when you press the button again or after it remains idle for a while. The LCD screen is small but effective, with a bar scale for the signal level. It also displays an icon when a voltage is detected. A hole at

the top of the unit indicates the exact measuring point, so you can accurately determine and mark where you can or can't drill a hole. The green illumination of this hole changes to red when the measured signal rises to a high level. In addition, the light starts blinking when a voltage is detected.

Bosch PDO Multi

Price: around £75 / €90



The 'big brother' of the PDO6 can detect wood in addition to metal and voltage. It also has a distinctive illuminated measuring hole. This scanner has a separate on/off button, a button for wood detection, a button for metal detection, and a Zoom button. The instrument switches on when any button is pressed, and it switches off automatically after several minutes of inactivity. You can also switch it off manually with the on/off button. The display has three separate bar scales: one for voltage and two for signal level. At high signal levels, the illumination of the measuring hole changes from green to red and the buzzer beeps. Fortunately, you can disable the buzzer if you wish. When you're looking for metal objects, you can press the Zoom button to determine the precise location after initial detection. This activates an additional bar scale. The Zoom button must be pressed and held continuously when scanning for wooden objects. There is a pencil in the bottom of the unit for marking identified locations.

Brennenstuhl WMV Plus

Price: around £16 / €20



This unit is housed in a modestly dimensioned enclosure and can detect wood, metal and AC voltage. It has a slide switch on the front that you first have to set to the desired position before you press the Scan but-

PIPE & WIRE LOCATORS

ton. Unfortunately, after this the display does not provide any indication of which function is selected, so you have to remember which position belongs to which function. There are two Scan buttons, and you can press whichever button is easier to reach in a particular situation. You must also hold it pressed while scanning. The display shows a two-digit number that indicates the signal level, along with a multi-segment bar scale as an extra indicator. Here again a buzzer provides the accompanying acoustic indication. The instrument must be rotated by 90° for more accurate detection of metal pipes.

Laserliner Starfinder

Price: around £25 / €30



This a small, handy scanner designed to detect studs and live electrical wiring. The user guide states that it can recognise metal studs as well as wooden studs and that no separate setting is necessary for this. Seven LEDs arranged in an arc are used to indicate the signal level as well as the selected sensitivity setting. Pressing the Mode button switches on the scanner, which switches off automatically after several minutes. You can also use the Mode button to switch between stud detection and voltage detection. Three different sensitivity levels can be selected with the Set button. There is a large Cal button for calibrating the unit. A 'calibrate' LED starts blinking when a new calibration is necessary. More LEDs light up when a stud or a voltage is detected, depending on the signal level, and a buzzer sounds when the maximum signal level is reached. A separate warning LED also lights up when an AC voltage is detected.

Laserliner Multifinder Pro

Price: around £50 / €60



This hefty scanner with a built-in handle resembles the smaller Starfinder in terms of functionality and operation, but instead of LED indicators it has a large illuminated LCD screen with a big multi-segment bar scale that indicates the signal level. The scanner has separate buttons for power on/off, wood, metal, voltage, sensitivity, and calibration. It switches off automatically after several minutes of inactivity. The display clearly indicates what you have to do. For example, the first thing you see is a message telling you to place the scanner against the wall and then press the Cal button. A voltage indicator LED lights up when a voltage is detected. There are three manually selectable sensitivity levels, and of course there's a buzzer.

Skil 550 multi-functional detector

Price: around £62.50 / €75



The sizeable scanner has a separate on/off button, a button for wood detection, a button for metal detection, and a Focus button. Like the Bosch scanners, this instrument has a hole that shows the exact measuring point. The instrument switches on when any button is pressed and switches off automatically after five minutes of inactivity, or earlier if you press the on/off button. The display has separate bar scales for voltage and wood or metal. When the indicated value rises, a LED also lights up and a buzzer sounds. When you're looking for metal objects, you can press the Focus button to determine the location more precisely after initial detection. The Focus button must be pressed and held continuously while scanning for wooden objects. Along with the Bosch PDO Multi, this is one of the few instruments that allows you to switch off the buzzer.

Stanley Fatmax Stud Sensor 400

Price: around £35 / €42



This scanner in typical Stanley colours has only one button, which acts as an on/off switch. It must be pressed constantly while you're scanning. The unit features automatic sensitivity setting, with the sensitivity level indicated by three LEDs below the LCD screen. The large display has several arrows and a bar scale to indicate the location of a stud or pipe. A buzzer sounds at the full-scale signal level or when an AC voltage is detected. A separate LED also lights up when a voltage is detected. There is a separate 'AC tracing' mode (selected by pressing the button twice in a row), for easy detection and tracing of electrical wiring.

Zircon Multiscanner Pro SL

Price: around £25 / €30



This model has a slide switch for selecting one of four different detection modes: wooden joists or studs, high sensitivity for deep joists or studs, metal, and voltage. The power button must be held pressed during scanning. The large LCD screen shows the selected settings, calibration mode, battery state, and – most importantly – the measured field strength with a 17-segment arrow, where the number of illuminated segments increases with increasing signal level. Here again a buzzer sounds when the maximum signal level is reached, and an LED lights up and shines on the exact measuring point on the wall, to make it easier to mark the right location.

Zircon Multiscanner i320

Price: around £41 / €50



The i320 closely resembles the Pro SL in terms of functionality. It also has a slide switch that can be set to metal, wood, or deep wood. The AC Scan mode of the Pro SL is missing here, but the i320 can

also detect AC voltage, which is shown by a blinking 'AC' indicator on the display. The instrument is fairly slim and has an on/off button on the side that must be held pressed during scanning. The display is virtually the same as the more expensive i700 model, but without backlighting. The signal level is shown by a broad bar scale, which also indicates the location of the joist, stud, pipe or wiring. Naturally, there's also a noisy buzzer, and like the other Zircon scanners we tested, this model has an LED that indicates the centre of the detected joist, stud, pipe or wiring.

Zircon Multiscanner i700

Price: around £66 / €80



This more expensive model from Zircon at least wins the prize for futuristic design. It consists of two sections joined by a hinge structure. This arrangement forces you to press the bottom part (the 'handle') slightly downward when the instrument is held against a wall, and this motion causes the scanner to switch on automatically. There is a slide switch for setting the scanner to wood, metal, or voltage mode. The large display has a horizontal bar scale that shows the signal level as well as left/right/centre indication. There are two LEDs that light up to indicate the precise location of the centre of the joist, stud, pipe or wiring, augmented by a beeper. The final feature of this model is an integrated marker in the form of a pencil lead that marks a line on the wall when you press the Mark button on the bottom section of the scanner.

Conclusion

After making a lot of measurements and performing various practical tests, we have good news as well as bad news for you. First the good news: all of the tested units work properly, even including the least expensive unit (£16/€20). Now the bad news: if you want more features, more convenience or a more elaborate display, you have to spend a good deal more than 16 pounds.

It's difficult to pick a clear winner. The Black & Decker BDS303 is the best choice for wood detection, while the Bosch PDO Multi is the best for detecting metal objects and the Stanley FatMax Stud Sensor 400 is the undisputed champion in detecting AC voltage.

In terms of the price/performance ratio, the BASETech is clearly the best instrument, but detecting wood is not its strong point. However, all of its other test results are above average. Next comes the

PIPE & WIRE LOCATORS



Zircon Multiscanner Pro SL, priced slightly higher, which is a somewhat older model but nevertheless works just as well as the newer Zircon models in terms of the test results. For this money, you get an excellent all-rounder that is also suitable for detecting wood and AC voltage.

If we consider ease of use in addition to the test results, we find that the Bosch PCO Multi and the Skil 550 (which clearly come from the same factory) have the most convenient design thanks to the combination of straightforward use, a clear display, and precise location of metal objects thanks to the coil located around the measuring hole. The only minus here is that you have to hold a button pressed while scanning for wood. Unfortunately, these units are also among the most expensive in our test.

Our recommendation if you're looking for a pipe and wire locator is to first consider what you want to use it for (what do you want to find), how often you are likely to use it, and how much you're willing to pay for the convenience. Based on this information, select a model from the table that meets your needs.

Good luck with your handyman jobs, and always watch out for hidden electrical conduits and water pipes!

(100016-1)

Black & Decker, Bosch, Brennenstuhl, Skil and Stanley scanners are available at building merchants and DIY shops.

BASETech products can be purchased from Conrad Electronics, www1.conrad-uk.com.

Zircon: www.zircon.com/buy/wheretobuy.html

Laserliner: www.umarex-laserliner.de.

Table 1. Test results: detection range (cm).

Model	Wood 4-8 x 17 cm	Iron	Copper	Aluminium	Uponor	PVC pipe	PVC conduit with wiring	AC voltage
BASETech 3-in-1 detector (€ 20)	2	10*	5*	5*	5*	< 1	2*	3
Black & Decker BDS300 (€ 40)	3	9*	4*	5*	5*	2.5**	2	1.5
Black & Decker BDS303 (€ 60)	6	7	3	4	5	4**	2	3
Bosch PDO 6 (€ 59)	-	8	5	6	5	-	< 1	2.5
Bosch PDO Multi (€ 92)	2.5	11	6	7	9	2**	1.5	2.5
Brennenstuhl MFD WMV Plus (€ 40)	3	4	2.5	2.5	3	< 1	1	5
LaserLiner Starfinder (€ 30)	3.5	4	3	4	5	< 1	5	1.5
LaserLiner MultiFinder Pro (€ 62)	4.5	9	5	5	6	2.5**	2.5	3
Skil multi-functional detector 550 (€ 75)	2.5	9	6	6	8	2**	2	2.5
Stanley FatMax Stud Sensor 400 (€ 42)	4	7	6	3	6	< 1	3.5	8***
Zircon Multiscanner Pro SL (€ 30)	3.5	6*	2.5	3	3.5	2**	4	7
Zircon Multiscanner i320 (€ 50)	4	6*	2*	3.5*	3*	< 1	2	1.5
Zircon Multiscanner i700 (€ 82)	2	6*	2.5*	3*	3.5*	< 1	2	2

PVC conduit, iron pipe and Uponor pipe diameter 5/8" (16 mm); copper pipe and aluminium tubing diameter 12 mm. All measurements made through a 9.5-mm gypsum board.

* Scanner rotated 90°

** Wood detection mode

*** AC detection LED lights up already at a distance of 16 cm

Prices are average retail prices including VAT. Euro / pound exchange rate: 0.83.



QUASAR
electronics

The Electronic Kit Specialists Since 1993

Quasar Electronics Limited
PO Box 6935, Bishops Cleeve
CM23 4WP, United Kingdom
Tel: 01279 467799
Fax: 01279 267799
E-mail: sales@quasarelectronics.com
Web: www.quasarelectronics.com

Postage & Packing Options (Up to 0.5Kg gross weight): UK Standard 3-7 Day Delivery - £4.95; UK Mainland Next Day Delivery - £9.95; Europe (EU) - £8.95; Rest of World - £12.95 (up to 0.5Kg)
!Order online for reduced price UK Postage!
We accept all major credit/debit cards. Make cheques/PO's payable to Quasar Electronics. Prices include 15.0% VAT.
Please visit our online shop now for details of over 500 kits, projects, modules and publications. Discounts for bulk quantities.



01279 Credit Card Sales 467799

Motor Drivers/Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full range and details.

Computer Controlled / Standalone Unipolar Stepper Motor Driver

Drives any 5-35Vdc 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps. Provides speed and direction control. Operates in stand-alone or PC-controlled mode for CNC use. Connect up to six 3179 driver boards to a single parallel port. Board supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - **£15.95**
Assembled Order Code: AS3179 - **£22.95**



Computer Controlled Bi-Polar Stepper Motor Driver

Drive any 5-50Vdc, 5 Amp bi-polar stepper motor using externally supplied 5V levels for STEP and DIRECTION control. Opto-isolated inputs make it ideal for CNC applications using a PC running suitable software. Board supply: 8-30Vdc. PCB: 75x85mm. Kit Order Code: 3158KT - **£23.95**
Assembled Order Code: AS3158 - **£33.95**



Bi-Directional DC Motor Controller (v2)

Controls the speed of most common DC motors (rated up to 32Vdc, 10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections. Kit Order Code: 3166v2KT - **£22.95**
Assembled Order Code: AS3166v2 - **£32.95**



DC Motor Speed Controller (100V/7.5A)

Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£17.95**
Assembled Order Code: AS3067 - **£24.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU445 £7.95

8-Ch Serial Isolated I/O Relay Module

Computer controlled 8-channel relay board. 5A mains rated relay outputs, 4 isolated digital inputs. Useful in a variety of control and sensing applications. Controlled via serial port for programming (using our new Windows interface, terminal emulator or batch files). Includes plastic case 130x100x30mm. Power Supply: 12Vdc/500mA. Kit Order Code: 3108KT - **£64.95**
Assembled Order Code: AS3108 - **£79.95**



Computer Temperature Data Logger

4-channel temperature logger for serial port. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor. Kit Order Code: 3145KT - **£19.95**
Assembled Order Code: AS3145 - **£26.95**
Additional DS1820 Sensors - **£3.95 each**



Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two and Ten channel versions also available. Kit Order Code: 3180KT - **£49.95**
Assembled Order Code: AS3180 - **£59.95**



DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. Not BT approved. 130x110x30mm. Power: 12Vdc. Kit Order Code: 3140KT - **£74.95**
Assembled Order Code: AS3140 - **£89.95**



Infrared RC Relay Board

Individually control 12 on-board relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112x122mm. Supply: 12Vdc/0.5A
Kit Order Code: 3142KT - **£59.95**
Assembled Order Code: AS3142 - **£69.95**



New! 4-Channel Serial Port Temperature Monitor & Controller Relay Board

4 channel computer serial port temperature monitor and relay controller with four inputs for Dallas DS18S20 or DS18B20 digital thermometer sensors (£3.95 each). Four 5A rated relay channels provide output control. Relays are independent of sensor channels, allowing flexibility to setup the linkage in any way you choose. Commands for reading temperature and relay control sent via the RS232 interface using simple text strings. Control using a simple terminal / comms program (Windows HyperTerminal) or our free Windows application software. Kit Order Code: 3190KT - **£69.95**



PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £14.95
18Vdc Power supply (PSU120) £19.95
Leads: Serial (LDC441) £3.95 / USB (LDC644) £2.95

USB & Serial Port PIC Programmer

USB/Serial connection. Header cable for ICSP. Free Windows XP software. Wide range of supported PICs - see website for complete listing. ZIF Socket/USB lead not included. Supply: 16-18Vdc. Kit Order Code: 3149EKT - **£49.95**
Assembled Order Code: AS3149E - **£59.95**

USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows Software. ZIF Socket and USB lead not included. Assembled Order Code: AS3128 - **£49.95**



See website for full range of PIC & ATMEL Programmers and development tools.



 www.quasarelectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads

Make Room for the Roomba!

Elektor Teardown Session

By Wisse Hettinga (Elektor Editorial)

Without question, one of the duties we enjoy the most at Elektor is organising teardown parties, where the only objective is to take something apart. There's nothing more fun or exciting than attacking a piece of equipment (preferably something expensive) with a screwdriver and a hobby knife, and with the vague expectation that we we'll be able put it all back together afterward. This time we wanted to have a closer look at a robot vacuum cleaner, and one of our colleagues in Customer Service just happened to have one. Jolanda! How about loaning us your Hoover for a little experiment?



Fortunately, she was willing to sacrifice her Roomba to the cause of science, and – believe it or not – she was even excited at the prospect. With a good supply of beverages and a keen photographer on hand, we were able to document the whole process for posterity. The iRobot Roomba is around 30 cm in diameter and stands 10 cm high. It (or should we say 'she', since it moves so gracefully?) travels around the room sucking up everything in its path.



encounters an obstacle it takes a different route. After finishing the job (all fully configurable), it returns to its charging station. It has sensors to make sure it doesn't fall down the stairs. If you turn it upside down, you can see that it's fitted with a roller brush, along with a small rotary brush (side brush) for the corners. Finally, there's an optical sensor on top of the Roomba that enables it to dock smoothly with its base station.

Teardown

When teardown time comes, there's only person on the team who can wield a screwdriver with no sign of hesitation: Jan. Even the threat of docking his pay to cover any resulting damage doesn't hold him back. Now we can see what's inside: a battery (3 A, 12 cells, 15.57 V) and sensor contacts, the spring-mounted wheels with their own motor (RS 540), a bunch of screws and bushes, and – of course – lots of dust. The front (steering) wheel has a black and white pattern, which makes it easy to see whether the Roomba

  It comes complete with a charging unit, and it has an extra device you can use to create a virtual wall. With its bumper, it automatically detects any obstacles in its path, and when it





is moving. We also see another four IR sensors that help keep the Roomba on the right path.

Some of the dust manages to get past the filter. Apparently it's a good idea to clean the Roomba from time to time.

Now we come to the electronics. There's a sizeable PCB, with as its most prominent features a WiFi daughterboard with a Freescale MC13202r, an ST ARM7 master micro-controller that looks after all the operating functions, and a connector for updating the software. Of course, there's also a 'kinda' control panel with LED display for setting the time and other functions. In order to maintain a good working relationship with its owner, the Roomba can report faults and problems in various languages. Now we have a big pile of parts, and it's time for the miracle: putting it all back together and make Jolanda happy again.

All's well that ends well, as they say.


With its update connector, the Roomba naturally lends itself to updating or reconfiguring the software. You can find all sorts of tweaks and hacks on the Web that let you use the Roomba for other purposes, such as a musical instrument. You can even turn it into a fighting machine, as illustrated at

- <http://roomba.pbwiki.com>

- www.makezine.com/blog/archive/2006/03/videos_from_roomba_fights.html

- <http://todbot.com/blog/2006/05/03/roombamidi-roomba-as-midi-instrument>

(100015-1)

 

Star LED instead of incandescent lamp

By Co Slokker (The Netherlands)

Traditional indicator lamps with a filament or often also available these days — on a one-for-one replacement basis — in versions made with LEDs. In this implementation the LED, together with a series resistor, is mounted in the traditional housing. In some applications there are wide variations in ambient light (for example day/night in the cabin of a vehicle). The lamps are dimmed at lower ambient light levels so that they are not annoyingly bright, usually using a series resistor. When you replace the incandescent signal lamp in such a circuit with an LED-lamp then the LED will be much too bright in the dimmed state. This is caused by the different characteristics between incandescent and LED-lamps.

However, by taking these characteristics into account it is certainly possible to dim the LED lamps. As an example, we will compare the characteristics of a green CML StarLED 1507145G3 with a standard 28 V/45 mA incandescent lamp. We start by determining the current drawn as a function of applied voltage for each type of lamp. Then we measure, in a dark environment, the change of relative brightness as a function of the applied voltage (see **Figure 1**). From this we conclude the following:

- At 28 V the LED is about four times as bright as the incandescent lamp at a third of the current
- The current characteristic of the incandescent lamp is strongly non-linear, while that of the LED is practically linear (after overcoming the forward voltage drop).
- The relative brightness of the incandescent lamp increases exponentially, while that of the LED is initially linear after which the slope gradually reduces.

When dimming the incandescent lamp you reduce the voltage with a series resistor. From the graph you can see that the lamp still draws about 28 mA at 12 V, while the brightness is effectively nil. The series resistor amounts to

$$(28-12) / 28 \times 10^{-3} = 571 \Omega$$

At 12 V the brightness of the LED hasn't even halved yet: 14.5 mS^[1] compared to 27.4 mS at 28 V.

From measurements it appears that for the LED at 12 V to appear just as bright as the incandescent lamp (6.8 μS^[1]), a current of only about 24 μA is required; more than 1000 times smaller than that for the incandescent lamp at 12 V! The series resistor required for this is

$$(28 - 2.5) / 24 \times 10^{-6} - 1800 = 1 \text{ M}\Omega \text{ (approx.)}$$

which is obviously much more than the 571 Ω required for the incandescent lamp!

Figure 2 shows a simple circuit for the practical evaluation of the automatic brightness control for two StarLEDs. Because the LEDs that we tested are at 6 V are already just as bright as the incandescent lamp at 28 V, a 9 V battery will suffice for the power supply. With S1 you can select between automatic and manual control; the third position turns the circuit off.

The automatic control is achieved with an LDR driven double current mirror, built around T1, T2 and T3. The current through each LED is

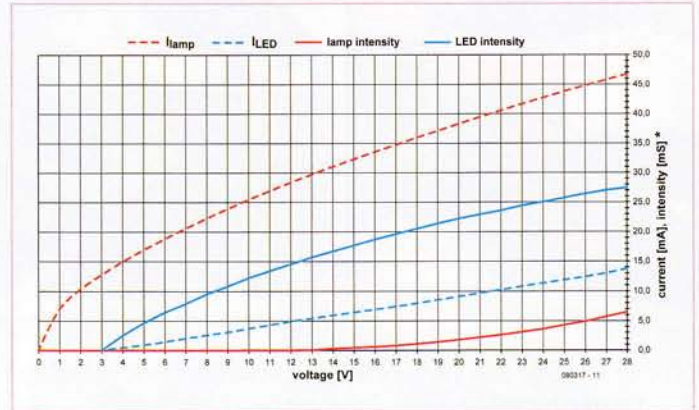


Figure 1. Brightness of the LED and incandescent lamp as a function of applied voltage.

equal to the current that flows through R1. You have to make sure that the position of the LDR is such that it is not illuminated by any of the LEDs, otherwise there is the chance of runaway feedback to maximum brightness.

With S1 in the 'manual' position you can also adjust the minimum desired brightness of the automatic control. In absolute darkness, after sufficient recovery time has elapsed, the LDR that we used here has a very high dark resistance (hundreds of MΩ) and only the current through R_v now determines the brightness. Once your eyes are sufficiently accustomed to the darkness you can set the desired brightness with potentiometer R_v. A logarithmic type is used for R_v to make the adjustment of low brightness levels easier.

Once S1 is switched back to 'automatic' there is no need for any further adjustments. The potentiometer could then be replaced with a trimpot or fixed resistor of appropriate value.

(090317)

 


Figure 2. Circuit to evaluate the brightness of the LEDs.

Measured again...

By Ton Giesberts (Elektor Labs)

The article 'Blinded by the Light?' in the February 2010 edition showed that LED lamps didn't exactly present a clean load to the AC grid and in fact created quite a bit of pollution and disturbance. A number of readers gave us some interesting feedback to this article. One of them was Gerard Grashof, who works for Fluke Industrial and provides product support for their Scopemeter and advice on Power Quality. He wanted to point out that the behaviour of such mains-powered devices could be closely monitored and analysed with the help of some special measuring equipment made by Fluke.


We were keen to find out more about this and invited Gerard over to the Elektor Labs, obviously along with a Fluke Power analyzer!

When we previously made measurements with a 'normal' oscilloscope in the Elektor Lab on various types of lamp we already determined that, although LED lamps were very energy efficient, they presented a strange, complex load to the AC grid. The harmonics created on the AC supply lines by these devices have an effect on the size of the substations required at the end of the electricity distribution system. These harmonics are responsible for extra losses in the transformers, which means they should really be over-engineered to cope with this extra heat (larger losses). The losses in the transformers are proportional to the frequency of the harmonic multiplied by its amplitude. This is represented by the so-called k-factor, which indicates how much a transformer should be de-rated as a result of harmonics in the current. Mid and high-voltage transformers in the power AC grid can normally cope with a k-factor of 3–4. Fluke has designed an analyzer specifically for measurements on (three-phase) AC powered equipment: the 434 Power Quality Analyzer. With the help of such an analyzer we have once more made some measurements on an LED lamp. To make it easier to measure the current we used an i310s AC/DC Current Clamp. This time round we tested the Pharox lamp made by Lemnis, a 6-watt LED lamp marked by a peak value in its current consumption that's similar to that of the LED lamps we used in the original article.

In order to calibrate the equipment we first measured a 100-watt incandescent lamp. After carefully adjusting the current clamp (the Hall sensor used inside it is slightly temperature dependent) we measured a power factor of 0.98. With a pure resistive load we were really expecting exactly 1. At first we thought this might have been due to a slightly less than perfect sinusoidal waveform of the mains voltage in our Lab. However, another reason could be that due to the small current flow the current clamp did not get a large enough signal to measure accurately. In this case a simple trick is to loop the cable twice through the current clamp instead of straight through. The measured value is then too big by a factor of 3, but at least the power factor was now found to be a perfect 1.

Now the time had come to take measurements on the LED lamp. The current consumption was found to be 0.067 A (*this*

represents the measured value divided by 3, which also applies to all other current measurements). $\cos \phi$ was a neat 0.98, but the power factor was only 0.42. The latter is therefore a problem with energy-saving lamps, especially with LED lamps. The measured pure power consumption was 5.87 W, the apparent power was 14 VA and the reactive power was 12.7 VAR. The following day we carried out the measurements again and obtained slightly different results: 5.83 W, 11.3 VA and 9.67 VAR, $PF = 0.51$ en $\cos \phi = 0.975$. The differences could possibly be explained by the temperature dependence of the current probe and the LED lamp.

 

The most important measurement we obtained was the k-factor for this LED lamp. This turned out to be a massive 99 (THD was 155 %)! The second measurement returned an even higher k-factor of 130, with a THD of 150 % (this changed as the lamp was on for longer). This really is an extreme value, especially when you consider that in many countries, AC power grid transformers are designed with a k-factor of 3–4 in mind...

These measurements show that big improvements have to be made in the design of LED lamps, otherwise there is a good chance that the electricity suppliers will suffer from big problems once these LED lamps start to be used on a large scale!

(100099)

Embedded World 2010 *or how to*



Vision enhancement? (source: NürnbergMesse/Frank Boxler)



Open vs. closed source: Microsoft cohabiting with a penguin. (source: NürnbergMesse/Frank Boxler)



More than 700 students came to visit the show on Student Day. (source: NürnbergMesse/Frank Boxler)

By Antoine Authier & Clemens Valens

In the first week of March the German city of Nuremberg once again hosted the Embedded World Exhibition & Conference. 730 exhibitors showed 18,350 visitors the full range of products for embedded technologies in 2010: hardware, software, tools, services and lots more. Elektor was among the visitors – here is our report.

Four huge halls full of booths (not booze) loaded with electronic novelties really are too much to handle, even when you have three days. At Elektor we knew this, so we came prepared with a list of exhibitors that we definitely wanted to visit. On this list was German Renesas distributor Glyn, and since they were conveniently located right in front of the main entrance, this was our first stop. Glyn staff informed us about the upcoming merger of Renesas and NEC, the companies continuing under the name 'Renesas Electronics Corporation' (REC). Other interesting news was the new RX MCU family positioned by Renesas as the upgrade successor to the H8SX and R32C, the latter well known to Elektor readers. This family is supposed to provide more power at less consumption, which was clearly the lead theme for this exhibition. It was green and low-power all over the place.

Being press we attended the official press conference and participated in a guided tour of the show. During this tour the green side of the show was once again emphasised with visits to (amongst others) Hitex, Mentor Graphics and Fraunhofer. Hitex presented a clever tool for current consumption analysis of software called PowerScale and won the Embedded World Award in the category Tools. The winner in the Hardware category was Energy Micro's EFM32, the world's most energy friendly 32-bit microcontroller that consumes only 180 μA per MHz when running from 3 V.

Microchip was of course present too with their extreme low-power (XLP) microcontroller family (50 μA per MHz). A novelty was their new MCP1640 ultra low-power boost regulator that took four years to develop. It will startup from 0.65 V and then pump from as low as 0.35 V up to 2 to 5.5 V which is obviously great to discharge batteries deeper.

Touch technology was another important theme during this exhibition. Atmel for instance won the award in the Special Merits category for their new maXTouch technology presented in the form of the chip mXT224. This IC allows for touch screens that support not just finger touch but also stylus, fingernails and even gloves for drawing or character recognition. Atmel's touch products are supported by the free Qtouch library and Altium integrated a module in their Designer schematic/PCB drawing software for quickly designing and drawing compatible touch sensors on PCBs in any shape you like.

STMicroelectronics distributed for free (and not asking for address details!) tiny development kits for their new STM8S 8-bit microcontroller family supported by free programming tools. This kit sports one capacitive touch key that controls an

develop green tactile products quickly

LED and a USB port. When connected to a computer it becomes a "mass" storage device of 32 KB.

That brings us to the third major theme of Embedded World 2010: making microcontroller development easy. An increasing number of microcontroller manufacturers offer free or 'mildly restricted' tools to quickly get an application up and running. ST teamed up some years ago with the French company Raisonance to develop cheap tools for ST's ARM products. The latest tool from Raisonance is the Open4 (business) that will be available from ST too, albeit under another. This tool, a Gameboy-ish device with a colour display, a touchscreen, a joystick, audio interface and USB debugging/programming port works with user supplied microcontroller cartridges that determine the functionality of the device. Software development for the user cartridge is done with cheap or even free programming tools and the device is supposed to sell for less than \$100.

Free tools are also available from FTDI for their brand new Vinculum II processor. The first Vinculum was a cheap solution for easily building of USB products, but FTDI went one step further with the second version that has become a full blown generic 16 bit microcontroller with lots of other peripherals and of course USB. Programming and debugging is cheap as the tools are all free. After we signed a non-disclosure agreement, FTDI showed us what will definitely be the next killer product for USB to RS-232 converters. Keep your eyes open, this product is going to change the world!

Green, cheap and easy are also the main features of the mbed ARM Cortex-M3 board. Essentially an ARM product, it was presented on the NXP stand because the currently available mbed boards have NXP processors. Software development for mbed employs a browser and a compiler farm on the internet. Write a program, compile it online and then download the executable to your mbed board. The boards are cheap and the tools are free, and many libraries are available.

Following NXP and their LPCxpresso product line with free-ish (up to 128 KB executable) programming tools by Code Red, compiler manufacturer Keil too presented a kind-a-free Eclipse & GCC based open source compiler for ARM processors, the DS-5. Keil (owned by ARM) made a point of telling us that they actively participate in the open source community and they contribute to the GNU C/C++ compiler. Similar statements were made by other software producing companies, which brings us to the interesting observation that the open source community seems to be slowly taken over by commercial entities that pay their employees to write free software together with their competitors.


Of course there were many more interesting products and demonstrations to see, but we do not have the space to mention them all here. So why don't you go and see for yourself next year? Nuremberg is a nice city with a well-preserved ancient centre and good food and accommodation. One warning though: try to not eat all the sweets, chocolates and cookies available on almost every booth, you need good teeth to eat your way through the information.



Tintin at the Embedded World. (source: NürnbergMesse/Frank Boxler)




Atmel's Qtouch suite.

 

The Vinculum II (VNC2) is more than just a USB host controller.

(100215-1)

The making of the dsPIC board (2)

 

Last month we began an insight to how we at Elektor hone a readers circuit to create a tested, reproducible design, the story continues... In the first instalment [1] we reported how one of our resident engineers, Daniel Rodrigues (who hails from Portugal) redesigned the PCB and finalised the parts list. The components for this board were now on order and Daniel began work on the second set of boards for the project. This is an expansion board containing interfaces to the peripherals such as motorised valves and sensors. The two boards together form a complete control unit which manages a solar heating installation to optimise the energy harvest (see the article elsewhere in this magazine).

Once all the components for the dsPIC controller board had arrived Daniel began with the building process "I decided to use the SMD oven for one of the boards and hand-solder the other one", explained Daniel. As luck would have it we received a visit by a representative from the Dutch distributor of the 'Magnus' professional USB microscope for PCB inspection [2] (with our lab assistant Jan Visser). This was too good an opportunity to miss; Daniel rigged it up to inspect the freshly built boards. It showed up a thin solder bridge between two microcontroller pins which curiously did not measure as a short circuit. In most cases this sort of failure can be quickly identified by simple electrical tests and easily remedied.

Once he was happy with the build Daniel sent off a finished prototype controller board to the project's authors for functional testing. Here in the Elektor lab we are familiar with Murphy's Law, we know if anything can go wrong then it will. In this case Yves Birbaum had unfortunately been laid low by an illness and wouldn't be able to test the board for a few days. The uncertainty of the board's functionality was worrying Daniel. He started browsing the software folders in the solar-array controller project trying to find a routine to help in testing. Hopes were raised when he found some C files with the word 'essai' (French for 'test') in their titles; "unfortunately the functions were not much help for what I had in mind" recalled Daniel. Instead of sending characters back and forth between the con-

troller and PC using a terminal emulator program he wanted a more useful test with the controller switching a few test LEDs. He built the test hardware (see photo) and quickly modified the Main function in the C program to 'sweep' the line of LEDs. "Up till now I had only worked with the standard range of PIC controllers but as you would expect there are a lot of similarities with the dsPIC instruction set and the MPLAB-IDE and C30 Compiler are really well documented" enthused Daniel. In the meantime Clemens Valens, our French editor responsible for the two articles had put the finishing touches to the original text and there was enough time for it to be sent for translation into the other languages. The Elektor test routine would likely be of interest to constructors so we have included it in with the rest of the software.

By this time we had taken delivery of two of the bare expansion boards for this project. All of the components except the relays had been ordered from Farnell, unfortunately one of them; a hex inverter was not in stock "this added another week to the process" said Daniel and by the time everything arrived it was looking doubtful we would get the finished board to the authors in time. Daniel placed all the components and cranked up the reflow oven. We were soon to witness an extension to Murphy's Law which states that the chances of anything going wrong are multiplied by the inverse of the remaining time. During board testing a DC/DC converter was found to be faulty; "when I took a closer look I could see two tiny beads of flux had apparently oozed out of the component housing". Chances are that the device had given up the ghost during the re-flow process using lead-free solder. With the component replaced he was relieved to send the boards off with a clean bill of health. The final functional test can now only really be carried out by the project's authors where both the Elektor boards will replace the author's original to control the solar installation. One practical test is worth a thousand simulations!

(100216)

[1] www.elektor.com/091079

[2] www.tagarno.dk

NEW

DISTANCE LEARNING COURSE

Programming Embedded PIC Microcontrollers

→ using Assembly, C and Flowcode


Special introductory price:
£40 | \$70 | € 50 DISCOUNT
www.elektor.com/distancelearning

In this course you will learn how to program an embedded microcontroller. We will start with the absolute basics and we will go into a lot of detail. You cannot learn about software without understanding the hardware so we will also take a close look at the components and schematics. At the end of the course you will be able to design your own embedded applications and write the appropriate software for it.



Contents:

 - Background
- Digital Ports
- Serial Communication (RS232)
- Analog Signals
- Pulse Width Modulation
- Timers/Counters/Interrupts
- Memory
- LCD Display
- I²C Communication
- SPI Communication
- USB Communication
- Configuration (Fuses)
- Answers to the assignments
- Appendix



Your course package:


- Courseware Ring Binder (747 pages)
- CD-ROM including software and example files
- Application Board
- Support at Elektor Forum
- Elektor Certificate

Price: £395.00 | \$645.00 | €445.00

Please note: to be able to follow this course, E-blocks hardware is required which you may already have (in part). All relevant products are available individually but also as a set at a discounted price. Please check www.elektor.com/distancelearning for further information.



 Further information and ordering at
www.elektor.com/distancelearning



Cloud Altitude Meter

your head in the clouds with 'AirControl'

By Antoine Authier (Elektor Labs)
from an idea by Jürgen Maiss (Germany)

This circuit was dubbed AirControl because it indicates the altitude of the clouds by measuring air temperature and humidity and then silently doing a mass of scientific calculations.

It should make an interesting meteorological tool for people who keep an eye on the sky.



When it landed (on my desk), Jürgen Maiss' 'AirControl' prototype immediately aroused my curiosity and seduced me by its originality: how could this circuit, using a simple humidity (and temperature) sensor, work out the altitude of the cloud base for cloud masses?

"A gliding enthusiast, Jürgen is also a pilot; so meteorological data are vital to him, he's bound to know his subject!" I said to myself, though still sceptical "But are the results obtained in this way reliable?"

In addition, this circuit uses a miniature digital sensor that I hadn't ever used before... that was all it took to launch me into the adventure, without a balloon or tape-measure in sight.

From a meteorological point of view

First of all, a few reminders about thermodynamics. Not being a meteorologist, I

poured over various encyclopaedias to try and understand the phenomena being exploited here. Here are some results of my research.

This circuit measures the ambient air temperature and relative humidity. In order to determine the altitude of the cloud base, it is necessary to first calculate the altitude at which the water vapour in the air condenses.

The dew point [7] or dew temperature corresponds to the saturation temperature of the air at a given pressure — in other words, the temperature at which the water vapour in the air is at a maximum. If, at constant pressure, the air temperature drops below this dew point (isobaric transformation), the excess water vapour will condense to form cloud, fog (low cloud), or dew, depending

on the altitude at which the phenomenon occurs. The warmer the air, the more moisture it can hold.

The August-Roche-Magnus formula lets us approximate this (dew) temperature T_d :

$$T_d(T, RH) = T_n \cdot \frac{\gamma(T, RH)}{m - \gamma(T, RH)}$$

$$\gamma(T, RH) = \ln\left(\frac{RH}{100}\right) + \frac{m \cdot T}{T_n \cdot T}$$


$$\text{using the constants } \begin{cases} T_n = 243.12 \text{ }^\circ\text{C} \\ m = 17.62 \end{cases}$$

This approximation is valid 'above water' (in the jargon), i.e. for temperatures between 0 and 60 Celsius, and relative humidity between 1 and 100 %.

In order to understand the explanations that follow, you'll probably find it helpful to read up about 'atmospheric pressure' and 'convective instability' from the link [8]. Let's now consider the standard atmosphere model as used by many meteorological offices, with a vertical temperature gradient that remains of the order of $-0.65 \text{ }^\circ\text{C}$ every 100 m (approx. 300 ft) in the lower atmosphere (also called troposphere).

Specifications:

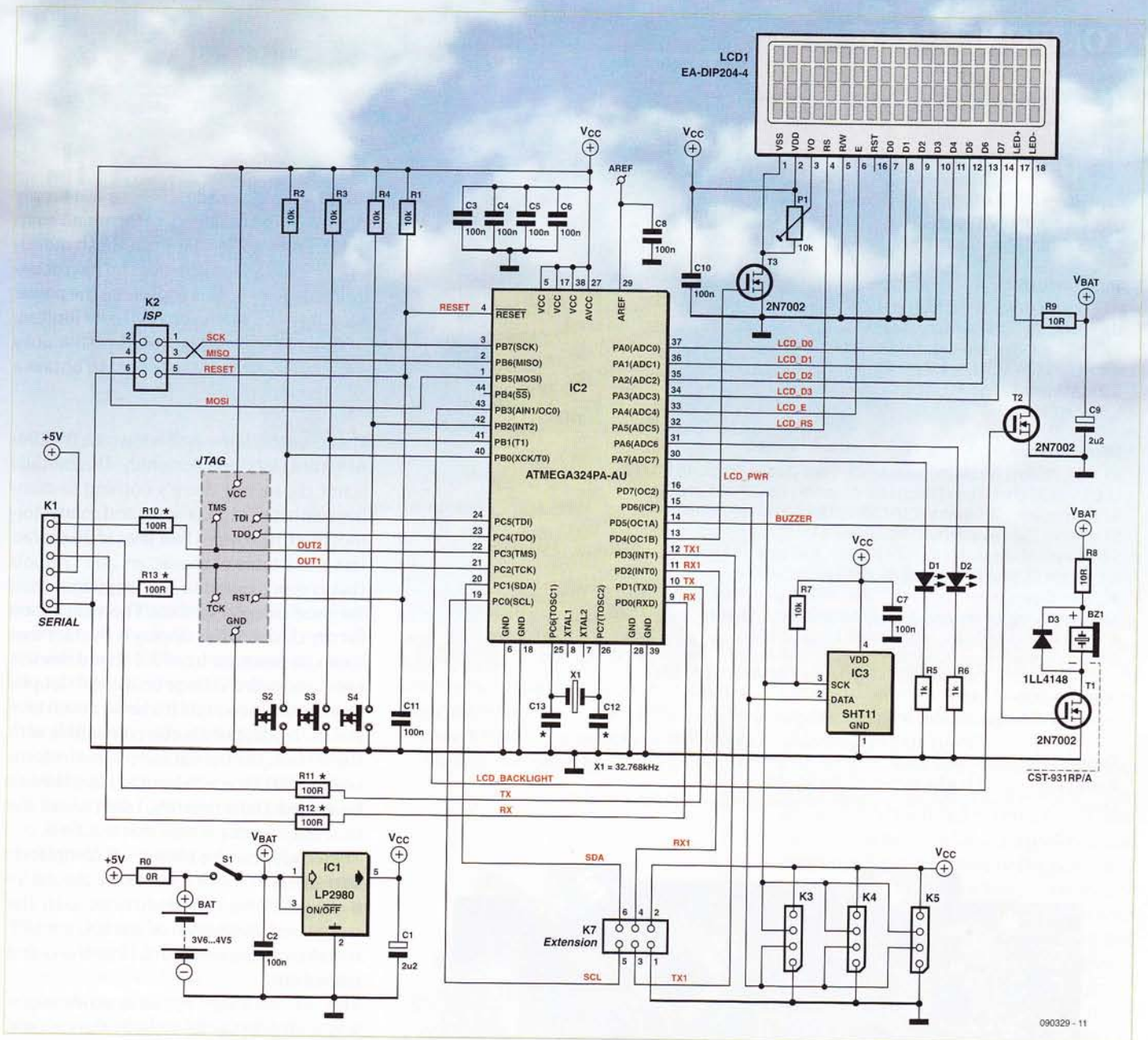- MCU: Atmega324PA-AU from Atmel, JTAG support
- SHT11 humidity sensor from Sensirion, 0–100 % RH, accuracy 3 %
- Powered by three AAA/R6 penlight cells
- Minimum battery life one week (with new batteries and without using the backlight)
- Works out the cloud base altitude
- 4 line × 20 character display
- Portable, sensor on detachable breakout board



090329 - 11

$$\nabla T(z) = \frac{-0.65}{100} [^{\circ}\text{C}/\text{m}]$$

$$\text{i.e. } \frac{T_d - T}{z_{\text{cloud}} - z_o} = \frac{-0.65}{100}$$

z_o being measurement altitude, we finally obtain

$$z_{\text{cloud}} = (T - T_d) \cdot \frac{100}{0.65}$$

This calculation assumes that the atmosphere is standard and that the humidity is constant with altitude... All that remains is to go up in a balloon to check if this model actually works in the troposphere (up to

about 16 km; 54,000 ft.). While we're waiting for the air in our balloon to heat up, let me tell you about the hardware platform.

Hardware

To be appealing a project like this needs to be portable, compact, elegant but sturdy, and have long battery life. Its supply voltage should not be more than 3.3 V. The display should be as compact as possible, but have good resolution. Everything housed in a little case with the power source, small enough to fit into your breast pocket or even smaller bits of textile.

Three 1.5 V AAA penlight batteries or 1.2 V rechargables, i.e. 4.5–3.6 V when connected in series, will each provide around 1000 mAh.

We'll come back later to the backlight for the display, which requires 5 V.

The supply for the various sensitive devices and modules is provided by an LP2980 [4] regulator IC from National, which can supply up to 50 mA with a very reasonable 0.12 V voltage drop. Ideal for battery-powered applications, this device supplies more than enough current for this part of the circuit, which at worst will consume 10 mA (during the measurement phase). The devices that consume more power — the backlight and resonator — will be connected to the batteries via resistors.

R8 protects the resonator [5], which is only rated for a maximum voltage of 4 V, whereas

COMPONENT LIST

Resistors (SMD 0805)

R1–R4, R7 = 10kΩ
 R5, R6 = 1kΩ
 R8, R9 = 10Ω
 P1 = 10kΩ SMD preset (Vishay TS53)

Capacitors (SMD 0805):

C1, C9 = 2.2μF 10V 10% tantalum (ESR 8Ω)
 C2–C8, C10, C11 = 100nF

Semiconductors


D1, D2 = LED, red, 3mm, high efficiency
 D3 = 1N4148 (SMD version: LL4148)
 T1, T2, T3 = 2N7002, n-channel MOSFET
 IC1 = LP2980AIM5-3.3, 3.3V / 50mA, regulator
 IC2 = ATmega324PA-AU, programmed
 IC3 = SHT11

Miscellaneous

X1 = 32.768kHz oscillator module, CL = 6pF (Epson Toyocom MC-306)
 LCD1 = 4x20 characters (Electronic Assembly EA DIP204-4NLED)
 BZ1 = miniature resonator (CUI CST-931RP/A)
 S1 = micro slide switch (EAO 09-10290-01)
 S2-S4 = pushbutton, SPNO, 12V / 50mA, 6x6 mm – 13 mm, Tyco Electronics FSM14JH
 K1 = 6-pin SIL pinheader, lead pitch 0.1 in. (2.54mm)
 K2, K6 = 6-pin pinheader, double row, angled pins, lead pitch 0.1 in. (2.54mm)
 K3, K4 = 4-way pin receptacle, lead pitch 0.1 in. (2.54mm)
 K5 = 6-pin SIL pinheader, lead pitch 0.1 in. (2.54mm)
 Enclosure, Bopla type BOS400 Streamline with battery compartment for 3 AAA cells (Bopla # BS 401 F-7024) and decorative fixing (Bopla # BS 400 DI-D-7024)
 PCB # 090329-1 [11]
 Front panel design, to print and cover with plastic foil, # 090329-F [11]

Complete kit (with SMD parts soldered on board)

 If you're interested in a kit version of this project, please let us know by e-mailing: editor@elektor.com, subject: AirControl Kit.



three new high-grade alkalines will supply over 4.7 V. The frequency of the sound emitted (around 2.7 kHz) is pulsewidth modulation (PWM) controlled by the microcontroller via FET T1. This also allows the power consumed by the resonator to be limited. Tests have shown that PWM with a duty cycle of 40 % makes it possible to obtain a good sound volume.

The LC display is the well-known EA DIP204-4 [3] from Electronic Assembly. This module is not cheap, but there's nothing to compete with it either. Compact and connector-mounted, it provides four lines of 20 characters and a table of characters and symbols that is more suited to our languages than the usual Oriental symbols. The main reason for my choice of this display is the fact that it can be powered from 3.3 V, and doesn't need a negative voltage on its contrast pin: just a preset is enough! It's being driven here in 4-bit mode, but it's also compatible with the SPI bus (see the data sheet for the Samsung KS4073), which I would have liked to have used. Unfortunately, I didn't have the time to experiment with that this time. The display can be turned off completely thanks to T3, which lets us save around 5–6 mA when the user doesn't need it. The complete initialisation of the LCD controller takes a little time each time the unit is turned on.

The LED backlight requires powering at 5 V, with resistor R9 to limit the current. The backlight is also connected to a microcontroller pin that can supply a PWM signal, which through FET T2 controls its brightness, and hence its power consumption. If the unit is powered from rechargeables rather than alkaline cells, the voltage to the backlight will only be 3.6 V (with fully charged batteries); in this event, the backlight brightness will be reduced, though that doesn't affect the readability of the display.

The circuit is based around an ATmega324PA processor [2] with numerous handy peripherals and very low power consumption. The ATmega88 originally used soon proved inadequate in program memory capacity, and in the number of input/output pins. What's more, the ATmega324 also



Figure 1. The PCB and main components. The great shy microcontroller is hiding under the display.

contains a real-time counter, which will let us measure the time. Watch out! Atmel provides here an `RTCCounter` which, even though it isn't a true `RTClock`, does prove jolly handy for developing a real-time clock in just a few minutes. This function will use a timer, a little bit of space in flash memory, an interrupt vector, and a few clock cycles. It's important to connect to pins `TOSC1` and `TOSC2` of the microcontroller a crystal oscillator that presents a load of 6 pF. In this event, capacitors `C12` and `C13` are not fitted. If the capacitive loading of the crystal is different, it must be corrected using capacitors `C12` and `C13`, the values for which can be determined with the help of the oscillator and ATmega data sheets.

The user interface consists of the display already described, three push-buttons, two LEDs, and a resonator.

The temperature and relative humidity measurements are performed using a SHT11 [1] from Sensirion, fitted onto a small breakout board, which will make it possible to fit it outside the case to improve measurement accuracy, as well as to use of for other projects (its size is small size, but not its price).

On the circuit diagram, you'll note three expansion ports:

`K1` is a serial port compatible with the USB-TTL232 cable available in the Elektor shop as ref. 080213-71, which is very handy for hassle-free development. This cable also lets you power the board from the USB bus 5 V rail, provided you make a solder bridge

across `R0` on the back of the board. In this case, it's vital to remove the batteries, as they'll be connected directly to the 5 V rail, which risks damaging them, or even causing them to explode!

Resistors `R10` to `R13` provide basic protection for the external connector, 100 Ω is fine.

 


Figure 2. The breakboard PCB before / after.

`K2` is an ISP connector for programming the microcontroller *in situ*, i.e. the pins of the SPI bus

`K7` offers a second serial port and the pins of the hardware I²C module. Both may come in useful later on.

Onboard software

The source code files for the onboard software, written in C, are available as a free

download on the project page on the Elektor website [11]; they can be compiled using the WinAVR software suite under Windows, or using `avr-gcc + avr-binutils` under Linux (see the `readme.txt` file to find out about the versions used).

I've tried to make everything as simple and easy to understand as possible. The program is structured in three layers. The hardware driver files have the prefix `dr` and contain the explicit name of the peripheral (e.g. `drSHT1x.c/h` for the Sensirion sensor). Only the driver layer can/needs to both access the hardware and provide a simple, but I hope effective, API (Application Programming Interface). The main file containing the 'main' function, which is nothing but the program's entry point (a sort of starting point) is `AirControl.c`, the files containing the tools have the prefix `tlk` and the user interface `ui`.

The sensor uses a synchronous serial link and a proprietary protocol for communicating with the microprocessor. This protocol is similar to the I²C bus one, but is sufficiently different to prevent us from using the ATmega's built-in hardware I²C module. No worries, Sensirion provides good explanations and I've written you a driver for reading the temperature and relative humidity of the air by simply calling the `drSHT1x_measure` function. This circuit returns the values for the air temperature or relative humidity. These values are linearized and compensated.

The real-time clock is available in the file `tlkTime.c/h`. It contains the code for

the date structure update interrupt vector every second, along with two functions for reading and setting the time.

You'll also find special drivers for the LEDs, the keypad, the resonator, and the display. There is also a driver for the serial port `drUART.c`, very handy for debugging the application.

The `tlkrRH.c` file contains the dew point and cloud base altitude calculation routines. It requires use of the `math(ematics)` library supplied with the `libc` for AVR, as I've implemented the calculations using floating point operators and variables to make the development faster... the downside is that the library takes up just over 2 KB of the flash memory, the code still runs fast, but I invite our readers to take up the challenge and re-program the whole thing using integers.

The dew point is calculated using the Magnus formula, the mathematical library provides the logarithm to base 10, knowing that

$$\ln\left(\frac{a}{b}\right) = \ln(a) - \ln(b)$$

and

$$\log_{10}(a) = \frac{\ln(a)}{\ln(10)}$$

and that

$$\gamma(T, RH) = \ln(10) \cdot (\log_{10}(RH) - 2.0) + \frac{m \cdot T}{T_n \cdot T}$$

with

$$\ln(10) = 2.302585$$

i.e. the C code:

```
H = (log10(RH) - 2.0)*2.302585 +
(m*T)/(Tn + T);
Tdp = Tn*H/(m - H);
```

The application is fairly simple and displays all the values available alternately.

Pressing the third push-button lets you set the time. All that remains is to program more economical power management, a turn-off delay time for the display, and configuration for the time interval between two measurements.

Construction

The circuit fits very snugly into the elegant *BOS Streamline 400* case from Bopla with its decorative sealing gasket, as long as you solder the display module directly onto the PCB. It will be flush with the front panel. Before soldering in the display, check the basic functioning of the device. Once the display is fitted, it hinders access to the microcontroller and the JTAG port.

Start by cutting off the part of the PCB intended for the SHT11, unless you really do want to use it inside the case — in which event, remember to provide good ventilation.

Don't try to snap it off; you must saw it off, using for example a little circular saw (and a vacuum cleaner). Avoid exposing the components to fine dust particles, and take care as well to protect your eyes and respiratory tract during this operation.

Connectors K3, K4, and K5 let you connect the humidity sensor inside or outside the case, depending on how you want to use it. For use outside, solder connector K4 **on the back** of the board. In this way, you'll find it easy to cut an opening in the case opposite the sensor PCB, without falling foul of the sealing gasket.

I recommend soldering the SHT11 onto its piece of PCB with a very fine-pointed iron, and avoid taking too long over it. You need to avoid drying out the sensor (refer to the documentation provided by Sensirion where applicable).

Then solder the SMS devices in the oven, then the through-hole components, finishing off with the connectors (only the ones you're going to be using) and the LEDs, which you'll need to fit under the front panel in the holes designed for this purpose.

For the switch and the serial link, it's best to start by milling out vertically within the

thickness of the lid so as to reduce it to around 1 mm. Then make the cut-out for the slide switch. The serial link is optional. If you're using neither it, nor the OUT1 / OUT2 signals, you don't need to make a hole in the case.

All that remains for you to do is to fix the PCB using two or three 2 mm self-tapping screws above the battery compartment. Print the front panel, laminate it with self-adhesive plastic film, for example, and stick it into the recess in the lid.

Conclusion

Many readers will be wondering what use it is to measure cloud base altitude. It will be of interest to pilots, modelling enthusiasts, and people who are simply curious about meteorology. But this project also forms a good base from which to develop a weather station or a climate-measuring device. We'll certainly be coming back to this later in these pages.

(090329-1)

Internet Links

Note that, for easier reading, links in the printed magazine are truncated. For the full links, please go to the project page at [11].

- [1] www.sensirion.com
- [2] www.atmel.com
- [3] www.lcd-module.de
- [4] www.national.com
- [5] www.cui.com
- [6] www.winavr.com
- [7] en.wikipedia.org/wiki/Dew_point
- [8] comprendre.meteofrance.com
- [9] www.astrosurf.com/luxorion/meteo-nu-ages.htm
- [10] http://en.wikipedia.org/wiki/Standard_temperature_and_pressure
http://en.wikipedia.org/wiki/International_Standard_Atmosphere
http://en.wikipedia.org/wiki/U.S._Standard_Atmosphere
- [11] www.elektor.com/090329



We add value to PCBs when others just sell it.




Designing Service

3D Enclosure Designing Virtual Assembly PCB Design

- One Stop Manufacturing Service
- \$10 ea. for 5pcs 4"x4" 2L
- Free Solder Mask & Silkscreen
- Free Components
- Free Assembly



 Assembly Components Pcb
Enclosures Fpcs Keypads



www.EzPCB.com Email: sales@ezpcb.com

Please Visit www.machinepier.com For Machining

nURVE NETWORKS LLC

XGAMESTATION

Powered By Atmel MEGA AVR 644
64K FLASH
4K SRAM

AVR 8-BIT

XGS AVR 8-Bit Main PCB Board.
XGS Gamepad Controller.
325+ Page Printed Manual.
Atmel AVR ISP MKII Programmer.
9V Power Supply & A/V Cable.
PC Serial Port to XGS Converter.
PC DVD-ROM.
1GB Micro SD Card + Adapter.
Bonus: eBooks on Hardware,
Game Console Design, and More!

Visit Youtube Channel: XGSDEV

THE MOST COMPLETE ATMEL MEGA AVR DEV KIT AVAILABLE!

WWW.XGAMESTATION.COM

www.elektor.com

Prototype & small series PCB specialists



PCB proto	dedicated prototype service
STANDARD pool	widest choice 1 - 8 layers
New TECH pool	100 µm technology
New IMS pool	metal-backed PCBs
On demand	all options up to 16 layers

Call us: 020 8816 7005 Email: euro@eurocircuits.com
New website - new services

ALL SERVICES

- Instant online pricing
- Instant online ordering
- Low pooling prices
- Deliveries from 2 days
- No tooling charges
- Stencil service

www.eurocircuits.com

In-vehicle CO₂ Meter

Safe(r) behind the wheel

Chris Vossen (Elektor Labs) & Thijs Beckers (Elektor Netherlands Editorial)

CO₂ itself is not really that dangerous, but it can lead to poor concentration relatively quickly. Under certain circumstances dangerous situations may arise from this, for example while driving a closed vehicle. To warn you of this a fast responding CO₂ meter was developed specifically for in-vehicle use.



Specifications

- 12 V operation (via cigarette lighter socket)
- Instantly ready for use
- Warns with indicator LEDs when CO₂ concentration is too high
- Suitable for measurements of up to 3000 ppm of CO₂

The CO₂ Meter published in our January 2008 edition continues to operate very well, so why bother to do a new design? The answer is both simple and obvious. In the previous article, we mentioned that too high a concentration of CO₂ negatively affects the ability to concentrate. And in which daily activity does the ability to concentrate play an important role? Exactly! While driving a car (excluding convertibles). We therefore wanted a CO₂ meter that was suitable for in-car use.

The 'old' CO₂ meter perfectly satisfied the requirements when it comes to its physical dimensions, but the long warming-up period and calibration phase of two hours

are of course not practical for use in a car, when you just want to start the engine and drive off.

Measuring principle

Since the long warming-up time was a requirement of the sensor that was used, there was no other option than searching for another (faster) sensor. And we found one! The ZG01C made by Taiwanese manufacturer ZyAura [1] (see **Figure 1**).

This sensor uses the NDIR measuring principle. NDIR stands for Non-Dispersive InfraRed absorption (see also [2]). This measures the concentration of CO₂ in a gas by using the fact that the CO₂ in the air absorbs infrared light with a specific wavelength of 4.27 μm . By taking a 'tunnel' of known dimensions and filling it with the gas to be measured, and using a suitable sensor and light source, the concentration of CO₂ in the gas sample can be determined quite accurately.

Since the concentration of CO₂ is (or should be) normally quite low in our intended application environment (the car), a relatively long optical path is required to obtain a suf-

ficiently accurate measurement. As a consequence, any suitable sensors are generally quite large and because of the high quality optics they contain, are also quite expensive. However, ZyAura have succeeded in manufacturing a relatively compact and affordable NDIR CO₂ sensor, which is perfectly suited for our intended use.

Intelligent sensor

The sensor is suitable for CO₂ concentrations ranging from 0 to 3000 ppm (refer to specifications), which is sufficient for the application we have in mind. The average CO₂ concentration outdoors amounts to about 400 ppm (parts per million). Values above 3000 are, certainly in a car, very undesirable and can lead the dangerous situations (see table 'CO₂ concentration and effects').

The electronics integrated on the PCB of the sensor module takes much of the work out of our hands. The chip covered with resin (presumably an ASIC) already does all the measuring and interface work and makes the measured data available via an SPI interface. In addition to the CO₂ sensor itself, the module also has a temperature sensor for

ZG01C specifications

- Measuring range : 0–3000 ppm / 0.3%
- Temperature range : 0–50 °C
- Humidity range : 0–95%
- Warming-up time CO₂ : <60 s
- Measuring interval : 7 s
- Accuracy : ±50 ppm or
5% of the measured value

 


Figure 1. The sensor PCB is already fitted with all the electronics for interpreting the measurement data.

calibration purposes, the measuring result of which is also available via the SPI bus. In fact, all we have to do is show the data from the SPI interface on a display. To do this we use a microcontroller, an ATmega88 from Atmel. Its function is to indicate the measured CO₂ concentration and temperature on a display.

Schematic and PCB layout

Largely aware of what's required for the hardware, we can take a look at the schematic (see Figure 2). Since most of the work is already carried out by the electronics integrated in the sensor module, the schematic is a simple matter.

The SPI data from the module goes via K2 and directly to the microcontroller, which subsequently shows it (via K1) on the display, and depending on the CO₂ value it will turn on one of the LEDs D1, D2 or D3. The microcontroller can be programmed in-circuit via K3. However, you have to disconnect the sensor module first, because both use the same (SPI) bus.

For the display we chose a 2-line by 8-character LCD display module with an HD44780-compatible controller, so that for driving this display you can pick a 'standard' software library off the internet. The display contrast can be set with P1.

For the power supply we started with the battery voltage from the car. The sensor electronics requires a voltage of 6 volts, which is derived from a 7806 powered from the battery voltage. The microcontroller requires a regulated voltage of 5 volts, which is generated using a low-drop voltage regulator type LP2950-50. The power

supply for the LEDs also comes from this 5 V. Diode D4 was added to protect against reversed polarity.

When designing the PCB layout the sensor PCB and LED were taken into account. Both

can be mounted on the PCB with stand-offs. (see Figure 3).

Software

The software for the microcontroller is quite

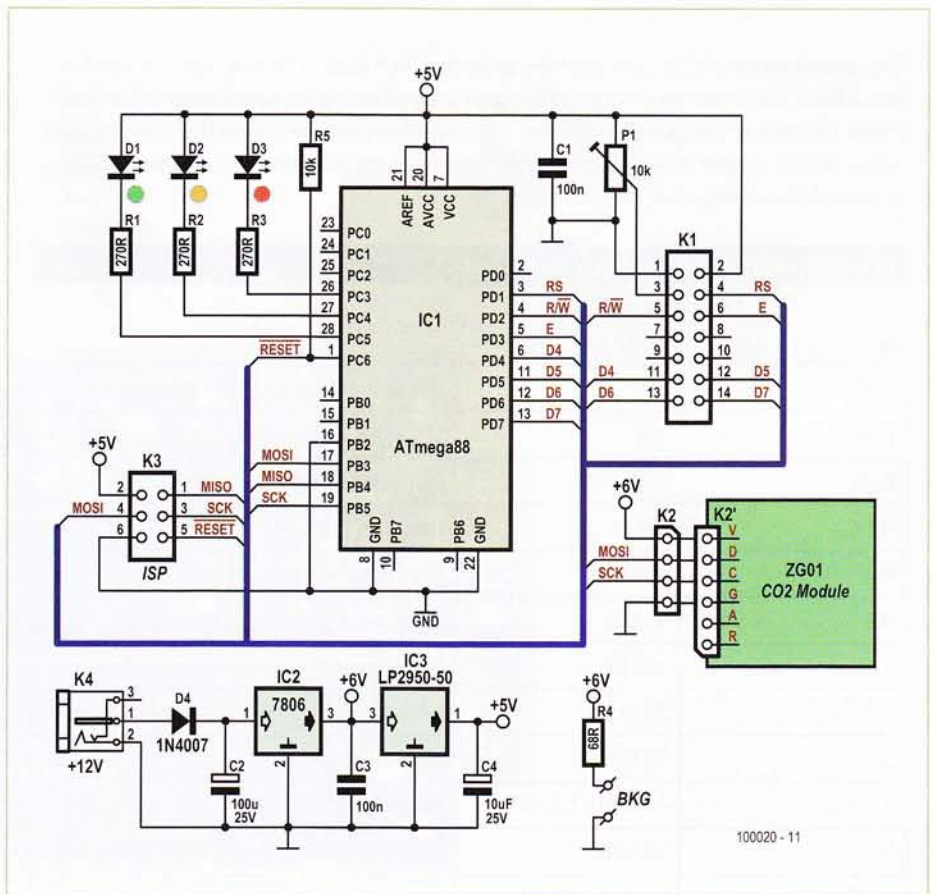


Figure 2. The schematic is very modest thanks to the integrated electronics on the sensor PCB.

CO₂ facts

CO₂ or carbon dioxide is a colourless and odourless gas which is heavier than air. The average concentration in outdoor air is about 380 ppm (= 0.0380% by volume). In cities this value is higher, typically around 700 ppm. In enclosed spaces and when there are (many) people, these values can easily be much higher. An example: exhaled air contains about 4–5% by volume of CO₂, or expressed differently, about 30 cc. When breathing about 16 times per minute that amounts to just under 30 litres per hour. In a completely sealed space of 2 m³ or 70 c.ft (small car) the concentration of CO₂ increases within 15 minutes from 0.05% (500 ppm) to 0.425% (4250 ppm). With four people in this same space this same value will be reached in only a few minutes! In the table you can see a brief overview of the number of CO₂ values and their effects.

The 'toxicity' of CO₂ is not really due to the gas proper. At high concentrations (over 2%) it dissolves easily in blood, which raises the acidity level; think of club soda or fizzy lemonade which has carbon dioxide dissolved in it to give it a 'refreshing taste'. The result is that the blood (or actually the red haemoglobin) can only absorb a limited amount of oxygen, which results in shortness of breath. The same effect is also observed during intense muscular effort and is known as acid build-up.

The concentration of CO₂ does not have to be that high to start to have a detrimental effect. Above about 800 ppm (0.08%) the sense of smell increases, which means that 'bad smells' can be noticed earlier and better. This contributes to the feeling that you find yourself in 'bad air'. Think about when entering an intensively used meeting room or a class room with poor ventilation after an exam.

CO₂-concentration by volume and effects

CO ₂ volume		Description
%	ppm	
0.038	380	World mean value (= 380 ppm)
0.07	700	Urban air, outdoors
0.08	800	Increased olfactory sensitivity
0.14	1,400	Urban air (indoors)
0.4	4,000	Max. value in classrooms
0,5	5,000	Long-term workplace exposure limit
2	20,000	Short-term workplace exposure limit
2.5	25,000	Intoxication-like effects on divers
3	30,000	Increased difficulty breathing
4 – 5.2	40,000 – 52,000	Exhaled air
5	50,000	(Onset of) dizziness and unconsciousness
6 – 8	60,000 – 80,000	Signs of paralysis
8 – 10	80,000 – 100,000	Lethal level

straightforward because of the high degree of integration of the sensor. A software library was downloaded from the internet for controlling the display. After initialising the hardware and configuring the controller as an SPI slave device, the display is cleared and the main loop waits for until it receives a frame. When the checksum of this frame is correct, the temperature and CO₂ value are shown on the display. Additionally, which LED should be turned on is also decided. If the checksum is incorrect, then the entire frame is ignored.

The sensor electronics, on its own accord, sends a data frame every seven seconds via the SPI bus to the controller, so that every seven seconds the displayed value is updated; more than fast enough for our application.

Construction and use

The assembly of the PCB is not likely to cause any problems. As usual, start by soldering the smallest (lowest) components (resistors, diodes, etc.) and finish with the largest (tallest). You can see the component placement in **Figure 4**. Using hook-up wire, solder a 4-pole connector to the sensor PCB, which will then be connected to K2. The schematic of **Figure 2** shows how this connector should be wired.

The PCB copper track layout can be downloaded from the web page for this project [3]. A kit is also available for this project, which has all the parts collected for you (see [3]). After assembly, the PCB can obviously be fitted in the enclosure which we offer with the kit in the Elektor online shop, but you are of course free to choose a housing of your own preference. Note that the enclosure is not supplied with pre-machined openings, so keep in mind when mounting the board in the housing that you need to make a few openings for the ambient air to pass.

The electronics will come to life as soon as the power supply is connected. The measured temperature appears on the display immediately. The CO₂ value requires 10 to 20 seconds of patience: the sensor needs a short warm-up period.

As will be obvious by now, the display shows the measured CO₂ concentration in ppm (and the temperature in °C). To make the readout slightly more noticeable in a car, three LEDs

 


Figure 3. Spacers are used to mount the sensor and display on the PCB. For connecting the display backlight ('A' and 'K') you can use a couple of leads trimmed from the resistors.

were added. The green LED (D1) is on when the CO₂ concentration is less than 1000 ppm and is 'normal'. The orange LED (D2) is on when the CO₂ concentration is between 1000 and 1400 ppm (elevated value) and the red LED (D3) will be on when the value is above 1400 ppm, at which point it is time to take action. Particularly when there are several people in the car, this value is reached quite quickly and easily exceeded (see also our 'test report' in last month's E-LABS INSIDE section 'CO₂ meter under test', where values in excess of 1700 ppm were no exception). Particularly during long road trips, both for holidays and business, your concentration is likely to suffer after a while as a consequence of the in-vehicle CO₂ level. While this circuit does not actively keep you awake, it will in any case monitor a potentially dangerous environment and warns you that it is time to open a window or turn up the ventilation a notch.

(100020)

Internet Links

- [1] www.zyaura.com
- [2] http://nl.wikipedia.org/wiki/Nondispersive_infrared_sensor
- [3] www.elektor.com/100020
- [4] www.elektor.com/090981

COMPONENT LIST

Resistors

- R1,R2,R3 = 270Ω
- R4 = 68Ω
- R5 = 10kΩ
- P1 = 10kΩ

Capacitors

- C1,C3 = 100nF
- C2 = 100μF 25V
- C3 = 10μF 25V

Semiconductors

- D1 = LED, 5mm green
- D2 = LED, 5mm, amber
- D3 = LED, 5mm, red
- D4 = 1N4007
- IC1 = Atmega88-20pu, programmed
- IC2 = 7806
- IC3 = LP2950-50

Miscellaneous

- K1 = 14-pin pinheader (14mm lead length)
- K2 = 4-way header
- 4-way socket for K2
- K3 = 6-pin (2x3) pinheader
- K4 = DC adapter socket, PCB mount
- LCD type PC0802LRS-AWA-B-Q
- IR module type ZG01
- Hookup wire
- PCB # 100020-1, see [3]
- Kit of parts, including sensor and LCD, Elektor order code 100020-71, see [3]
- Enclosure, Elektor order code 100020-72, see [3]


 


Figure 4. In the component overlay you can clearly recognise the space reserved for the sensor and LCD. Also keep in mind the contrast adjustment using P1.

VisiOLED

 ATM18 with colour OLED display, wireless link and RFID



Wolfgang Rudolph (Germany) and Gregory Ester (France)

It's a fascinating hardware combination, but what can we do with it? VisiOLED is a wireless door-opener featuring RFID cards for visitor identification, and visualisation using an OLED display. The whole thing is based around the ATM18 board.

For a slightly more detailed overview, take a look at the block diagram in **Figure 1**. The outdoor part of the system (situated near to the front door or front gate) and the indoor part, inside the house, employ the same printed circuit boards: the VisiOLED transceiver board and the ATM18 test board. The only difference is in how they are connected up: the outdoor transceiver board is equipped with an RFID reader and an electri-

cally-operated door latch, while the indoor board is connected to an OLED display. The indoor and outdoor stations communicate using a 433 MHz (or equivalent ISM band) wireless link.

This is VisiOLED, your doorman

The following functions are provided by the software running on the ATM18 boards. Visitors can announce their arrival at the

door using a low-cost RFID card. The RFID data are sent to the indoor unit over the wireless link. If the visitor's RFID card is recognised, an image of the visitor appears on the OLED display for confirmation. The door can now be opened remotely by pressing a button on the indoor unit. In communications between the two units the indoor unit acts as the master and the outdoor unit as the slave. The source code for the project is,

as always, made freely available and so can be used as the basis for other applications involving similar peripherals.

The RFID reader comes from the same stable as the ATM18 board, and was described in the article 'ATM18 = RFID Savvy' published in the June 2009 issue of *Elektor*^[1]. A TDL2A 433-9 transceiver (see text box) is used to send the RFID code from the outdoor unit to the indoor unit, where it is compared against a stored list of codes. If a code matches a buzzer sounds and the corresponding image is fetched from the memory card and shown on the OLED display.

Printed circuit boards

Each of the two stations requires an ATM18 test board and a transceiver board (Figure 2). The boards are populated differently in the two stations, which is why we have given two separate parts lists.

The circuit diagram of the transceiver board is shown in Figure 3. It provides all the connections between the ATM18 test board and the other components of the system. The wireless transceiver module (Mod1), the buzzer circuit (T2 and Bz1) and the FTDI cable interface (K2) are fitted in both indoor and outdoor stations. The relay for the door latch (T1 and Re1) and the RFID reader board, plus its antenna coil Ant2, are fitted only in the outdoor station. The following items are only fitted in the indoor station: the OLED module, connected at Mod2 (see separate text box); the 74HC4053 multiplexer (IC1), used to switch the ATM18's serial port signals (TXD and RXD) between the transceiver and the display module; R2 and R7, pull-up resistors that provide defined logic levels on otherwise open-circuit inputs to the display and transceiver module; and R5 and R6, which protect the 74HC4053 when an FTDI interface cable is connected at K2 to program the unit.

Construction

Populate the two transceiver boards according to their respective parts lists, and check over the boards carefully. In the outdoor unit, don't forget the wire links that run from R5 and R6 to pins 5 and 4 of K3. These are shown as white lines in the component mounting overlay on the circuit board (Fig-

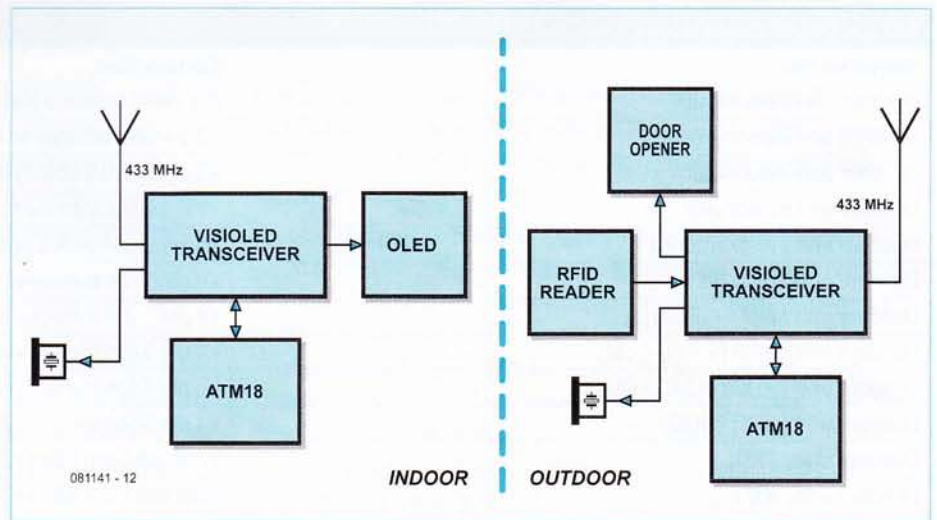


Figure 1. Block diagram of a VisiOLED installation. The outdoor unit is located at the front door, while the indoor unit can be located in any convenient position inside the house.

ure 2) and as dotted lines in the circuit diagram (Figure 3).

The ATM18 board is simply plugged into the transceiver board, mating K5 on the ATM18 board with K3 on the transceiver board. Since the transceiver board receives its 5 V supply from the ATM18 board over this connection, all three pins of JP1 on the ATM18 board must be linked together. The ATM18 board itself is powered from a mains adaptor via K1. A complete list of the necessary connections is given in Table 1.

Before use, the ATmega88 microcontrollers on the ATM18 boards must be programmed with the relevant software. As usual, the software is available as a free download^[2] from the web pages accompanying this article. Within the software the outdoor unit is referred to as the 'slave' and the indoor unit as the 'master'. The program for the slave is written using BASCOM and the program for the master in C.

The software in the master unit must be configured with the codes of the RFID cards

 


Figure 2. Both indoor and outdoor units consist of a transceiver board and an ATM18 test board. However, different subsets of the components are fitted in the two cases.

Required for:	Connection
Outdoor and indoor unit	JP1: pin 1 to pins 2 and 3 (on ATM18 board)
Outdoor and indoor unit	12 V mains adaptor to K1 (on ATM18 board)
Outdoor and indoor unit	K5 (on ATM18 board) to K3 (on transceiver board)
Outdoor and indoor unit	17 cm whip antenna to Ant1 (on transceiver board)
Outdoor unit / RFID antenna	Antenna coil to Ant2 (on transceiver board)
Outdoor unit / relay (RE)	K4 pin 1 (on transceiver board) to PC2 (ATM18 board)
Outdoor unit / buzzer (BUZ)	K4 pin 2 (on transceiver board) to PC1 (ATM18 board)
Outdoor unit / RFID (SHD)	K4 pin 3 (on transceiver board) to PD5 (ATM18 board)
Outdoor unit / RFID (DEMOD OUT)	K4 pin 4 (on transceiver board) to PD3 (ATM18 board)
Outdoor unit / RFID (MOD)	K4 pin 5 (on transceiver board) to PD4 (ATM18 board)
Outdoor unit / TXD	Wire link from R5 to K3 pin 5 (on transceiver board)
Outdoor unit / RXD	Wire link from R6 to K3 pin 4 (on transceiver board)
Indoor unit / IC1 (S1)	K4 pin3 (on transceiver board) to PC0 (ATM18 board)
Indoor unit / IC1 (S2)	K4 pin4 (on transceiver board) to PC1 (ATM18 board)
Indoor unit / button S3	K8 pin3 (on ATM18 board) to PD5 (ATM18 board)
Indoor-unit / Zoemer BZ1	K4/pen22 (transceiver-print) met PC2 (ATM18)

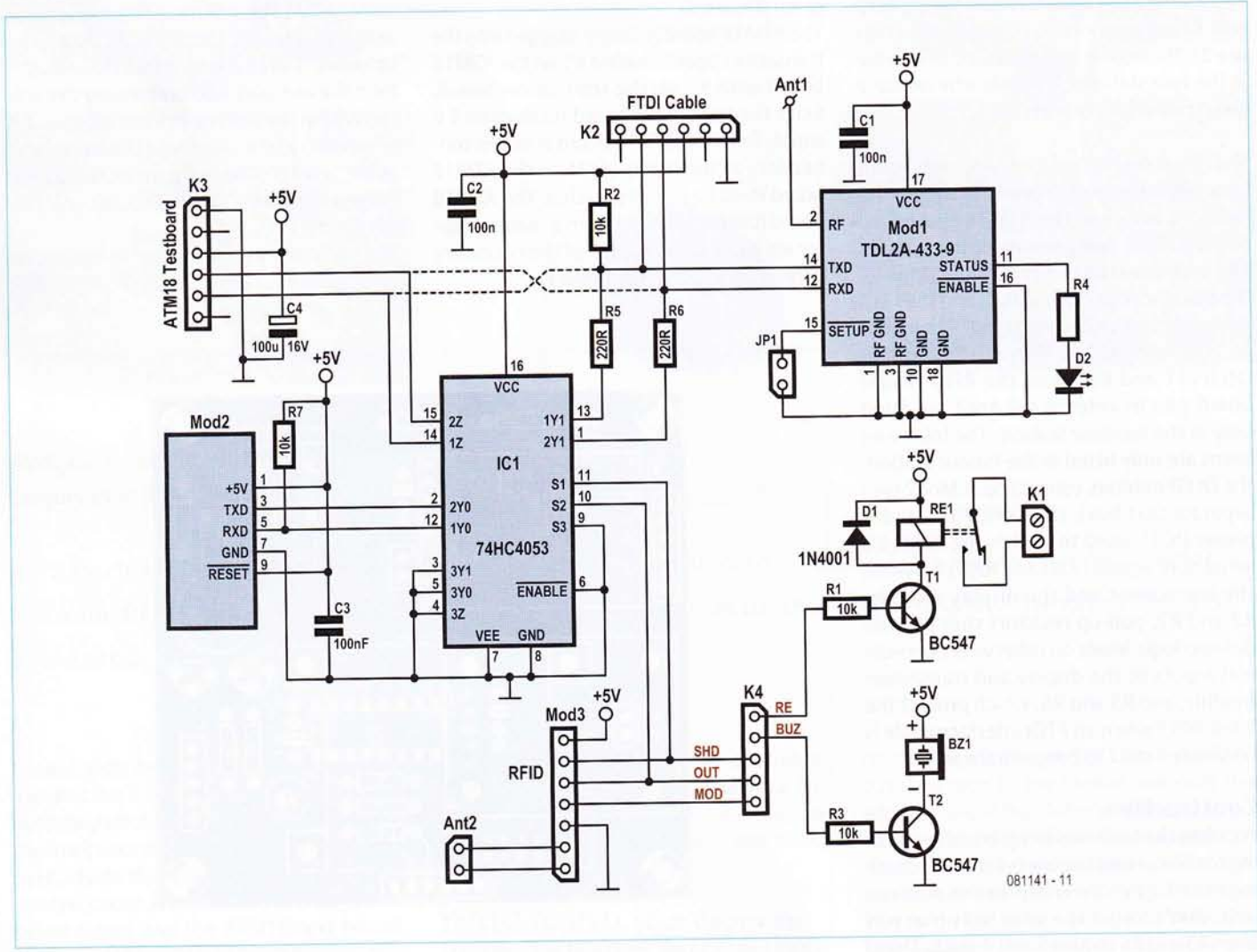



Figure 3. The main job of the transceiver board is to connect the various modules (wireless link, RFID and OLED) to the ATM18 board.

OLED: the future of light production

There are many examples of luminescence in nature. One well-known example is the glow-worm (actually a kind of beetle), which can turn its yellowish light on and off just like an (O)LED. The principle of operation of the glow-worm is biochemical rather than electrical, of course, and it can reach an energy efficiency as high as 95 %!

The first discoveries of electroluminescence in organic materials date back to 1953. Once it had been determined that certain natural polymers exhibit semiconductor properties, processes were developed to synthesise these materials, called conjugated polymers, artificially. The road was now open to manufacture semiconductors and other electronic components from plastics rather than based on a crystalline substrate.

The principle behind light-production in conjugated polymers has parallels to that behind our old friend the light-emitting diode. However, the practical development of electroluminescent displays only began in earnest in 1987, when Kodak, and shortly afterwards Pioneer, started to invest in the technology. Now OLED technology stands on the threshold of wide commercial application. According to DisplaySearch, an American market research company, turnover in OLED displays will grow from US\$ 500m in 2004 to US\$ 7bn by 2016.

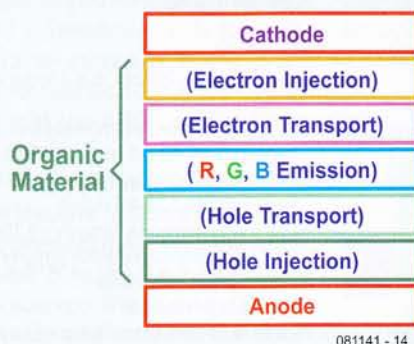

OLED manufacture

OLED displays have a simple structure built from one or more organic layers sandwiched between two electrodes. Typically the thick-

ness of the layers is around 100 nm to 200 nm. Two types of organic material are used: long-chain polymers, prepared in solution, and smaller molecules that are deposited using thermal chemical vapour deposition in a vacuum.

For so-called passive matrix displays the layers of molecules prepared in solution are deposited using spin coating, an inkjet process, or similar technique. The light emission principle of these 'polymer OLEDs' is mainly based on fluorescence. OLEDs that employ the smaller molecules ('small molecule OLEDs') also rely on phosphorescence. At voltages of between 3 V and 10 V electrons are injected into the active layer from the cathode. The material of the cathode is chosen to have a low work function (the energy required to liberate electrons from its surface). Suitable choices are metals such as barium or calcium, as well as certain fluorides. Simultaneously holes (positive charges) are injected into the organic material from the anode, which is made from a transparent material such as indium tin oxide (ITO) with a higher work function.

LCD versus OLED

The advantages of OLEDs compared to LCDs arise directly from their principle of operation. The liquid crystal material inside the LCD works like a Venetian blind, either blocking or passing the light generated by the backlight to the observer. OLED displays have no backlight: the light is produced directly in the panel. To display a dark pixel, an LCD has to block its backlight; in an OLED display, the pixel is simply turned off and then draws no power. OLEDs are therefore much more energy efficient than a fully backlit LCD, especially if (as is often the case for video material) the images to be displayed are largely dark. OLEDs have better contrast, some reaching ratios as high as 1 000 000 to 1. Since there is no backlight, an OLED module can be very thin. The low power consumption and economy in materials make them environmentally friendly, and the wafer-thin polymer layers do not contain any harmful substances.

Disadvantages, however

The materials used in OLED panels are extremely sensitive to moisture and oxygen and must therefore be protected behind a glass cover. Also, not all colours of light are produced with the same efficiency: this means higher current consumption and shorter lifetime, and is an obstacle to the widespread use of large full-colour panels. The lifetime of today's OLED panels is no match for that of an ordinary LED: to put this in perspective, however, Sony claims that its first OLED television has an operating life of 30 000 hours before the panel reaches half its original brightness, which corresponds to four hours of viewing every day for some twenty years.

to be accepted along with the address of the image corresponding to each one: the software download includes instructions on how to do this, along with screenshots. The datasheet for the OLED panel includes the necessary information on how to store images on the SD card in the module. All that is needed is an SD card adaptor for

your PC or laptop and a program that you can download for free: see the OLED module manufacturer's website^[3] for further details as well as the datasheet itself.


It is possible to configure the Radiometrix transceiver module before use with the help of a serial-to-USB adaptor cable (or 'FTDI

cable') 080213-71^[4] connected at K2. Configuration is essential if, for example, several transceivers are to be used in close proximity to one another. Normally this will not be the case, and the default configuration of the module will be perfectly satisfactory and no programming is necessary. On the other hand, if you do wish to program the

μOLED-128-G1

This compact low-cost OLED display module uses passive matrix technology. The module includes an embedded graphics controller to provide 'stand-alone' functionality. Two software platforms are available: the serial command platform (SGC) and the 4D Graphics Language (4DGL) platform.

 The SGC module that we have chosen for this project can be used



as a slave device connected to a suitable host (see accompanying figure).

The protocol used on the serial interface is very simple, with each command consisting of one or more bytes.

μOLED-128-G1 features

- 128 by 128 pixel resolution
- 256 or 65k colours
- 1.5 inch diagonal, module size 45.5 mm by 33.5 mm by 6.3 mm
- Active screen area: 27 mm by 27 mm
- Viewing angle: almost 180 °
- Simple five-pin interface
- Operating voltage 3.6 V to 6.0 V
- Current consumption typically 40 mA at 5 V
- RS-232-like interface (0 V/3.3 V levels) with automatic baud rate selection (300 baud to 256 kbaud)
- Two software versions: serial command platform or 4D Graphics Language

COMPONENT LIST

Transceiver board # 081141-1 with RFID (outdoor)

Resistors

R1,R3 = 10kΩ
R4 = 1kΩ

Capacitors

C1,C3 = 100nF
C4 = 100μF 25V radial

Semiconductors

D1 = 1N4001
T1,T2 = BC547B
D2 = LED, red, low current, 3mm

Miscellaneous

Re1 = 5V relay with 250VAC/5A contacts (e.g. Omron type G6D-1A-ASI 5DC)
Bz1 = 5V piezo buzzer (e.g. Megacera type CPM121A0A)
Mod1 = 433MHz data transceiver, Radiometrix type TDL2A-433-9 or equivalent
Mod3 = RFID module # 080910-91 from Ele-

ktor Shop or www.elektor.com/080910

Ant1 = wire antenna, length = 170mm (6.7 in.)

Ant2 = RFID antenna coil (160 turns 0.2mm / AWG#31 ecw, 23mm diam., L = 780μH)

JP1 = 2-pin pinheader with jumper

K1 = 2-way PCB terminal block, lead pitch 7.5mm (0.3 in.)

K2,K3 = 6-pin pinheader

K4 = 5-pin pinheader

PCB # 081141-1 from Elektor Shop or www.elektor.com/081141

ATM18 Test Board # 071035-92 with controller module -91 (Elektor Shop or www.elektor.com/071035)

Transceiver board 081141-1 with OLED (indoor)

Resistors

R2,R3,R7 = 10kΩ
R4 = 1kΩ 5%
R5,R6 = 220Ω

Capacitors

C1,C2,C3 = 100nF
C4 = 100μF 25V

Semiconductors

T2 = BC547B
D2 = LED red, low current, 3mm
IC1 = 74HC4053

Miscellaneous

Bz1 = 5V piezo buzzer, e.g. Megacera type CPM121A0A
Mod1 = 433MHz data transceiver, Radiometrix type TDL2A-433-9 or equivalent
Mod2 = OLED display module, 4D Systems type μOLED-128-G1 (SGC)
Ant1 = wire antenna, length = 170mm
JP1 = 2-pin pinheader with jumper
K2,K3 = 6-pin pinheader
K4 = 5-pin pinheader
PCB # 081141-1 from Elektor Shop or www.elektor.com/081141
ATM18 Test Board # 071035-92 with controller module -91 (Elektor Shop or www.elektor.com/071035)

TDL2A 433-9 transceiver module

The TDL2A from Radiometrix is a 9600 baud half duplex multichannel wireless module for use in the 433 MHz ISM (license-free) band. It is designed to emulate a simple serial cable wirelessly, offering automatic synchronisation, bit balancing and error detection, as well as automatic noise squelch in the absence of an RF signal.

The TDL2A can be set to one of eight different addresses, and can be programmed to operate on one of five preset frequencies within the 433 MHz band. The channels used are non-overlapping, and so several TDL2A wireless links can be used simultaneously.

TDL2A 433-9 features

- Default operating frequency: 433.925 MHz (ISM)
- Modulation: 16 kbps bi-phase FSK
- Power supply: 5 V at 28 mA (transmitting), 22 mA (receiving)
- Transmit power: +10 dBm (10 mW)
- Sensitivity: -107 dBm (for 1 % BER)
- Adjacent channel rejection: 65 dB at ±320 kHz
- Receiver blocking: 84 dB
- 32 byte data buffer

transceiver module, you will find a description of the various available settings for ID codes and channels on page 6 of the Radiometrix datasheet [5]. Support from Lextronic [6], the French distributor of both the 4D Systems OLED module and the Radiometrix wireless module, has been very helpful in the development of this project.

Operation

The functions provided by the VisiOLED system were described in the introduction to this article. Communication between slave and master to implement these functions uses a very simple protocol.

When the slave reads an RFID card it sends the ID code to the master and then switches its transceiver to receive (or 'listen') mode. The master receives the ID code and looks through its stored ID code list. If the received code matches an entry on the list it displays the corresponding stored image on the OLED panel and sounds the buzzer (the 'doorbell'). Simultaneously it sends the ASCII character capital 'A' to the slave, which in turn sounds its buzzer, indicating to the visitor that the RFID card has been recognised.

If button S3 on the ATM18 board in the master unit is now pressed, it will send the ASCII character capital 'B' to the slave. When this character is received the slave software sounds the buzzer and activates the door latch relay Re1 for 20 seconds. The slave then returns to listen mode.

And that is essentially all there is to it. The software has deliberately been kept simple with space for you to make your own extensions and modifications. Devious readers will have spotted immediately that it is possible to build a master unit based on the design in this article that allows unauthorised opening of any door controlled by a slave unit. This can be prevented by modifying the software to use a more intelligent protocol than just the character 'B' to control the opening of the door. Also, the slave can be protected from casual hacker attack by switching it off when leaving the house. Furthermore, since identification is based solely on possession of an RFID card, the

 


Figure 4. The board for the outdoor unit, fitted with wireless link and RFID modules.

system offers no protection against the use of stolen or cloned cards.

An advantage of the wireless connection is that it is possible to use one slave with more than one master, allowing the front door to be opened from several different places within the house.

(o81141)

Internet Links

- [1] www.elektor.com/080910
- [2] www.elektor.com/081141
- [3] www.4dsystems.com.au/prod.php?id=78
- [4] www.elektor.com/080213
- [5] www.radiometrix.co.uk/dsheets/tdl2a.pdf
- [6] www.lextronic.fr

 



Figure 5. The transceiver board is connected as an extension to the ATM18 board.

Colossus — the Rebuild

A giant digital computer that uses valves as its main logic elements

By Charles Coultas (UK)

 Colossus was a digital computer that contained 2400 valves and ran its programs as fast as a modern computer. It was designed in 1943 and made a significant contribution to ending World War 2. This is the story of that machine and the rebuilt version that you can visit at Bletchley Park (UK). How did Colossus come about, and how were valves made into computing elements?



During World War 2 Enigma provided a high level of security for battlefield messaging but Hitler wanted something much more secure, an encryption method that couldn't be broken by clever cryptanalysts. (High Command never knew that Enigma had been broken, they were convinced it was secure.) The machine they chose was called the Lorenz SZ42. It had 12 code wheels (see **Figure 1**), similar to Enigma's three but each wheel had a number of tabs that could be folded in or out. The total number of tabs was 501. In very simplified form, each message character was scrambled by these tabs, then the wheels moved on exposing the next set of tabs. The wheels didn't all move together. This scrambling process was actually the Exclusive-Or function (see later). It was the job of Colossus to find the starting position of these 12 wheels. The message was now effectively randomised and unintelligible — and sure, it was transmitted by radio.

As an aside, at Elektor Live! 2009, Messrs Marc Simons and Paul Reuters demonstrated their Enigma-E kit based on PIC microcontroller technology — the legend lives on!

Secure — in theory

At the receiving station the process was reversed: each scrambled character was exclusive-or'ed (XOR'ed) with an identical set of 12 wheels with the same tab settings. The resulting unscrambled text was the original message (if you exclusive-OR twice, you finish up

with the original). The receiving station had to know the tab settings in advance of course; these were distributed by highly secure manual means.

This was pretty secure because it was virtually impossible to guess the settings of the wheels. There were strict operating procedures which limited the length of each message, and several other things to make decryption virtually impossible. You might be thinking that letter frequency analysis could lead to a solution but letters were not converted to the same corresponding code letter each time. The method was almost a One Time Pad which is unbreakable (Google it: Wiki One Time Pad).

But on the 30th of August 1941 a German operator sent a long message to a High Command Post, probably in Vienna or Athens. The messages all began with a 12 character identifier (technically known as The Identifier), something like MESSAGE NO 4. He sent his 4000 character message via his Lorenz machine. But the reply came back over the air "Didn't get that, send it again". Of course, all messages were in German.

Breaking a very important rule, both parties reset their machines to the same initial state and the sender retyped his message. He was obviously fed up by this process because he abbreviated some words and made a few mistakes. This nullifies the One Time Pad aspect, allowing analysts to break into the code and possibly solve it.

A British listening post at Knockholt (in Kent) received both messages and the astute operator realised that it was probably the

same message (nearly) again. The results were rushed to Bletchley Park where analysts set to work on it. To have two essentially different messages encoded with the same key was a fantastic gift and Bill Tutte worked out the logical structure of the machine that had encrypted the message.

From this the first Colossus machine was designed and built. It got its name from its high level of complexity. The Mk1 version had 1500 valves and numerous relays and uniselectors. Its sole purpose was to help work out the wheel tab settings — Colossus didn't decode the encrypted messages, that was done on another machine called Tunny pictured in **Figure 2**. A full description of Colossus and the theory of this type of encryption would take up this whole magazine, so please refer to the references at the end, they will point you to full and interesting descriptions. The rest of this article will concentrate on using valves as computing elements.

Into technology

The main reason for starting work on Colossus was to store a possible key, all 501 bits of it, electronically. Previous methods used two paper tapes running side by side in a machine nicknamed Heath Robinson due to its weird appearance and complexity. One tape contained the encrypted message, the other contained a tentative key. These two tapes ran at high speed and valve/relay logic did statistical analysis on the resulting data stream. The problem was speed. To run the tapes fast enough to make code-breaking possible in a reasonable time, high speeds were needed, in excess of 1000 characters per second. The results were not good. Tapes broke and keeping the two tapes synchronised was a real problem.

A brilliant engineer at the Post Office had a bright idea. Tommy Flowers had been experimenting with valves (as part of the telephone network) and he saw a way of storing the possible key electronically, in a form of memory. Only one paper tape (the message) would then run and the electronically stored key would be accessed using valves. This promised to give enough speed to make the whole task feasible (Colossus runs at 5000 characters per second). The whole project was highly secret of course. Churchill was so impressed that he made unlimited resources available.

Critics of Flowers warned that valve failure would be so great that the machine would never work. But Flowers knew otherwise, by never switching the filaments (heaters) off, very high levels of reliability could be achieved.

Heater energy worries

The rebuild of the Colossus was started in 1994 by Tony Sale. In 1943 the engineers working on Colossus kept the valve heaters on as long as possible, 24 hours a day, 7 days a week. Tony Sale knew this but the thought of several kilowatts day and night was a worry. His solution was to use a large rotary transformer driven by a motor (Google: Variac). This applies the heater voltages (4 and 6.3 volts) very slowly, over a period of a couple of minutes. Similarly, the heaters are powered down by a reverse process. This technique has stood the test of time with very few valve failures over several years. It is the sudden heating that causes heater failure in valves.



Figure 1. The coding wheels in a Lorenz machine were a wonder of precision metalworking.

The 12 wheels with their 501 tabs are simulated by 501 valves called thyratrons. These are gas filled and once conducting they will stay in that state until triggered off by pulling the anode Low and extinguishing the conduction ('quenching'). They are like a single valve flip-flop. Unfortunately the heaters of these need 4 V at 1.4 A. This gives 2.8 kilowatts just for the heaters of the thyratrons! These 501 thyratrons are arranged in 12 loops to simulate the 12 wheels of the Lorenz machine. Complicated circuits drive these in exactly the same way as the Lorenz wheels; see **Figure 3** for 1 of 12 controllers — 1 for each wheel. And this is where some of the programmability of Colossus comes in: the starting point of each wheel simulation can be changed, either by hand or automatically by Colossus itself. In effect the machine will automatically search for wheel start positions that seem to give a better match to the key being tried. But how did valves become logic elements?

From amplifier to logic element

Valves were always intended to be analogue amplifying devices. With just a cathode and an anode, we have a thermionic diode. If the anode is more positive than the cathode, current will flow. But if the cathode is more positive than the anode, no current will flow. Add a fine grid of wires between the anode and cathode (called the control grid) and we have the triode. This grid controls the current flow between cathode and anode. Apply a varying voltage to the grid and an amplified version of this flows as a current in the triode. Now comes the clever bit. Tommy Flowers was a dab hand with valves and he knew all about valves with more electrodes than just cathode, grid and anode. I would guess that he woke up one morning and realised that you didn't have to use the grids for the purpose they were designed for. A pentode has two extra grids between the cathode and the anode: it has a control grid, a screen grid and a suppressor grid. The latter two grids are to improve the amplify-



Figure 2. Little known, this machine called Tunny did the actual decoding of Enigma-encrypted messages.

ing characteristics of the valve but Flowers used them all as control grids. If you keep any one of these grids negative with respect to the cathode, it doesn't matter what you do to the other grids, no current will flow. It is rather like a NAND gate – all three grids have to be positive to cause the anode to pass current. In other words, any grid being Low (negative) will cause the valve to cut off. We have a logic element. (I have simplified this process somewhat.) One circuit that is used very many times in Colossus is the Exclusive-Or circuit (XOR). Remember that the function of Colossus was to detect the subtle key settings on the 12 wheels of the Lorenz machine and this involved making many comparisons. “Does the current character on the input tape match this part of the key” for example. The XOR function produces no output if its two inputs are

the same. You might like to try to design such a circuit. Let's say that a '1' input is a positive voltage and a '0' input is a zero voltage. If both inputs are '1' then the output is '0'. If both inputs are '0' then the output is '0'. But if either input differs from the other, the output is '1' – a true XOR function.

Figure 4 shows one of the XOR circuits from Colossus. The actual XOR function is done by V1 and V2. V3 and V4 are an output buffer. It works as follows: each input is made up of two signals, A and B as shown in the drawing. A and B are always opposite in polarity. If A is positive, then B is negative. The actual voltage levels are plus and minus 80 volts, a hangover from the days of telegraphs and teleprinters. They are a differential pair, and remember, this is only one input. To simplify your understanding how the XOR works assume that if any grid of the valve in question is negative with respect to its cathode, then that valve will not conduct, it will be cut off and its anode voltage will rise. If all grids are positive with respect to the cathode, that valve will conduct and its anode voltage will fall.

Look at V1. One of its grids is driven by I/P1 A line. Another of its grids is driven by I/P2, A line. Thus for V1 to conduct, I/P1 A must be a high voltage, as must the A line of I/P2. Now what does this mean about inputs 1 and 2? Well, it means that both A's of inputs 1 and 2 are High. In other words both inputs 1 and 2 are in the same state, A=80 V and B=-80 V, and V1 will turn on. If either A of I/P1 or I/P2 is Low, at -80 V, V1 will not conduct and V1's anode will rise. Now look at V2. Exactly the same situation exists but this time with the B inputs of I/P1 and I/P2. If both B lines are High, it means that both inputs 1 and 2 are in the same state, with A=-80 V and B=+80 V. If both B lines are at +80 V then V2 will turn on and its anode voltage will fall. If this seems complicated then just keep going over the various states, it is really quite logical.

Notice that the anodes of V1 and V2 are tied together. If they are both off (not conducting) then their anodes rise, pulled towards +200 V by the 68 kΩ resistor, causing the control grid of V3 to rise above its cathode voltage, and V3 conducts, pulling its anode Low. But if the anode of V3 goes Low, the control grid of V4 also goes Low, causing V4 to stop conducting, and its anode goes High.

To summarise: if I/P1 and I/P2 both have their A lines High at +80 V (and this automatically means that their B lines will be Low at -80 V) then V1 will turn on. If the situation is reversed and both B lines are High, then V2 will turn on. If either V1 or V2 turns on, then the anodes of both V1 and V2 will go Low. V3 will turn off allowing the B output line to go High (+80 V), V3 going off will force V4 on and output line A will swing Low. So if both inputs 1 and 2 are the same, output line A will be Low (-80 V) and output line B will be High (+80 V). If the two inputs are different, output line A will be High and B will be Low. Exclusive-OR using just two valves! V3 and V4 are simply to buffer the output. These signals can be used in many different ways inside Colossus.

The resistors are potential dividers to ensure that the valves are comfortably on or off, well away from any doubt about what logic

level is being represented. A simple yet elegant solution to quite a complicated problem. You might like to try designing this using transistors.

This explanation is simplified somewhat, you can't make each grid act as a control grid without careful biasing. But this circuit diagram is a real part of Colossus. Notice that the screen grids of V1 and V2 are at +100 V, which ensures that they don't hold the valve off. In some other parts of Colossus the screen grids are also used for logic purposes. You might notice that the screen grids of V3 and V4 are near zero volts and this would suggest that the valves could not be turned on. But look at the cathodes of V3 and V4, they are tied to -100 V and this means that the screen is in fact 100 volts above the cathode voltage so the screen grid will not stop the valve being turned on.

You will see a three pole jack socket on the diagram. Several such sockets are mounted on a patch panel, they allow an operator to interconnect signals using flexible patch cords (as were used in telephone exchanges in those days). V1 and V2 are EF37A, V3 and V4 are 6V6 (later to become very popular in guitar amplifiers).

The valve with most electrodes used in Colossus is the 6K8G, it is a double valve with one cathode, two anodes and five grids. It is used in the control circuit for each ring of thyratrons (in the front row, middle of Figure 3) — a very complicated circuit. You can Google on '6K8G datasheet'. A good description of pentode valves can be found at [1]. Other valves used in Colossus included types EF36, EF37, EF37A, 6J5, 6V6, 6K8, 807 and GT1C.

At the end of the war ten Colossi were operating at Bletchley Park with two more nearing completion. Churchill had them dismantled (although another two about to be delivered went to GCHQ).

Famous last words

Tony Sale masterminded and initially funded the Colossus rebuild. Some twenty other retired or part-retired engineers helped him with the rebuild. Tony's website [2] contains interesting information. Tony who had the idea of rebuilding this magnificent British computer in the first place must have the last word: "I feel very privileged to have met Tommy Flowers before he died in 1998 and to have had the opportunity to recreate his wartime masterpiece, the Colossus computer. The rebuild was started in 1994 and phase one was completed in 1996, the 50th anniversary of the American ENIAC computer. It just made the point that Colossus was the first in 1944 and was British. Because Colossus was kept secret until the 1970s the Americans had got away for far too long with the myth that ENIAC was the first. Now computer history has rightfully been corrected."

Thanks to Bob Alexander (on the rebuild team) for his help with the XOR circuit diagram. You can see Colossus at The National Museum of Computing [3]. Much more detailed information on Colossus and Lorenz can be found at [4].

(100130)

 


Figure 3. The valve equivalent of a single Lorenz wheel.

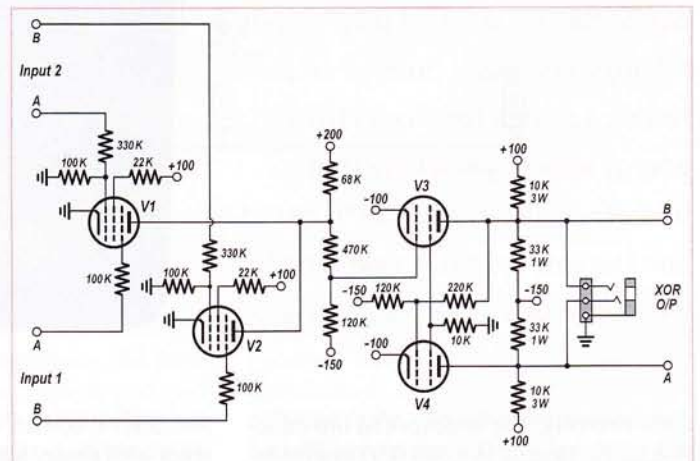


Figure 4. Typical Colossus XOR circuit based on panel J11.

Internet Links


- [1] <http://en.wikipedia.org/wiki/Pentode>
- [2] http://www.vectorsite.net/ttcode_09.html#m3
- [3] <http://www.tnmoc.org>
- [4] <http://www.codesandciphers.org.uk/lorenz/fish.htm>

Low-cost Electric Vehicle Charge Station

A coin operated kWh vending machine

By Miguel Martín Ballbé (Spain)

 The acceptance of electric cars seems to be hindered by a general lack of stations where you can charge your battery just as you would 'fill up' at a fuel station, but taking some more time, of course. Here's a design for an electrical energy vending machine that's operated with coins. It's PIC based and the software was developed with Flowcode.



Until recently, the widespread introduction of the Electric Vehicles (EV) as a mainstream option ran into two major obstacles. First, there's the higher price (Tesla Roadster: 100 k\$; Mini-e: 50 k\$; Reva Microcar: 12 k€) which does not yet balance the lower running cost compared to an ICE (internal combustion engine) vehicle. The other problem is related to EV's limited range (typ. 100 km / 60 miles) compared to the ICE cars, and the need for an AC power outlet to charge the batteries.

The latter is serious — nobody wants to be stuck with empty batteries during the daily commute. However there are some things to consider:

1. the daily to commute distance (home to work), is typically less than 60 km (40 miles);
2. there are AC power outlets (almost) everywhere, far more than gas stations;
3. the cost per kilometre/mile is about one third compared to ICE, because the performance of an electric motor is about

85% while ICE performance is about 30%, where most of the energy is dissipated as heat by the exhaust, radiator, clutch, gearbox and brakes.

Installing public AC power outlets close to, or on, parking places is relatively simple, and seems to require only a small investment. EV charging stations can be installed in or near places like restaurants, shopping centres, motorway service areas, municipality parking areas, train stations and so on. For example, there are big shopping malls

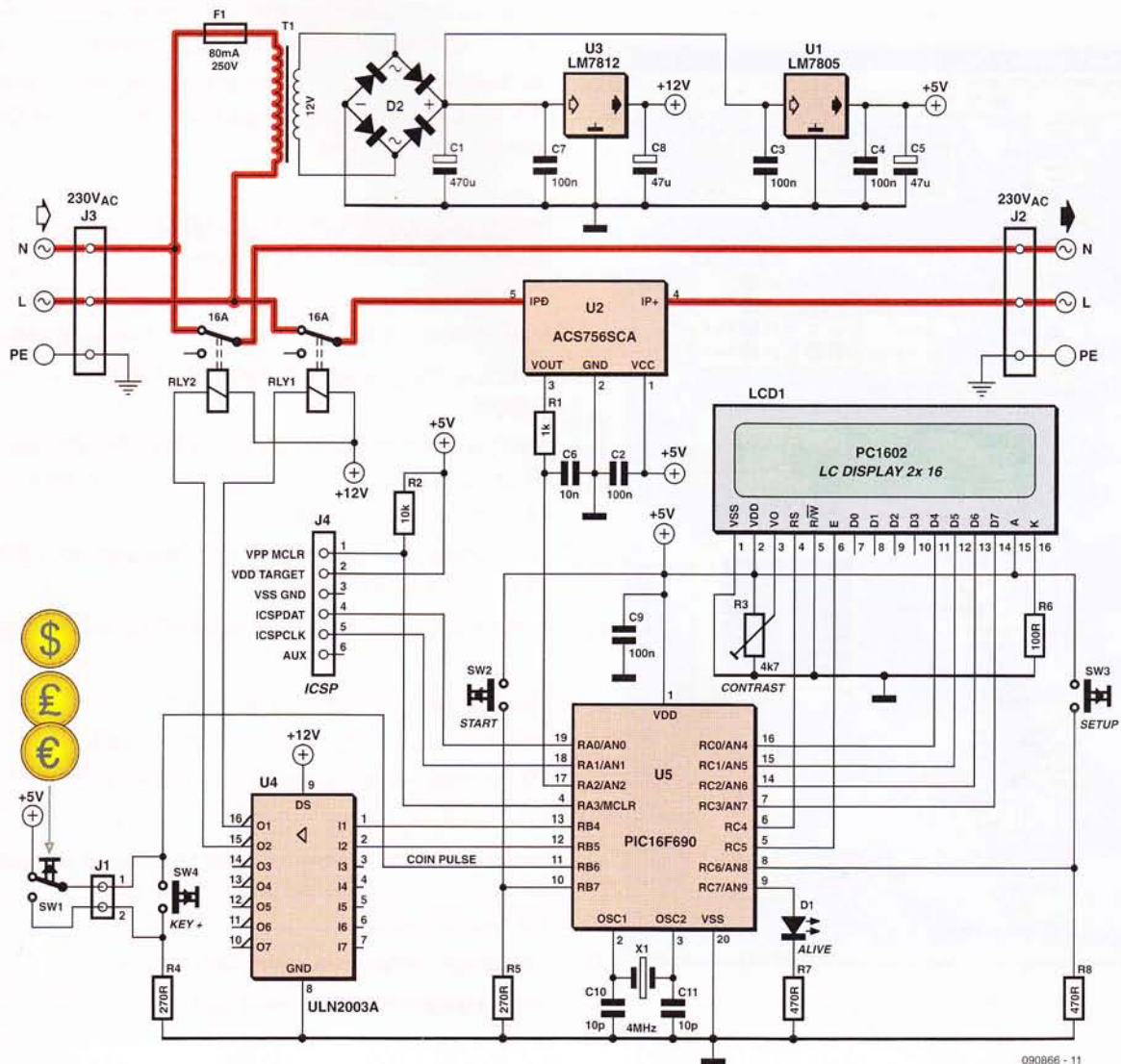


Figure 1. The EV Charge Station schematic.
Be careful with all lines, components and connections carrying live AC – they are highlighted in red.

with underground parkings. The proprietors' interest in installing EV charging stations should be not the immediate revenue, but the time the EV owners could spend there while charging ("shop till you drop"). Basically the same example applies to restaurants, roadside diners and cinemas with their own parking areas. But the energy has to be paid for, and that's where a cost effective EV Charge Station can be useful. To set up a coin operated EV Charge Station, all that's needed is a simple little coin unit in which a switch closes briefly with every euro (pound/dollar) coin accepted. Next, a circuit should start to

measure the current flow, calculate the energy 'sold' in kWh, and cut off the supply according to the rate set (by you).

Design requirements


To allow the use of a standard coin-operated vending unit the system has to be able to measure the AC current flow when an EV is being charged. The system will turn the charger on after at least one coin is inserted, and count the total number of coins to compute the equivalent energy in kWh to be supplied to the customer. Measuring the average current flow per second, the system can calculate the amount of energy (in kWh)

delivered to the EV (kWh is the standard unit for billing electricity). The system turns the charger off when the energy supplied equals the amount paid for by coin insertion.

Circuit description

Let's have a look at the schematic in **Figure 1**. When AC power is present, a classic power supply based on 7812 and 7805 regulators delivers 12 V and 5 V DC. The 12V supply is used to energise the coils of relays RL1 and RL2. As the 5 V DC ramps up, the PIC MCU starts running its firmware. There is a small delay provided by the POWERUP-TiMeR set in the config BITS.

The Flowcode macros

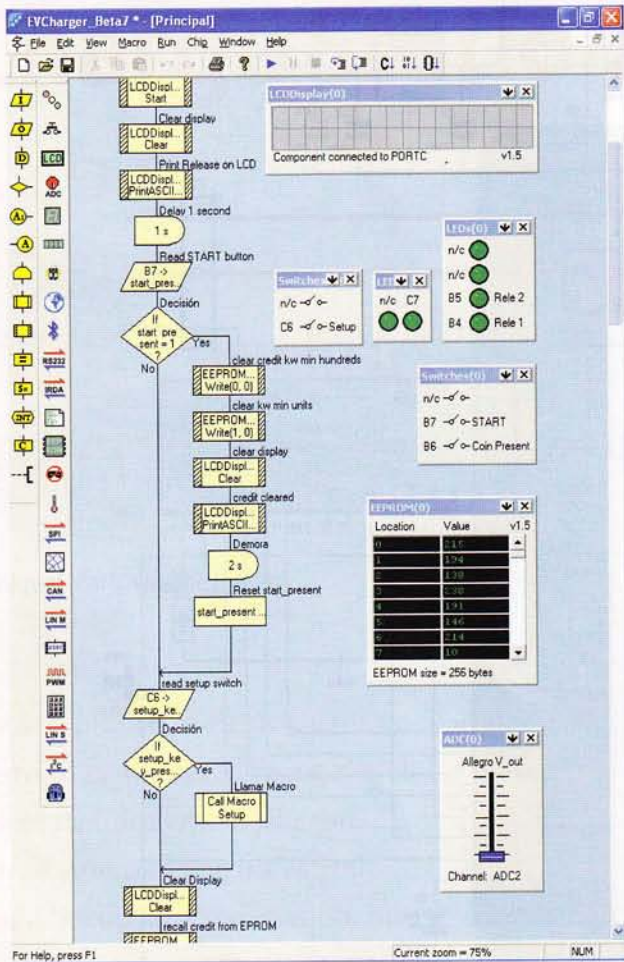

Assuming an EV is charging at 10 A_{rms} and the current is sine shaped (largely depending on the load!) then $I_{max} = 10\sqrt{2} = 14.14$ A.

The Allegro device's $V_{out} = 2.5 V \pm (40 \text{ mV} \times 14.14 \text{ A}) = 3.0656 \text{ V}$ max. ($\approx 627 \text{ ADC}$) and 1.934 V min. ($\approx 396 \text{ ADC}$) (due to alternating direction of current flow).

Peak_V_{out}_ADC: $\text{ADC}(V_{max}) - \text{ADC}(V_{min}) = 627 - 396 = 231 \text{ ADC}$, this gives the amplitude of AC component in V_{out}.

Scale multiply x10 for better resolution: (8-bit PIC: limited maths!)

Peak_V_{out}_ADC = Peak_V_{out}_ADC x 10 = 231 ADC x 10 = 2310 (integer).

Peak V_{out}_mV = $(\text{Peak_Vout_ADC} / 1024) \times 500 = (23100 / 1024) \times 50 = 1127$

231 ADC = 1.127V = 1127 mV

Peak_current_A: $\text{Peak_Vout_mV} / 40$. Peak_current = $1127 \text{ mV} / 40 \text{ mV} = 28 \text{ A}$ (= 14 + 14 A)

Peak_current_A = Peak_current_A/2, i.e. $28/2 = 14 \text{ A}$

Scale multiply x 100 for better resolution:

Peak_current_A: $\text{Peak_current_A} \times 1000 = 14000$

RMS_current = $\text{Peak_current_A} / 141 = 14000 / 141 = 99$ (9.9 A)

$14/1.41 = 9.9 \text{ A}_{rms} = I_{rms}$

This yields the RMS current multiplied by 10 for better accuracy.

The 'second' macro

Calculate the RMS current and produce kW/min:

- Peak_current: $\text{ADC}(V_{max}) - \text{ADC}(V_{min})$

Once the client inserts coins and pushes the START button, SW2, The PIC sets RB4 and RB5 high, causing the two driver stages in the ULN2003 to pull their open-collector outputs ground, which causes the relays to activate. The Allegro ACS756SCA (U2) measures the current flowing to the EV, and generates a V_{out} signal that's proportional to the instantaneous current passing effectively from the AC power outlet into the EV.

The MCU, a PIC16F690 (U5) keeps track of the energy passed to the EV, and updates the display to show to the user how much energy he or she has 'pumped' into the EV. When the energy supplied reaches the value paid for, the PIC de-activates the relay and returns to its initial state.

The resistor in series with the backlight LED in the LCD module keeps the standby current low, at the cost of reducing the light output somewhat. Current consumption of the cir-


cuit proper is about 30 mA at 12 V input in standby, and 150 mA when charging.

Software and calculations

Flowcode V3 for PIC Micros was used to develop, simulate and compile the program. The .fcf file is available free from the Elektor website.

The Macro 'Main' is summarized below. Print release on LCD. If the START button is pressed, reset the credit value stored in EEPROM (this allows the owner to clear remaining credits). Copy credit value stored in eeprom. This makes possible to resume charging in the event of a power failure, recalling the credit data. Display 'enter coins and press START'. Read input switch Coin from the coin validator.

 Customer credit is increased with every coin. When the customer has inserted the coins and plugged the EV, he/she can push



- Peak_Vout: (convert from ADC to mV)
- Delta_current: Peak_mV/40
- RMS_current: Delta_current/2
- Reset min. max. values to 512 (prepare for next measurement cycle)

Calculate W/s:

- W/s: RMS_current(Amps) x 230 V (or AC grid voltage defined in 'setup' macro)

- instead W_s= RMS_current x 23 = 99 x 23 = 2277 W/s (RMS_current was multiplied x10)

Show in LCD RMS_current (divided by 10) and remaining credit in kW/min.

(Aside) counting in kW/min gives the charger a 'fuel pump' feel so you can see the initial credit decreasing slowly. Remember, 1 kWh = 3.6×10^6 Ws = 60 kWmin.

Calculate W/s

- Carry_W/s= W/s + Carry_W/s

- if carry_W/s > 60000 then kWmin= kWmin+1; and carry_W/s= carry_W/s - 60000

- if kWmin >= 6 then subtract 1100 Wh from credit and set kWmin = 0

- Credit= credit - 1

- then go to macro 'update LCD'

- return

Compare credit, IF credit <= 0 then switch relay off and goto init.

return

Let's suppose an EV draws 10 A, and the user has paid effectively for

6 kWh i.e. 360 kWmin)

power= 10 A x 230 V = 2.3 kW

time= 1/2.3 kWh = 0.434 hours = 26 minutes. (i.e. 1 kWh is transferred every 26 minutes)

The system measures I_{rms} every second. $I_{rms} = 10$ A

Power = $I_{rms} \times 230$ V = 2300 Ws

carry_W/s will reach the value 60000 every 26 seconds (60000 Ws / 2300 Ws = 26)

60000 Ws = 1 kWmin and 60 kWmin = 1 kWh

Every 26 seconds kWmin will decrease one unit, from 360 downwards.

After 360 x 26 seconds = 9360 seconds = 156 minutes (shopping done ☺), the relays will switch off.

The 'set-up' macro

A setup facility is provided to allow the owner to adjust the system to the voltage present in the installation, to calibrate the accounting of energy, and to change the kWh vending price.

Set-up is entered when the system boots while switch 'setup' is pressed.

The Coin switch doubles as '+'; Setup doubles as '-'; Start doubles as 'confirm'.

The AC grid voltage, price and calibration are stored in EEPROM for use in the macro 'main'.

The 'finish' macro

This clears the LCD and switches off the relays.



the START button and the relays close. Even Top Gear's Captain Slow should be able to do this.

Credit = coin credit x 6 x 60. i.e. 6 kWh; however the internal unit is kWmin (1 kWh = 60 kWmin).

If credit > 0, START charging after 30 seconds, even without the user pressing START. This is to resume charging in the event of a power failure.

The program has a loop to take 2000 (or 'calibration number') measurements of the V_{out} signal from the current sensor. The actual value will be compared and max. and min. values will be saved. The output of the ACS756SCA is linear, depending on the current flow, so knowing V_{out}, implies knowing the instantaneous current value (IP).

The Allegro's V_{out} is V_{cc}/2 when I_p = 0. In terms of the ADC (10-bit) this equals 1024/2 = 512 ADC, since V_{cc} = 5 V =

1024 ADC. The current is AC and sensitivity is 40 mV/A.

The current I_{rms} is measured and calculated from: $I_{rms} = I_{peak} / 2\sqrt{2}$.

A discussion of the rest of 'main' and other macros, including several calculations performed by the system may be found the **inset**. You may want to refer to the Flow-code program in archive file **090866-11.zip** to be able to follow the use of some labels. "Lest we forget", the PIC config bits: XT, WDT-OFF, POWUPTMR-ON, MCLR-External. Fail-Safe clock enabled. A 4 MHz quartz crystal is used.

First start-up

The first time the system is powered up, the data in the EEPROM is inconsistent, showing abnormally high credit values. To solve this, simply switch the system ON with the



START button pressed. The display will show 'credit cleared'.

Next, run the SETUP macro, this will load correct values into several variables. This is done by switching the system ON but this time keeping 'SETUP' pressed. Some instructions are displayed about the COIN switch acting as the '+' key, likewise 'SETUP' doubling as '-' and 'START' to confirm your selection.

First the system asks for the voltage setting. You can press keys to increase or decrease AC grid voltage. The initial value is 230 VAC. Set the actual value in your area, not the nominal value.

Second, the calibration value — lowering it makes the system calculate faster.

Finally the selling price is adjusted by setting the number of kWhs credited by one coin.

Example!

Test conditions: Velleman Power Monitor, input 230 VAC but only 220 VAC out when loaded with a 1400-watts heater. Credit equal to 6 kWh, shows 360 kWhmin on display. Power monitor showing 0.0 kWh. Calibration value default: 2000. Connected load (1400 W heater), 6 A detected both in Velleman and EV charger. After approx. 46 minutes, the Velleman Power Monitor reading changed from 0.9 to 1.0 kWh. The credit on the EV Charger was 302 kWhmin. End of test.

So the EV Charger accounted for 58 kWh/min, instead of 60 kWhmin. Recalling that 1 kWh = 3,600,000 Ws, we have 58 kWhmin = 3,480,000 Ws and consequently a difference

of 120,000 Ws to account for. The upshot is that the macro 'second' was called in a too large period. With $3,600,000/3,480,000 = 1.034$ you get an approximation only, but the period of calling macro 'second' appears to be 34 ms too long. Now, if 1.034 s is achieved with calibration '2000' then 1 second is achieved with $2000/1.034 = 1933$, which will be the required calibration value.

Closing considerations and ideas

Looking at different kinds of EV, a typical electrical scooter charge in kWh is: $48\text{ V} \times 60\text{ Ah} = 2.88\text{ kWh}$. An electric car charge in is much larger at up to 30 kWh, say, for the BMW Mini-e AC Propulsion, or the Tesla Roadster. The ElektorWheelie, then: $24\text{ V} \times 9\text{ Ah} = 216\text{ Wh}$ which in the author's country cost 3 eurocents to recharge (assuming 1 € gives 33 recharge units). An electric scooter takes only one hour to recharge, while a car can take up to eight hours.

The use of an Allegro current sensor was inspired by the *ElektorWheelie* article. The 756ACS device being bidirectional, it's better suited for AC applications. The device comes factory calibrated and a comparison of readings against a high-end Fluke current clamp gave identical results.

Future enhancements include improving the disconnecting of the relays when the credit is zero. First check for I_{RMS} , and if the current is still large, say larger than 4 A, switch the relays when the current passes the zero crossing. This involves delays in the relay, the driver and the MCU to be accounted

for. Lastly, I'd like to see an AC line voltage measurement included to ensure energy calculations are fair to both vendor and customer.

(ogo866)

Some interesting websites

<http://ewworld.com/index.cfm>

http://fadisel.com/vending-cebek/coins-selector_P_325.aspx

www.abberfield.com.au/a/60.html

Electrical safety

The hardware is connected to an AC power outlet and does not constitute an isolating device between the AC grid and the load. Consequently, **all relevant electrical safety precautions for equipment carrying and routing live AC power must be observed when building and using this project.** This should not be taken lightly and some help is provided by the red lines in the circuit diagram; these indicate connections carrying live AC and requiring suitable isolation. Constructors should also observe 'safety guidelines for charging' supplied by the manufacturer of any EV connected up.

It is mandatory to install proper earthing for outdoor use, as well as an external current limiter. The *Campsite AC Monitor* from Elektor June 2009 is an ideal complement for ad hoc grids with 10 A or less available.

All plugs, cables, wiring and sockets used on, or in conjunction with, the EV Charger must be rated and approved for outdoor use. The unit should be mounted in a rugged enclosure complying with your national or local electrical safety regulations and the same goes for the coin validator.

Finally, beginners should seek the assistance of a qualified electrician when building this project.

NOW, THERE'S EVEN MORE TO DISCOVER.

NEW!



The upgraded Elektor-PLUS subscription!

- All 11 issues including the Summer Circuits edition
- Included in your PLUS subscription: Annual DVD 2010
- **20%** cheaper than normal retail price
- Welcome gift worth £25
- Up to **40% discount** on selected Elektor products
- Elektor is delivered to your doorstep every month
- Read your copy before everyone else
- **NEW:** On your personalized Elektor PLUS website, you have permanent access to the three latest issues of the magazine in PDF format, as well as to a fast Elektor search engine!

NEW:
exclusive access to
www.elektor-plus.com!

When taking out an Elektor PLUS subscription you get **exclusive access** to www.elektor-plus.com where the three latest editions of Elektor magazine are available in the form of pdf files (i.e. the current issue and the two preceding ones). With a simple click you download the complete issue (front to back!) or any single article. www.elektor-plus.com also supplies the most extensive Elektor search engine found on the web. However the upgraded PLUS subscription offers many more interesting extras like free E-books and supplementary articles.

www.elektor.com/subs • Tel. +44 (0) 20 8261 4509


Or use the subscription order form near the end of the magazine.

elektor

Grid Dipper

By Ronald Dekker (The Netherlands)

For a long time, the grid dip meter was the 'HF multimeter' of every RF engineer or technician. Like an ordinary multimeter, it is a simple instrument that can be used for a wide variety of quick and useful measurements on high frequency circuits, such as determining the resonant frequency of an LC circuit, determining the values of unmarked coils or capacitors, and checking the signal paths of RF stages.

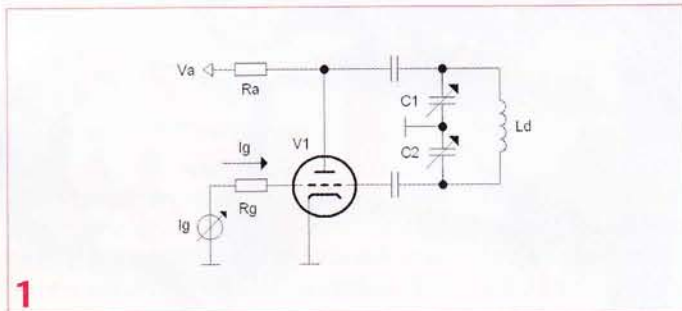

1

A grid dip meter essentially consists of nothing more than an LC oscillator with a moving-coil meter that provides an indication of the amount of power drawn by the oscillator. The oscillator coil is mounted outside of the grid dipper enclosure so that it can be brought close to the LC circuit to be measured. The operating principle is very simple in practice. The frequency of the oscillator is varied slowly by adjusting a variable capacitor. When the oscillator frequency matches the resonant frequency of the circuit being measured, the circuit will start to resonate. The circuit thus draws power from the oscillator, which is indicated by a 'dip' on the meter. The resonant frequency of the circuit being measured can be deter-


mined by reading the oscillator frequency from a calibrated scale attached to the tuning knob. Grid dip meters usually have plug-in coils to make it easy to connect different coils. This allows the meter to be used over a wide range of frequencies.

The name 'grid dip meter' originates from the time when these instruments were built using valves. In these instruments, the grid current drops when the oscillator draws more power. This may sound a bit strange at first glance, since increased power consumption is ordinarily associated with increased current. To understand what's happening here, let's first examine the circuit of a grid dip meter in its most rudimentary form. **Figure 1** shows a Colpitts oscillator built around an RF triode. The advantage of a Colpitts oscillator is that it has a single simple coil without any taps, which makes it easy to exchange coils using a plug-and-socket connector. The drawback of this arrangement is that the circuit requires a two-gang variable capacitor.

Immediately after the oscillator is switched on, the grid voltage will be nearly zero and the valve current will be high. At first this current will be a noise signal resulting from the noise generated by the grid resistor or other noise sources. As the anode load consists of a tuned circuit, only one frequency component of this noise signal will be present on the anode. In addition, the LC circuit is designed to feed back part of the amplified signal to the grid in phase, which causes the circuit to start oscillating with gradually increasing signal amplitude at the oscillating frequency. Of course, the amplitude cannot increase indefinitely. After a few cycles, the signal amplitude on the grid increases to the point that the grid goes positive on the positive half-cycles of the signal, which causes a grid current to flow. This grid current imposes a negative DC component on the grid voltage, which acts to cut off the valve and reduce the gain. This control mechanism stabilises the oscillator at a constant signal amplitude. If



2

 

3




a second circuit tuned to the same frequency is now brought close to the oscillator, it will draw power from the oscillator. This power loss is offset by a slight reduction in the negative DC component of the grid voltage, which increases the gain. Naturally, this causes the grid current to drop, which produces the 'grid dip'.

The Philips Research laboratory, originally established as the 'Naturkundig Laboratorium' (physics laboratory) or NatLab for short, will celebrate its 100th anniversary in 2014. Despite what the name may suggest, during the past 100 years it has carried out research not only in the field of physics, but also in many other fields such as chemistry, mathematics, semiconductor fabrication and (of course) electrical engineering and electronics. Especially at the time when you couldn't simply order or purchase everything you needed, the NatLab had extensive workshops for the fabrication of mechanical and electronic devices and glassware, where highly skilled craftsmen produced outstanding instruments to order for the researchers. It's hardly surprising that very intriguing items can occasionally be found in the nooks and crannies of a laboratory with such a rich history.

For example, the grid dipper shown in **Figure 2** turned up during a housecleaning operation in the instrumentation section – the

group within NatLab that is responsible for purchasing and renting test equipment. This splendid instrument, which was produced exclusively in the service shops, bears a strong resemblance to the famous Model 59 grid dip meter from Measurements Corporation [1]. It consists of a probe head housing a high-frequency oscillator and a small enclosure housing the power supply (**Figure 3**) and the moving-coil meter, along with a compartment holding a set of coils for frequency ranges extending from 2.2 MHz to 400 MHz (**Figure 4**). Sadly, the documentation for this instrument was no longer available, but the point-to-point wiring makes it easy to trace the circuit diagram (**Figure 5**). This instrument had probably not been used for 30 years or so, so it was certainly a good idea to first carefully reform the electrolytic capacitors in the power supply [3]. After we treated the selector switch with a little bit of contact spray, the dipper worked perfectly – practically as good as new!

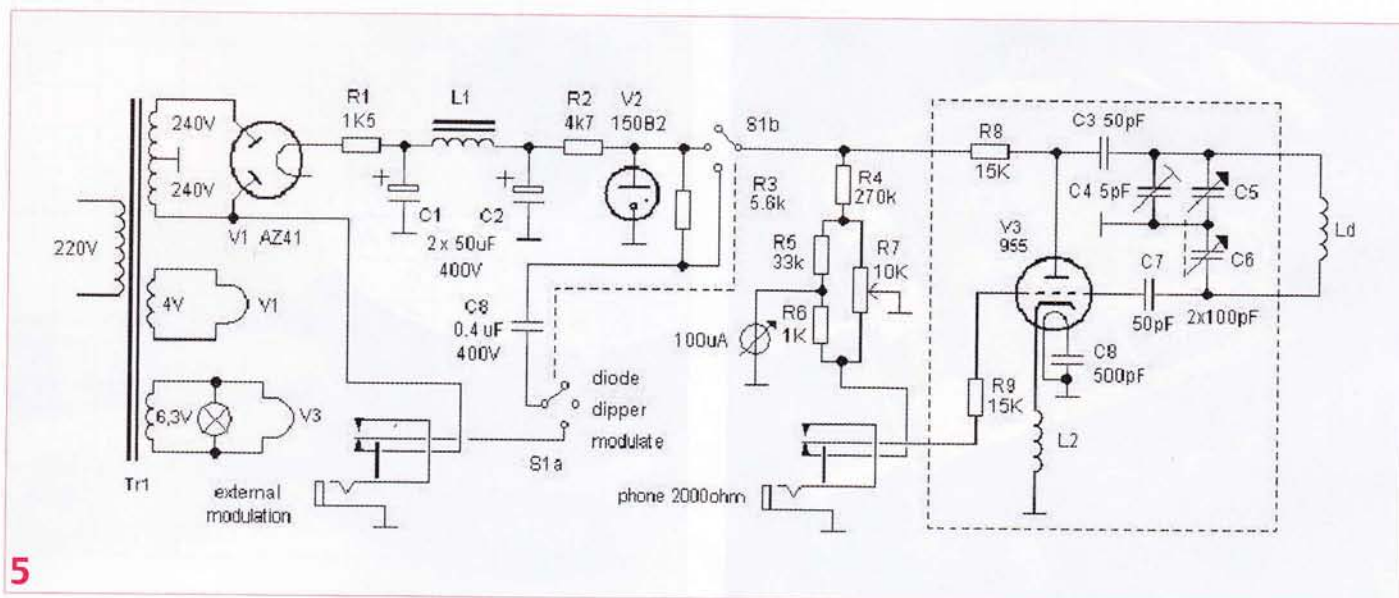The Colpitts oscillator is built around a type 955 acorn triode valve (**Figure 6**). This type of miniature valve, which is called an 'acorn' on account of its shape, was developed by RCA in 1935 [2]. The special method used to fabricate the contacts minimises the parasitic capacitance and inductance of the lead wires, so the valves can be



Winding data for L_d (all coils wound on 19-mm plastic coil forms unless otherwise specified)

Frequency range [MHz]	Number of turns	Wire diameter [mm]
2.2 – 5	113	0.15
5 – 10	52	0.5
10 – 22	21	0.7
22 – 45	7	1.0
45 – 100	3	1.0
100 – 220	1 turn, length 4.5 cm, width 18 mm	
220 – 400	1 turn, length 11 mm, width 8 mm	

used to build oscillators operating into the gigahertz range. The oscillator of the grid dipper is built entirely in accordance with the rules of high-frequency engineering, with the leads kept as short as possible by connecting the grid and the anode directly to the tuning capacitor via tubular capacitors C3 and C7. As the gain of the 955 varies considerably over the full frequency range, P1 is provided to allow the operating point of the valve to be adjusted over a wide range.

The grid dip meter is easy to use. First you select a coil according to the estimated resonant frequency of the circuit to be measured and plug it in to the probe head. With S1 in the Dipper position, you then adjust P1 until the pointer is somewhere to the right of the midrange position. Next you place the sense coil close to the coil to be measured (Figure 7). The strongest magnetic coupling is obtained when the windings of the two coils are parallel. Now you rotate the tuning knob until you see a clear dip in the grid current. The oscillator frequency is affected to a certain extent by the presence of the circuit to be measured (frequency pulling), so the next step is to reduce the coupling by increasing the distance between the coils and then repeat the measurement.

When S1 is in the Modulate position, the oscillator is AM modulated at 50 Hz and the grid dip meter can be used as a signal generator. When S1 is in the Diode position, the anode voltage of the oscillator is switched off and the instrument can be used to detect the presence of a high-frequency signal, either visually by the motion of the meter pointer or audibly using headphones.



If you aren't afraid of a bit of precision mechanical construction, this circuit is an excellent choice for building a DIY copy of the instrument. You can use a Philips type 4761 (E1C) valve in place of the 955, or you can try using a normal RF triode such as an EC92, although this will considerably reduce the maximum frequency range. Be sure to use only one common ground point for the oscillator. Naturally, the valves in the power supply can be replaced by semiconductor diodes or Zener diodes. Coil L2 consists of a 10-k Ω resistor wound with 30 turns of 0.15-mm copper wire (Figure 6). The winding data for coil L_d is given in the table. Finally, for those of you who regard messing about with valves and high voltages as a waste of time, lots of schematic diagrams for dip meters using transistors can be found on the Web [4].

(100101-I)

Links and Reference documents

- [1] http://oak.cats.ohiou.edu/~postr/bapix/Dip_59.htm
- [2] www.antiquewireless.org/otb/acorntube.htm
- [3] 'Reforming Old Capacitors', Elektor May 2006
- [4] www.qsl.net/iz7ath/web/02_brew/15_lab/02_dipper/pag01_eng.htm

  Retronics is a monthly column covering vintage electronics including legendary Elektor designs. Contributions, suggestions and requests are welcomed; please send an email to editor@elektor.com



Hexadoku

Puzzle with an electronics touch

High time for some puzzle fun with this new May 2010 Hexadoku. Leave the lawn mower in the shed, the solder iron in the stand and get cracking with this month's challenge.

Send the hexadecimal numbers in the grey boxes to us and you automatically enter the prize draw for four Elektor Shop vouchers. Have fun!

The instructions for this puzzle are straightforward. Fully geared to electronics fans and programmers, the Hexadoku puzzle employs the hexadecimal range 0 through F. In the diagram composed of 16 × 16 boxes, enter numbers such that all hexadecimal numbers 0 through F (that's 0-9 and A-F) occur once only in each row, once

in each column and in each of the 4×4 boxes (marked by the thicker black lines). A number of clues are given in the puzzle and these determine the start situation. Correct entries received enter a draw for a main prize and three lesser prizes. All you need to do is send us the numbers in the grey boxes.

Solve Hexadoku and win!

Correct solutions received from the entire Elektor readership automatically enter a prize draw for one Elektor Shop voucher worth £ 80.00 and three Elektor Shop Vouchers worth £ 40.00 each, which should encourage all Elektor readers to participate.

Participate!

Before June 1, 2010, send your solution (the numbers in the grey boxes) by email, fax or post to

Elektor Hexadoku – 1000, Great West Road – Brentford TW8 9HH
United Kingdom.

Fax (+44) 208 2614447

Email: hexadoku@elektor.com

Prize winners

The solution of the March 2010 Hexadoku is: 51E7A.

The £80.00 voucher has been awarded to: Jan Schoubo (Denmark).

The £40.00 vouchers have been awarded to: Paul Kirsch (Luxembourg), Laurence Hamelin (France) and Maarten Koppe (The Netherlands).

Congratulations everybody!

3	2			5		0	4	E							
	7		F		A	1				D	5	0			2
	5	E	A						1	8		7	4		
4	0		1	6			B			2	F				
D						3	A	C	0		5		E		
6		A	E				0		2	1		D	8	7	
C	B	9										A	3	F	
		4	0			C		3		8	E	9			
1			4		7	B		A		E		C			
		3	6				C		5	9		B			8
	9	5	B	A	E	4			0	C			7	6	3
F	7	C	9	3		1	B		2			A			
		1			B					5					6
		B	7		2	E	D	1					C	8	
9	4		8		5	F			E	0				A	
A		F		1					4	6					3

(c) PZZL.com

1	9	C	F	3	7	8	D	A	4	E	B	2	0	6	5
5	2	7	4	6	E	0	B	F	C	D	3	9	A	8	1
3	D	6	0	C	2	A	9	5	1	7	8	F	E	4	B
8	E	B	A	1	5	4	F	0	2	9	6	C	D	3	7
7	1	E	9	4	0	2	6	3	8	B	F	D	C	5	A
6	8	5	D	B	C	7	A	4	9	1	0	3	F	2	E
2	0	F	3	8	D	5	1	E	7	A	C	4	6	B	9
4	C	A	B	F	9	3	E	6	D	5	2	7	1	0	8
A	4	2	6	0	8	1	7	B	3	C	5	E	9	F	D
B	7	0	5	9	6	E	2	1	A	F	D	8	3	C	4
9	F	1	8	D	3	C	5	7	6	4	E	B	2	A	0
C	3	D	E	A	F	B	4	2	0	8	9	5	7	1	6
D	A	3	2	5	4	6	8	C	E	0	7	1	B	9	F
F	B	9	7	2	1	D	0	8	5	3	A	6	4	E	C
E	6	8	1	7	A	F	C	9	B	2	4	0	5	D	3
0	5	4	C	E	B	9	3	D	F	6	1	A	8	7	2

The competition is not open to employees of Elektor International Media, its business partners and/or associated publishing houses.

ELEKTOR SHOWCASE

To book your showcase space contact Huson International Media

Tel. 0044 (0) 1932 564999 Fax 0044 (0) 1932 564998

ARMAIDE

www.armaide.com

An integrated software development system targeting NXP LPC2000-family microcontrollers.

- Efficient native ARM7 code without C or assembler
 - Suits Pascal / Delphi programmers
 - IEEE Floating-point Real support
- Professional software at hobbyist prices.

ATOMIC PROGRAMMING LTD

www.atomicprogramming.com

- AP-114 ISP/JTAG Programming System
- JTAG Programming and Testing
- Boundary Scan Testing
- Universal In-System Programming
- EEPROM and SPI Flash Out-of-Circuit Programming
- Generic GDB Proxy Server
- Jennic JN5148 ZigBee Development Applications
- Training Platform available



AVIT RESEARCH

www.avitresearch.co.uk

USB has never been so simple... with our USB to Microcontroller Interface cable. Appears just like a serial port to both PC and Microcontroller, for really easy USB connection to your projects, or replacement of existing RS232 interfaces.



See our webpage for more details. From £10.00.

BETA LAYOUT

www.pcb-pool.com


Beta layout Ltd Award-winning site in both English and German offers prototype PCBs at a fraction of the cost of the usual manufacturer's prices.



BLACK ROBOTICS

www.blackrobotics.com

 Robot platforms and brains for research, hobby and education.



- Make your robot talk!
- TalkBotBrain is open-source
- Free robot speech software
- Robot humanisation technology
- Mandibot Gripper Robot

ByVac

www.byvac.com

- PIC32 With BASIC
- ARM With Forth
- USB to I2C
- Serial Devices
- VT100 LCD Displays



DECIBIT CO.LTD

www.decibit.com

- Development Kit 2.4 GHz
- Transceiver nRF24L01
- AVR MCU ATmega168



CEDA

www.ceda.in

ceda@vsnl.com

CEDA e-learning
PADS | OrCAD | ALLEGRO
PCB layout @ \$5 Hourly

- PCB Layout @ \$5 Hourly
- Learn PCB Designing with Multimedia DVD in OrCAD, PADS & ALLEGRO
- Self or e-learning with support by email, phone & web-meeting

DESIGNER SYSTEMS

<http://www.designersystems.co.uk>

Professional product development services.

- Marine (Security, Tracking, Monitoring & control)
- Automotive (AV, Tracking, Gadget, Monitoring & control)
- Industrial (Safety systems, Monitoring over Ethernet)
- Telecoms (PSTN handsets, GSM/GPRS)
- AudioVisual ((HD)DVD accessories & controllers)

Tel: +44 (0) 845 5192306

EASYSYNC

<http://www.easysync.co.uk>

EasySync Ltd sells a wide range of single and multi-port USB to RS232/RS422 and RS485 converters at competitive prices.



ELNEC

www.elnec.com

Europe's leading device programmers manufacturer:

- reliable HW:
 - 3 years warranty for most programmers
- support over 52.000 devices
- free SW updates
- SW release: few times a week
- excellent technical support: Algorithms On Request, On Demand SW
- all products at stock / fast delivery



FIRST TECHNOLOGY TRANSFER LTD.

<http://www.ftt.co.uk>

- Training and Consulting for IT, Embedded and Real Time Systems
- Assembler, C, C++ (all levels)
- 8, 16 and 32 bit microcontrollers
- Microchip, ARM, Renesas, TI, Freescale
- CMX, uCOSII, FreeRTOS, Linux operating systems
- Ethernet, CAN, USB, TCP/IP, Zigbee, Bluetooth programming



FLEXIPANEL LTD

www.flexipanel.com

TEAclippers - the smallest PIC programmers in the world, from £20 each:

- Per-copy firmware sales
- Firmware programming & archiving
- In-the-field firmware updates
- Protection from design theft by subcontractors



HAMEG® Instruments

A Rohde & Schwarz Company

- Oscilloscopes
- Power Supplies
- Spectrum Analyzers
- RF Instruments
- Programmable Measuring Instruments

Great Value in Test & Measurement

www.hameg.com

products and services directory

FUTURE TECHNOLOGY DEVICES

<http://www.ftdichip.com>

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s.

Complete with PC drivers, these devices simplify the task of designing or upgrading peripherals to USB



MQP ELECTRONICS

www.mqp.com

- Low cost USB Bus Analysers
- High, Full or Low speed captures
- Graphical analysis and filtering
- Automatic speed detection
- Bus powered from high speed PC
- Capture buttons and feature connector
- Optional analysis classes



www.elektor.com

HEXWAX LTD

www.hexwax.com

World leaders in Driver-Free USB ICs:

- USB-UART/SPI/I2C bridges
- TEAleaf-USB authentication dongles
- expandIO-USB I/O USB expander
- USB-FileSys flash drive with SPI interface
- USB-DAQ data logging flash drive

ROBOT ELECTRONICS

<http://www.robot-electronics.co.uk>

Advanced Sensors and Electronics for Robotics

- Ultrasonic Range Finders
- Compass modules
- Infra-Red Thermal sensors
- Motor Controllers
- Vision Systems
- Wireless Telemetry Links
- Embedded Controllers



ROBOTIQ

<http://www.robotiq.co.uk>

Build your own Robot!

Fun for the whole family!

Now, available in time for X-mas

- Arduino Starter Kits *NEW!!*
- Lego NXT Mindstorms
- Affordable Embedded Linux Boards
- Vex Robotics (kits and components)
- POB Robots (kits and components)

email: sales@robotiq.co.uk Tel: 020 8669 0769



RFID COMPONENTS

<http://www.apdanglia.org.uk>

For DIY, OEM's & Experimenters

- EM4100 Cards .99 p (Prices inc vat)

- Keyfobs £1.09

- R/W Keyfobs £1.65

- RFID Coils £2.95

- RFID PCB

- with RS232 port

- RFID IC's EM4095 - U2270B

- microRFID module (similar to Core ID12)

- Free Reader download - Technical pages

Order online 24 hrs - Tel: 01244 520684



USB INSTRUMENTS

<http://www.usb-instruments.com>

USB Instruments specialises

in PC based instrumentation

products and software such

as Oscilloscopes, Data

Loggers, Logic Analysers

which interface to your PC via USB.



VIRTINS TECHNOLOGY

www.virtins.com

PC and Pocket PC based

virtual instrument such

as sound card real time


oscilloscope, spectrum

analyzer, signal generator,

multimeter, sound meter,

distortion analyzer, LCR meter.

Free to download and try.

 

SHOWCASE YOUR COMPANY HERE

Elektor Electronics has a feature to help customers promote their business. Showcase - a permanent feature of the magazine where you will be able to showcase your products and services.

- For just £242 + VAT (£22 per issue for eleven issues) Elektor will publish your company name, website address and a 30-word description
- For £363 + VAT for the year (£33 per issue for eleven issues) we will publish the above plus run a 3cm deep full colour

image - e.g. a product shot, a screen shot from your site, a company logo - your choice

Places are limited and spaces will go on a strictly first come, first served basis. So-please fax back your order today!

I wish to promote my company, please book my space:

- Text insertion only for £242 + VAT
- Text and photo for £363 + VAT

NAME: ORGANISATION:

JOB TITLE:

ADDRESS:

.....

..... TEL:

PLEASE COMPLETE COUPON BELOW AND FAX BACK TO 00-44-(0)1932 564998

COMPANY NAME

WEB ADDRESS

30-WORD DESCRIPTION

.....

.....

.....

.....


.....

.....

.....

Going Strong

 A world of electronics from a single shop!



Limited Period Offer for Subscribers!
£5 DISCOUNT
www.elektor.com/may

Get started quickly and proceed rapidly

Python Programming and GUIs

This book is aimed at people who want to interface PCs with hardware projects using graphic user interfaces. Desktop and web based applications are covered. The programming language used is Python, an object-oriented scripting language; a higher level language than, say, C. Obviously having fewer lines of code will be quicker to write but also fewer lines of code means fewer opportunities to make mistakes. Code will be more readable, and easier to modify at a later date. You can concentrate on the overall operation of the system you are making. This abstraction also applies when writing graphic user-interfaces. Writing low level code for graphics and mouse clicks and the like is something that you do not have to do. In Python all this is wrapped up in relatively simple functions. The book guides you through starting with Linux by way of a free downloadable, live bootable distribution that can be ported around different computers without requiring hard drive installation. Practical demonstration circuits and downloadable, full software examples are presented that can be the basis for further projects.

224 pages • ISBN 978-0-905705-87-3 • £29.50 • US \$47.60




Microsoft approved!

Learn more about C# programming and .NET

C# 2008 and .NET programming

This book is aimed at Engineers and Scientists who want to learn about the .NET environment and C# programming or who have an interest in interfacing hardware to a PC. The book covers the Visual Studio 2008 development environment, the .NET framework and C# programming language from data types and program flow to more advanced concepts including object oriented programming.

 240 pages • ISBN 978-0-905705-81-1
 £29.50 • US \$47.60




Circuit design and programming

Complete practical measurement systems using a PC

This book covers both hardware and software aspects of designing typical embedded systems based on personal computers running the Windows operating system. It's use of modern techniques in detailed, numerous examples has been designed to show clearly how straightforward it can be to create the interfaces between digital and analog electronics, programming and Web-design. Readers are encouraged by examples to program with ease; the book provides clear guidelines as to the appropriate programming techniques "on the fly".

292 pages • ISBN 978-0-905705-79-8
 £28.50 • US \$46.00

Books

 


Home electric power

Your own Eco-Electrical Home Power System

This book provides the semi-technical, power-conscious homeowner a place to begin in the quest for home electric power. Both the essential principles and detailed information on how to build or maintain a home electric system off the utility grid are presented in an easy-going style. This booklet will help you to safeguard or develop your own home electricity supply. It contains step-by-step calculations, practical details, examples and much more.

 75 pages • ISBN 978-0-905705-82-8
£16.50 • US \$26.70




Several case studies included

PIC Cookbook for Virtual Instrumentation

The software simulation of gauges, control-knobs, meters and indicators which behave just like real hardware components on a PC's screen is known as virtual instrumentation. In this book, the Delphi program is used to create these mimics and PIC based external sensors are connected via a USB/RS232 converter communication link to a PC. Case studies of virtual instruments are detailed including a compass, an oscilloscope, a digital and analogue thermometer and virtual displays for cars and aircraft.

 264 pages • ISBN 978-0-905705-84-2
£29.50 • US \$47.60



Look into the electronics of eco-power

Practical Eco-Electrical Home Power Electronics


This book is a sequel to *Your own Eco-Electrical Home Power System* and goes deeper into the electronics of photovoltaic and thermal solar technologies, wind power conversion, inverter circuits, and loads such as electronic lighting. Power electronics circuit theory is presented while analyzing commercial circuits, including little-known converters and subtleties such as snubbers and leakage inductance. The book also offers in-depth coverage of power system strategizing for optimal efficiency and utility, including a 170 V DC bus, commercial solar charger design with detailed circuit explanations, wind generator electric machine electromechanical theory, wind converter design requirements and the series-L zero-current-switching converter and power supplies found inside loads connected to home power systems and their potential problems and consequences for inverters.

150 pages • ISBN 978-0-905705-83-5
£24.90 • US \$40.20

More information on the
Elektor Website:
www.elektor.com

Elektor
Regus Brentford
1000 Great West Road
Brentford
TW8 9HH
United Kingdom
Tel.: +44 20 8261 4509
Fax: +44 20 8261 4447
Email: sales@elektor.com

elektor

 


See the light on Solid State Lighting

DVD LED Toolbox

This DVD-ROM contains carefully-sorted comprehensive technical documentation about and around LEDs. For standard models, and for a selection of LED modules, this Toolbox gathers together data sheets from all the manufacturers, application notes, design guides, white papers and so on. It offers several hundred drivers for powering and controlling LEDs in different configurations, along with ready-to-use modules (power supply units, DMX controllers, dimmers, etc.). In addition to optical systems, light detectors, hardware, etc., this DVD also addresses the main shortcoming of power LEDs: heating. This DVD contains several Elektor articles (more than 100) on the subject of LEDs.

 ISBN 978-90-5381-245-7
£28.50 • US \$46.00



110 issues, more than 2,100 articles

DVD Elektor 1990 through 1999

This DVD-ROM contains the full range of 1990-1999 volumes (all 110 issues) of Elektor Electronics magazine (PDF). The more than 2,100 separate articles have been classified chronologically by their dates of publication (month/year), but are also listed alphabetically by topic. A comprehensive index enables you to search the entire DVD.

ISBN 978-0-905705-76-7
£69.00 • US \$111.30



Bestseller!

A whole year of Elektor magazine onto a single disk

DVD Elektor 2009

This DVD-ROM contains all editorial articles published in Volume 2009 of the English, American, Spanish, Dutch, French and German editions of Elektor. Using the supplied Adobe Reader program, articles are presented in the same layout as originally found in the magazine. An extensive search machine is available to locate keywords in any article. With this DVD you can also produce hard copy of PCB layouts at printer resolution, adapt PCB layouts using your favourite graphics program, zoom in / out on selected PCB areas and export circuit diagrams and illustrations to other programs.

ISBN 978-90-5381-251-8

£17.50 • US \$28.30




Completely updated

Elektor's Components Database 5

The program package consists of eight databanks covering ICs, germanium and silicon transistors, FETs, diodes, thyristors, triacs and optocouplers. A further eleven applications cover the calculation of, for example, LED series droppers, zener diode series resistors, voltage regulators and AMVs. A colour band decoder is included for determining resistor and inductor values. ECD 5 gives instant access to data on more than 69,000 components. All databank applications are fully interactive, allowing the user to add, edit and complete component data.

ISBN 978-90-5381-159-7

£24.90 • US \$40.20

 


UniLab

(April 2010)

A power supply with adjustable output voltage and current limiting is part of the basic equipment of every electronics lab. However, the increased complexity of a switch-mode design scares away many potential builders, even though it actually isn't all that complicated if you use a suitable combination of well-known technologies. This circuit is suitable for building a single or dual power supply.

PCB and all components, less power transformer

Art.# 090786-71 • £64.00 • US \$103.30

 

Reign with the Sceptre

(March 2010)

This open-source & open-hardware project aims to be more than just a little board with a big microcontroller and a few useful peripherals — it seeks to be a fast prototyping system. To justify this title, in addition to a very useful little board, we also need user-friendly development tools and libraries that allow fast implementation of the board's peripherals. Ambitious? Maybe, but nothing should deter you from becoming Master of Embedded Systems Universe with the help of the Elektor Sceptre.

PCB, populated and tested, test software loaded

Art.# 090559-91 • £132.00 • US \$212.90



Bestseller!


Modulo D

(March 2010)

The external appearance of this small module with an LC display almost belies what it has inside: a complete stereo preamplifier and final amplifier with IR remote control, adjustable tone, volume and signal levels, and an output power of 2 × 20 W (Class D), all with a single 12-V supply voltage. This makes it perfect for use in a car, boat or motor home.

PCBs, SMD-populated, and all other components

Art.# 090563-71 • £69.90 • US \$112.80

 

Preselector for Elektor SDR

(December 2009)

Elektor's Software Defined Radio (SDR) is deservedly popular. The performance of a receiver depends to a large extent on its input filters. A selective input circuit improves antenna matching and immunity to interference from other strong signals. This preselector allows the use of up to four filters, tuned under software control using varicap diodes. A tuned loop antenna is also described that lets you use our SDR without an outdoor antenna.

Kit of parts, contains partly populated board, coil formers, ferrite rod with coils

Art.# 090615-71 • £47.00 • US \$75.90

	£	US\$
May 2010 (No. 401)		
dsPIC Control Board		
090073-91 PCB, populated and tested	www.elektor.com	
Cloud Altitude Meter		
090329-91 Populated PCB in enclosure (see poll).....	www.elektor.com	
In-vehicle CO2 Meter		
100020-71 Kit of parts	137.00	221.20
100020-72 Enclosure	19.00	30.70
VisiOLED		
081141-1 Printed circuit board.....	13.30	21.50
April 2010 (No. 400)		
UniLab		
090786-1 Printed circuit board.....	16.00	25.90
090786-71 PCB and all components, less power transformer	64.00	103.30
Small is Beautiful: Minimod18		
090773-41 Programmed controller with Bootloader pre-programmed	21.80	35.20
090773-91 PCB, populated and tested with Bootloader pre-programmed.....	56.00	90.40
Bluetooth for OBD-2		
090918-71 PCB with SMDs fitted, BTM222 Bluetooth module.....	26.70	43.10
Fun with Fireflies		
100014-1 Printed circuit board.....	11.00	17.80
100014-41 Programmed controller.....	11.00	17.80
Beep, beep... Sesame		
081143-41 Programmed controller.....	15.50	25.00
5 V Power Controller		
090719-1 Printed circuit board.....	8.90	14.40
March 2010 (No. 399)		
Reign with the Sceptre		
090559-91 PCB, populated and tested, test software loaded	132.00	212.90
Modulo D		
090563-71 PCB, SMD-populated, and all other components.....	69.90	112.80
February 2010 (No. 398)		
Battery Checker		
071131-41 ATmega32-16PU, programmed	17.80	28.80
071131-71 Kit of parts, excl. enclosure	124.00	200.00
Winamp Controller		
090531-71 Kit of parts	89.00	143.60
The ATM18 Radio Computer		
090740-71 PCB with Si4734/35 radio IC ready mounted and tested.....	27.50	44.40
January 2010 (No. 397)		
USB Magic Eye		
090788-1 Printed circuit board.....	9.90	16.00
090788-41 ATtiny2313-20PU, programmed	9.90	16.00
MIAC for Home Automation		
090278-91 Populated PCB in enclosure	154.00	248.40
Dimmer with a Micro		
090315-41 PIC12F629A, programmed.....	7.60	12.30
December 2009 (No. 396)		
Preselector for Elektor SDR		
090615-71 Kit of parts, contains partly populated board, coil formers, ferrite rod with coils.....	47.00	75.90
Top-of-the-Bill Lights Sequencer		
090125-1 PCB, bare (master module).....	10.80	17.50
090125-2 PCB, bare (lamp module).....	2.30	3.80
090125-41 Controller (PIC18F2550) for main PCB, programmed	14.50	23.40
090125-42 Controller (PIC12F508-I/SN) for lamp unit, programmed	2.30	3.80
The Vikings Are Coming!		
080948-71 Kit of parts: bare PCB and bluetooth module BTM222	23.70	38.30


Bestsellers

Books	1	PIC Cookbook for Virtual Instrumentation ISBN 978-0-905705-84-2 £29.50US \$47.60
	2	Complete practical measurement using a PC ISBN 978-0-905705-79-8 £28.50US \$46.00
	3	C# 2008 and .NET programming ISBN 978-0-905705-81-1 £29.50US \$47.60
	4	PIC Microcontrollers ISBN 978-0-905705-70-5 £32.00US \$51.70
	5	Eco-Electrical Home Power Electronics ISBN 978-0-905705-83-5 £24.90US \$40.20
CD/DVD-ROMs	1	DVD Elektor 2009 ISBN 978-90-5381-251-8 £17.50US \$28.30
	2	DVD High-End Valve Amplifiers ISBN 978-0-905705-86-6 £24.90 US \$40.20
	3	DVD LED Toolbox ISBN 978-90-5381-245-7 £28.50US \$46.00
	4	DVD Elektor 1990 through 1999 ISBN 978-0-905705-76-7 £69.00US \$111.30
	5	ECD 5 ISBN 978-90-5381-159-7 £24.90US \$40.20
Kits & Modules	1	Modulo D Art. # 090563-71 £69.90 ...US \$112.80
	2	SDR Preselector Art. # 090615-71 £47.00 US \$75.90
	3	Bluetooth for OBD-2 Art. # 090918-71 £26.70US \$43.10
	4	WinAmp Controller Art. # 090531-71 £85.00US \$143.60
	5	Battery Checker Art. # 071131-71 £124.00 ...US \$200.00

Order quickly and securely through
www.elektor.com/shop
 or use the Order Form near the end
 of the magazine!




 Elektor
 Regus Brentford
 1000 Great West Road
 Brentford TW8 9HH • United Kingdom
 Tel. +44 20 8261 4509
 Fax +44 20 8261 4447
 Email: sales@elektor.com




Unilab V/I/Temp. Readout

 The lab power supply published in the April 2010 edition now gets a dedicated measurement circuit showing not just voltage and current on a 4 x 20 character LCD, but also temperature inside the case. The A-D conversion and calculations are handled by an Atmega 168 processor. A special circuit configuration is used to measure the current in the negative supply rail.



Program your Own RFIDs

 RFID devices type EM4102 are widely available and a suitable reader was described in Elektor some months ago, based on an EM4095 reader chip on a small circuit board. The same board is now used to implement an RFID reader based on an ATtiny2313 micro. As part of the project, you'll be making your own sensor RFIDs for wireless transmitting of measured sensor data to the reader.



OBD2 Mini Simulator

Those of you keen on writing or developing utilities for vehicle diagnosis will soon discover that a real car is bit of a problem to have around in the electronics lab. In cases where a professional OBD-2 analyser is not available or affordable, our mini simulator for OBD signals may prove useful. The circuit supports four OBD-2 protocols and is likely to become indispensable to everyone working with OBD hardware and software.

We regret that 'Auto Balancer for LiPo Battery Packs' could not be accommodated in the May 2010 issue as planned.

*Article titles and magazine contents subject to change; please check the Magazine tab on www.elektor.com
Elektor UK/European edition: on sale May 20, 2010. Elektor USA edition: published May 13, 2010.*

www.elektor.com www.elektor.com www.elektor.com www.elektor.com www.elektor.com www.elektor.com

Elektor on the web

All magazine articles back to volume 2000 are available online in pdf format. The article summary and parts list (if applicable) can be instantly viewed to help you positively identify an article. Article related items are also shown, including software downloads, circuit boards, programmed ICs and corrections and updates if applicable. Complete magazine issues may also be downloaded.

In the Elektor Shop you'll find all other products sold by the publishers, like CD-ROMs, DVDs, kits, modules, equipment, tools and books. A powerful search function allows you to search for items and references across the entire website.

Also on the Elektor website:

- Electronics news and Elektor announcements
- Readers Forum
- PCB, software and e-magazine downloads
- Time limited offers
- FAQ, Author Guidelines and Contact



ORDERING INSTRUCTIONS, P&P CHARGES

All orders, except for subscriptions (for which see below), must be sent BY POST or FAX to our Brentford address using the Order Form overleaf. Online ordering: www.elektor.com/shop

Readers in the USA and Canada should send orders, except for subscriptions (for which see below), to the USA address given on the order form. Please apply to Elektor US for applicable P&P charges. Please allow 4-6 weeks for delivery.

Orders placed on our Brentford office must include P&P charges (Priority or Standard) as follows: Europe: £6.00 (Standard) or £7.00 (Priority) Outside Europe: £9.00 (Standard) or £11.00 (Priority)

HOW TO PAY

All orders must be accompanied by the full payment, including postage and packing charges as stated above or advised by Customer Services staff.

Bank transfer into account no. 40209520 held by Elektor Electronics with ABN-AMRO Bank, London.

IBAN: GB35 ABNA 4050 3040 2095 20.

BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

Cheque sent by post, made payable to Elektor Electronics. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA and MasterCard can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

COMPONENTS

Components for projects appearing in Elektor are usually available from certain advertisers in this magazine. If difficulties in the supply of components are envisaged, a source will normally be advised in the article. Note, however, that the source(s) given is (are) not exclusive.

TERMS OF BUSINESS

Delivery Although every effort will be made to dispatch your order within 2-3 weeks from receipt of your instructions, we can not guarantee this time scale for all orders. **Returns** Faulty goods or goods sent in error may be returned for replacement or refund, but not before obtaining our consent. All goods returned should be packed securely in a padded bag or box, enclosing a covering letter stating the dispatch note number. If the goods are returned because of a mistake on our part, we will refund the return postage. **Damaged goods** Claims for damaged goods must be received at our Brentford office within 10-days (UK); 14-days (Europe) or 21-days (all other countries). **Cancelled orders** All cancelled orders will be subject to a 10% handling charge with a minimum charge of £5.00. **Patents** Patent protection may exist in respect of circuits, devices, components, and so on, described in our books and magazines. Elektor does not accept responsibility or liability for failing to identify such patent or other protection. **Copyright** All drawings, photographs, articles, printed circuit boards, programmed integrated circuits, diskettes and software carriers published in our books and magazines (other than in third-party advertisements) are copyright and may not be reproduced or transmitted in any form or by any means, including photocopying and recording, in whole or in part, without the prior permission of Elektor in writing. Such written permission must also be obtained before any part of these publications is stored in a retrieval system of any nature. Notwithstanding the above, printed-circuit boards may be produced for private and personal use without prior permission. **Limitation of liability** Elektor shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connexion with, the supply of goods or services by Elektor other than to supply goods as described or, at the option of Elektor, to refund the purchaser any money paid in respect of the goods. **Law** Any question relating to the supply of goods and services by Elektor shall be determined in all respects by the laws of England.

January 2010

SUBSCRIPTION RATES FOR ANNUAL

SUBSCRIPTION

	Standard	Plus
United Kingdom	£49.00	£61.50
Surface Mail		
Rest of the World	£63.00	£75.50
Airmail		
Rest of the World	£79.00	£91.50
USA	£64.95	See www.elektor.com/usa for special offers
Canada	£75.95	

HOW TO PAY

Bank transfer into account no. 40209520 held by Elektor Electronics. with ABN-AMRO Bank, London. IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

Cheque sent by post, made payable to Elektor Electronics. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA and MasterCard can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

SUBSCRIPTION CONDITIONS

The standard subscription order period is twelve months. If a permanent change of address during the subscription period means that copies have to be despatched by a more expensive service, no extra charge will be made. Conversely, no refund will be made, nor expiry date extended, if a change of address allows the use of a cheaper service.

Student applications, which qualify for a 20% (twenty per cent) reduction in current rates, must be supported by evidence of studentship signed by the head of the college, school or university faculty.

A standard Student Subscription costs £39.20, a Student Subscription-Plus costs £51.70 (UK only).

Please note that new subscriptions take about four weeks from receipt of order to become effective.

Cancelled subscriptions will be subject to a charge of 25% (twenty-five per cent) of the full subscription price or £7.50, whichever is the higher, plus the cost of any issues already dispatched. Subscriptions cannot be cancelled after they have run for six months or more.

January 2010



Prototypes Multilayer Professional PCBs



Order custom-designed boards from the Elektor PCB Service

The advantages at a glance

- Professional quality PCBs.
- No film charges or start-up charges.
- No minimum order quantity or charge for this service.
- Available to private and commercial customers.
- Design check applied to all entries. We'll let you know within 4 hours!
- Two PCBs supplied – three produced. If the third board is also okay, you receive it as well – free of charge!

Quick, cheap and secure

www.elektorpcbservice.com

INDEX OF ADVERTISERS

Armaide, Showcase	www.armaide.com	78	HexWax Ltd, Showcase	www.hexwax.com	79
APD, Showcase	www.apdanglia.org.uk	79	Labcenter	www.labcenter.com	88
Atomic Programming Ltd, Showcase	www.atomicprogramming.com	78	MikroElektronika	www.mikroe.com	3
Avit Research, Showcase	www.avitresearch.co.uk	78	MQP Electronics, Showcase	www.mqp.com	79
Beijing Draco Electronics Ltd	www.ezpcb.com	53	Nurve Networks	www.xgamestation.com	53
Beta Layout, Showcase	www.pcb-pool.com	25, 78	Parallax	www.parallax.com	25
Black Robotics, Showcase	www.blackrobotics.com	78	Peak Electronic Design	www.peakelec.co.uk	25
ByVac, Showcase	www.byvac.com	78	Pico	www.picotech.com/scope2002	11
CEDA, Showcase	www.ceda.in	78	Quasar Electronics	www.quasarelectronics.com	39
Decibit Co. Ltd, Showcase	www.decibit.com	78	Robot Electronics, Showcase	www.robot-electronics.co.uk	79
Designer Systems, Showcase	www.designersystems.co.uk	78	Robotiq, Showcase	www.robotiq.co.uk	79
Diamond Systems	www.screenscopetraces.com	13	Showcase		78, 79
Easysync, Showcase	www.easysync.co.uk	78	USB Instruments, Showcase	www.usb-instruments.com	79
Eltec, Showcase	www.eltec.com	78	Virtins Technology, Showcase	www.virtins.com	79
Eurocircuits	www.eurocircuits.com	53			
First Technology Transfer Ltd, Showcase	www.ftt.co.uk	78			
FlexiPanel Ltd, Showcase	www.flexipanel.com	78			
Future Technology Devices, Showcase	www.ftdichip.com	2, 79			
Hameg, Showcase	www.hameg.com	78			

Advertising space for the issue 24 June 2010
may be reserved not later than 25 May 2010

with Huson International Media - Cambridge House - Gogmore Lane - Chertsey, Surrey KT16 9AP - England - Telephone 01932 564 999 - Fax 01932 564 998 - e-mail: ros.elgar@husonmedia.com to whom all correspondence, copy instructions and artwork should be addressed.



GO FASTER WITH PROTEUS PCB DESIGN

The latest version of the Proteus Design Suite harnesses the power of your computer's graphics card to provide lightning fast performance. Together with unique transparency options it's now easier than ever to navigate and understand large, multi-layer boards.

PROTEUS DESIGN SUITE Features:

- Hardware Accelerated Performance.
- Unique Thru-View™ Board Transparency.
- Over 35k Schematic & PCB library parts.
- Integrated Shape Based Auto-router.
- Flexible Design Rule Management.
- Polygonal and Split Power Plane Support.
- Board Autoplacement & Gateswap Optimiser.
- Direct CAD/CAM, ODB++ & PDF Output.
- Integrated 3D Viewer with 3DS and DXF export.
- Mixed Mode SPICE Simulation Engine.
- Co-Simulation of PIC, AVR, 8051 and ARM7.
- Direct Technical Support at no additional cost.

All levels of the Proteus Design Suite include a world class, fully integrated shape-based autorouter at no additional cost - prices start from just £150 exc. VAT & delivery

labcenter  www.labcenter.com
Electronics

Labcenter Electronics Ltd. 53-55 Main Street, Grassington, North Yorks. BD23 5AA.
Registered in England 4692454 Tel: +44 (0)1756 753440, Email: info@labcenter.com

Visit our website or
phone 01756 753440
for more details